

6.1 T Junction resistive divider

Module:6 Microwave Passive circuits
Course: BECE305L – Antenna and Microwave Engineering

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: richards.stanislaus@vit.ac.in



VIT[®]



Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI

Module:6 Microwave Passive circuits 7 hours

- T junction and resistive power divider, Wilkinson power divider, branch line coupler (equal & unequal), Rat Race Coupler, Filter design: Low pass filter (Butterworth and Chebyshev) - Richards transformation and stepped impedance methods.
- Source of the contents: Pozar


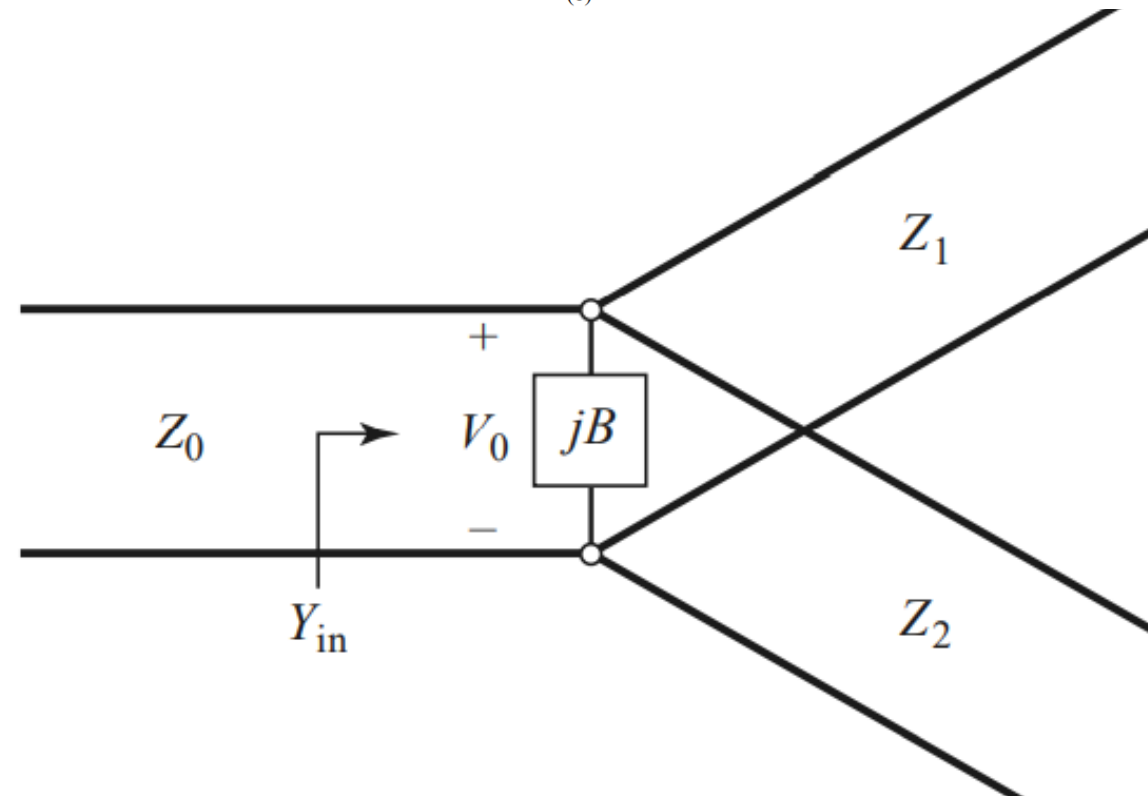
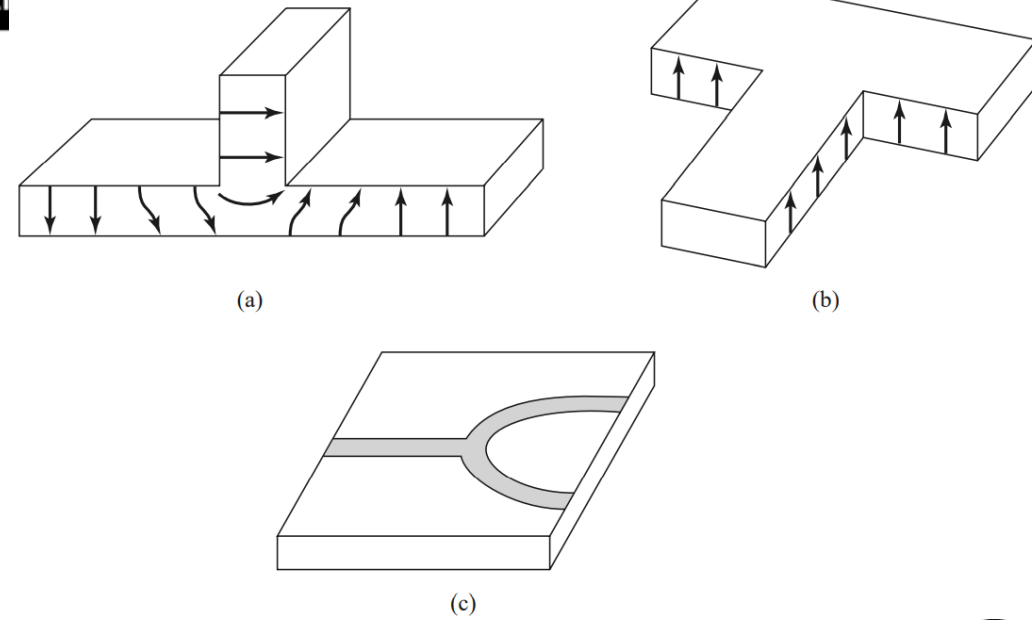
6.1 Lossless T junctions

- E plane T and H plane T
- Fringing fields and higher order modes with **discontinuity at junctions**



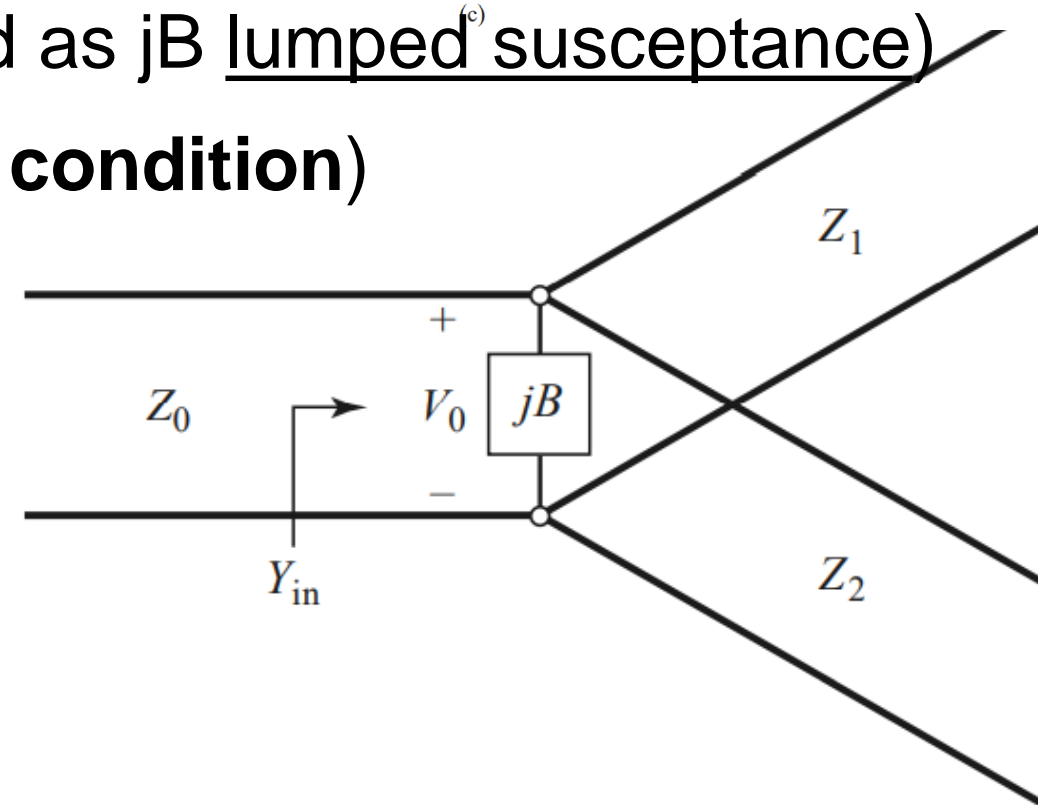
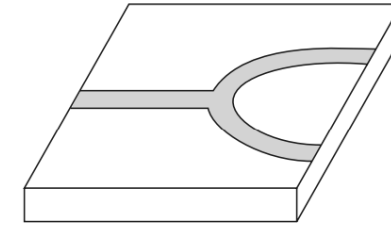
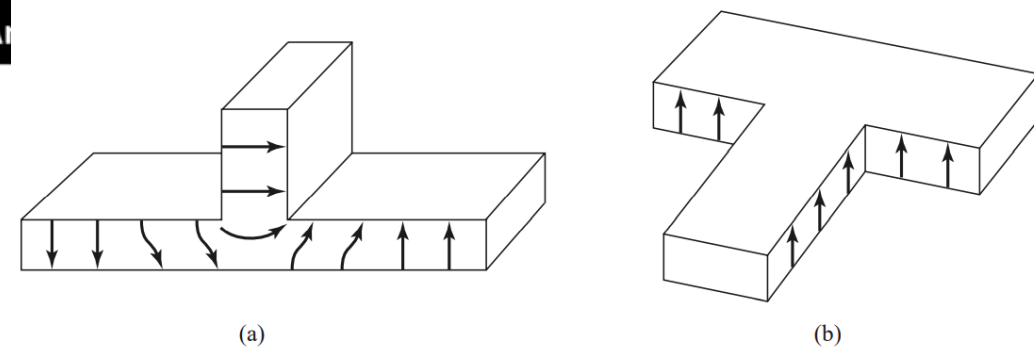
6.1 Lossless T junctions

- E plane T and H plane T
- Fringing fields and higher order modes with discontinuity at junctions
- This results in **stored energy** (modelled as jB lumped ^(c) susceptance)
- $Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$ (**For matched condition**)



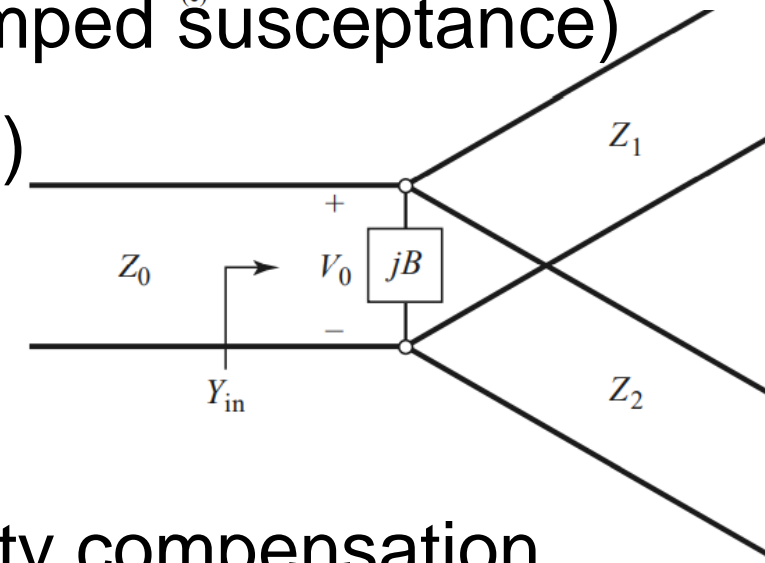
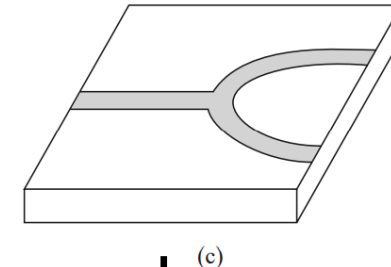
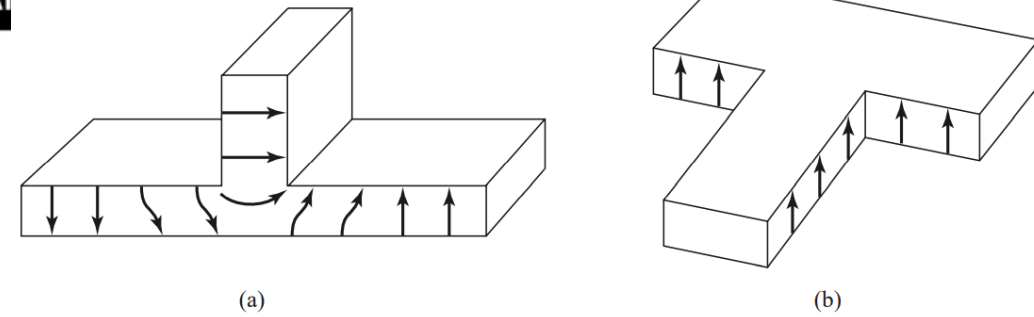
6.1 Lossless T junctions

- E plane T and H plane T
- Fringing fields and higher order modes with discontinuity at junctions
- This results in stored energy (modelled as jB lumped susceptance)
- $Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$ (For matched condition)
- For **lossless transmission lines**
Characteristic impedance is real Z_0
- **Practical case: B is not negligible,**
Additional reactive tuning element or discontinuity compensation



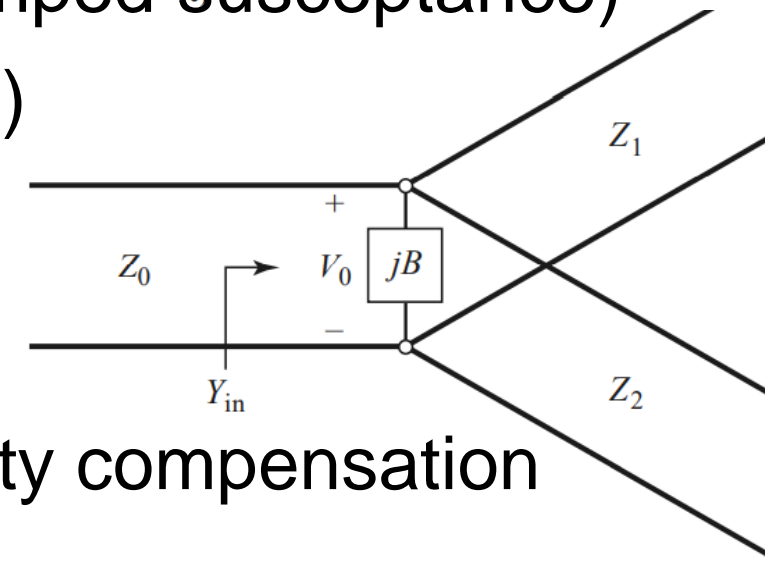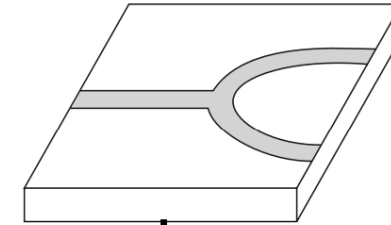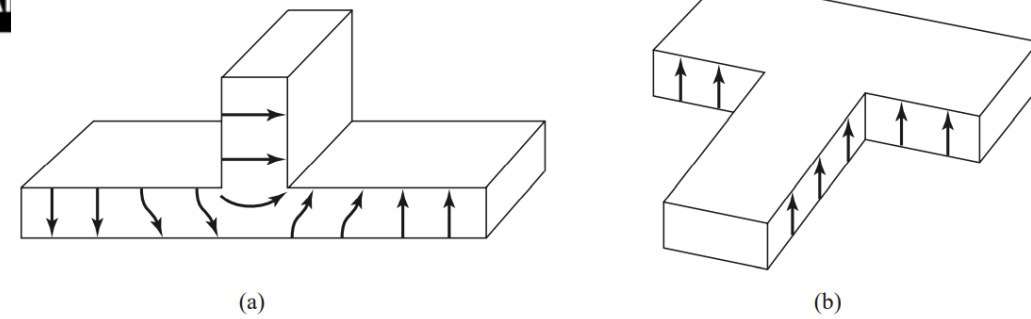
6.1 Lossless T junctions

- E plane T and H plane T
- Fringing fields and higher order modes with discontinuity at junctions
- This results in stored energy (modelled as jB lumped susceptance)
- $Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$ (For matched condition)
- For lossless transmission lines
Characteristic impedance is real Z_0
- Practical case: B is not negligible,
Additional reactive tuning element or discontinuity compensation
- **Ideal case:** $jB = 0 \quad \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$



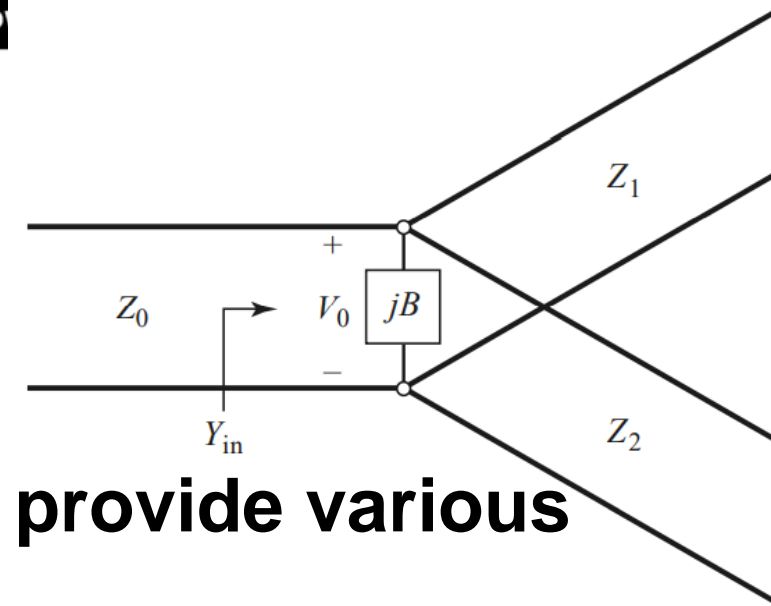
6.1 Lossless T junctions

- **Ideal case:** $jB = 0$ $\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$
- Output line impedances Z_1 and Z_2 - **selected to provide various power divisions.**
-



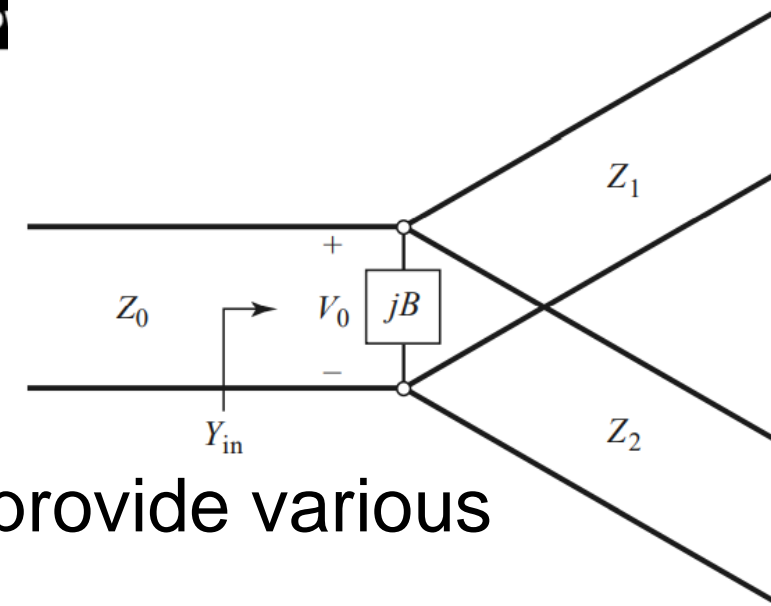
6.1 Lossless T junctions

- Ideal case: $jB = 0$ $\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$
- Output line impedances Z_1 and Z_2 - selected to provide various power divisions.
- **3dB(equal split) power divider:**
For a $Z_0 = 50\Omega$ input line, the **output lines can be made as two 100 Ω lines.**



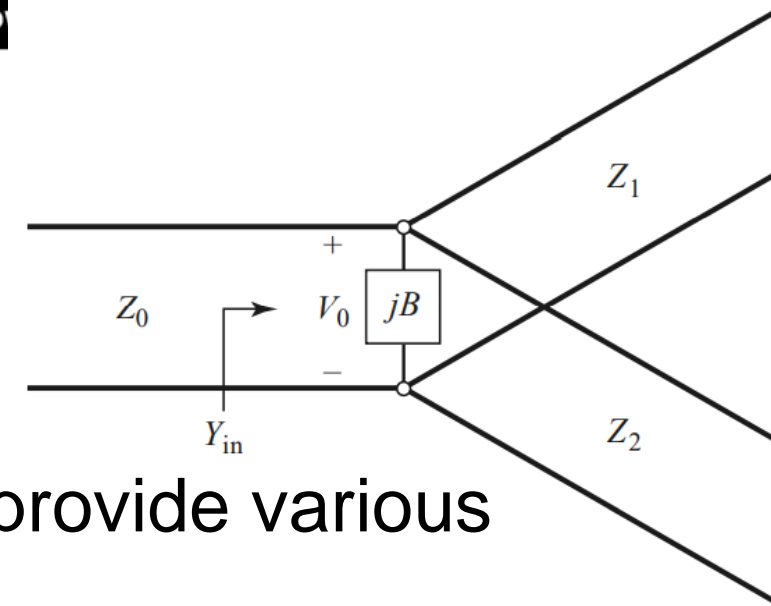
6.1 Lossless T junctions

- Ideal case: $jB = 0$ $\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$
 - Output line impedances Z_1 and Z_2 - selected to provide various power divisions.
 - 3dB(equal split) power divider:
For a $Z_0 = 50\Omega$ input line, the output lines can be made as two 100Ω lines.
- Quarter wave transformers** can be used to bring output lines at 50Ω .



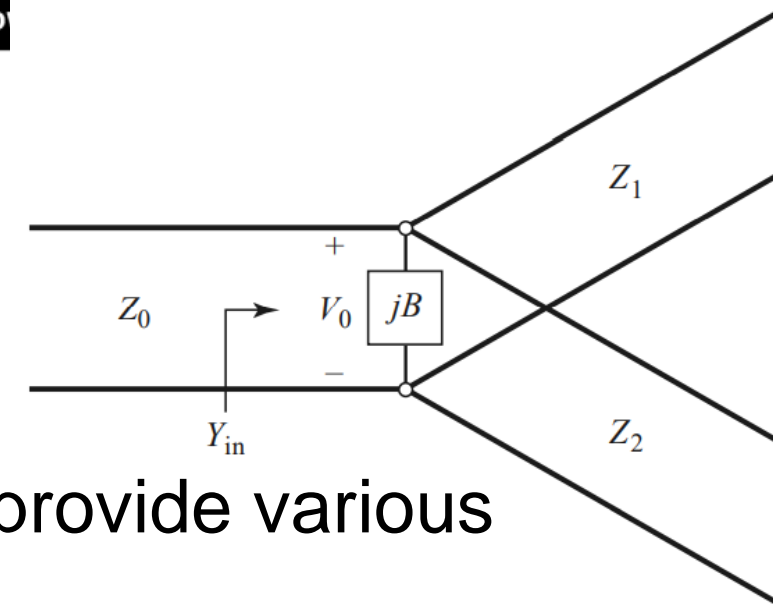6.1 Lossless T junctions

- Ideal case: $jB = 0$ $\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$
- Output line impedances Z_1 and Z_2 - selected to provide various power divisions.
- 3dB(equal split) power divider:
For a $Z_0 = 50\Omega$ input line, the output lines can be made as two 100Ω lines.



Quarter wave transformers can be used to bring output lines at 50Ω .


For matched output lines, input will also be matched.

Disadvantage: No isolation between two output ports

Mismatch looking into output ports

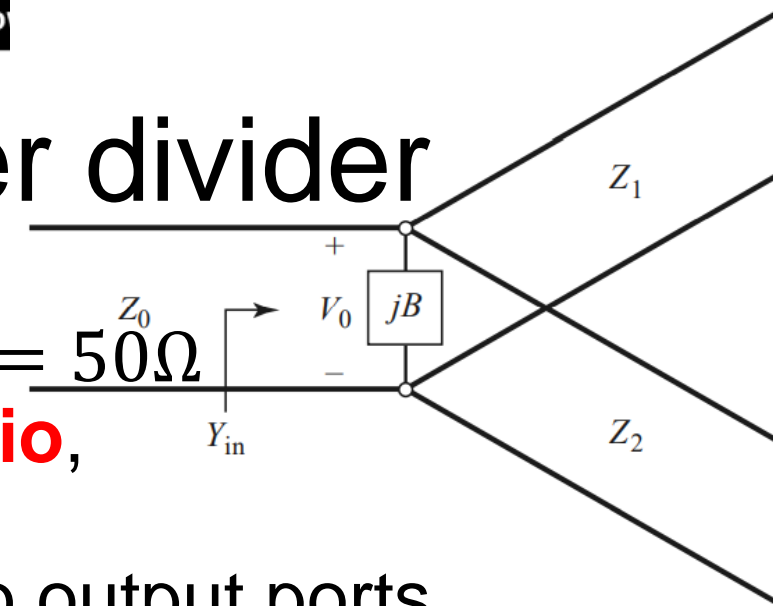
6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
 For output powers in **two ports to be in 2:1 ratio**,
 Find output characteristic impedances.
 Compute reflection coefficients seen looking into output ports.



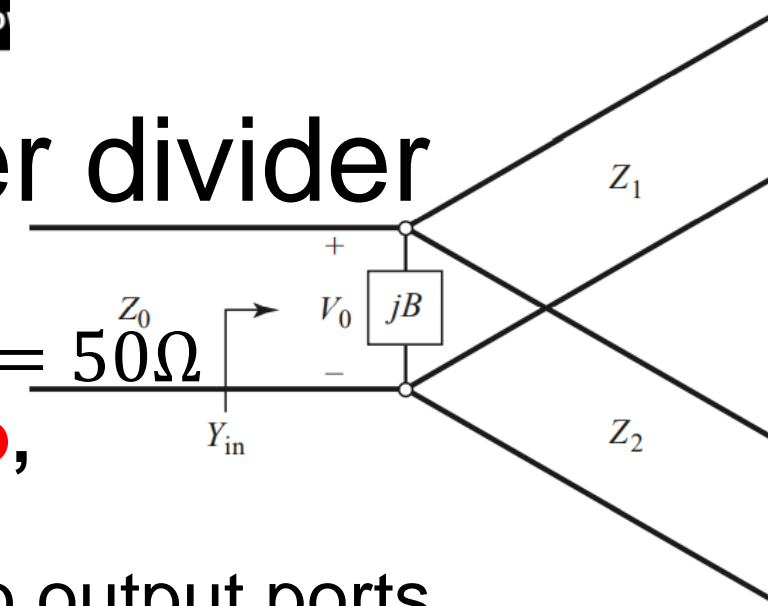6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in **2: 1 ratio**,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.




- Voltage at junction** is V_0 ,

Input power into matched divider: $P_{in} = \frac{1}{2} \frac{V_0^2}{Z_0}$ while

output powers are $P_1 = \frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} P_{in}$ and $P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} P_{in}$

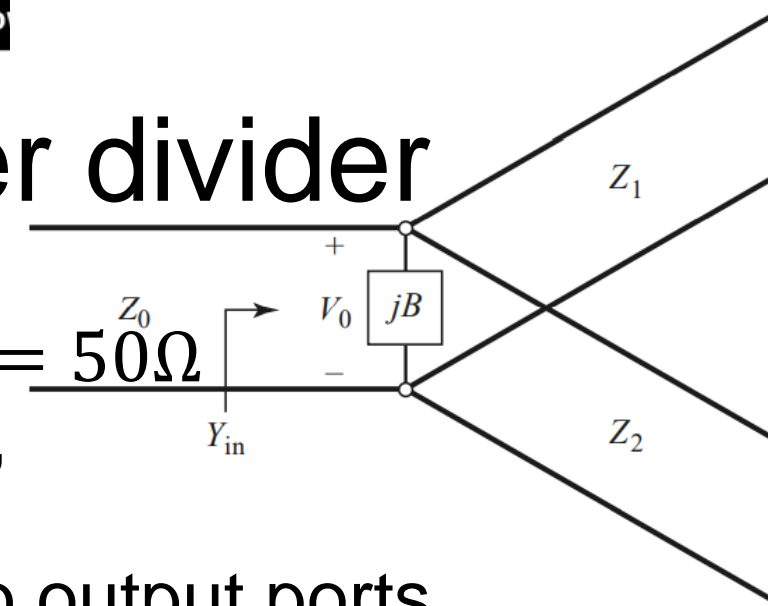6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.



- Voltage at junction is V_0 ,


Input power into matched divider: $P_{in} = \frac{1}{2} \frac{V_0^2}{Z_0}$ while

output powers are $P_1 = \frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} P_{in}$ and $P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} P_{in}$

$$\frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} \left(\frac{1}{2} \frac{V_0^2}{Z_0} \right) \quad \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} \left(\frac{1}{2} \frac{V_0^2}{Z_0} \right)$$

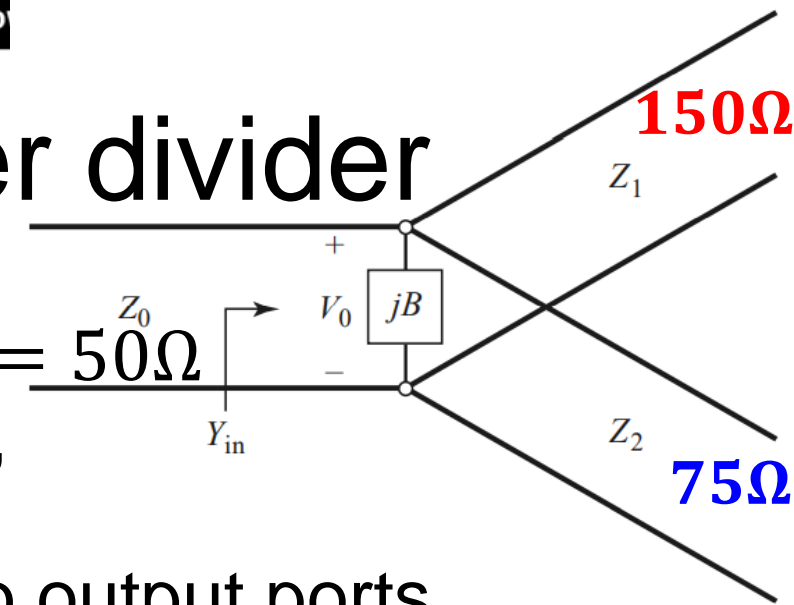6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.



- Voltage at junction is V_0 ,

Input power into matched divider: $P_{in} = \frac{1}{2} \frac{V_0^2}{Z_0}$ while


$$\text{output powers are } P_1 = \frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} P_{in} \text{ and } P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} P_{in}$$

$$\frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} \left(\frac{1}{2} \frac{V_0^2}{Z_0} \right) \quad \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} \left(\frac{1}{2} \frac{V_0^2}{Z_0} \right)$$

$$Z_1 = 3Z_0 = 150\Omega \quad Z_2 = \frac{3Z_0}{2} = 75\Omega$$

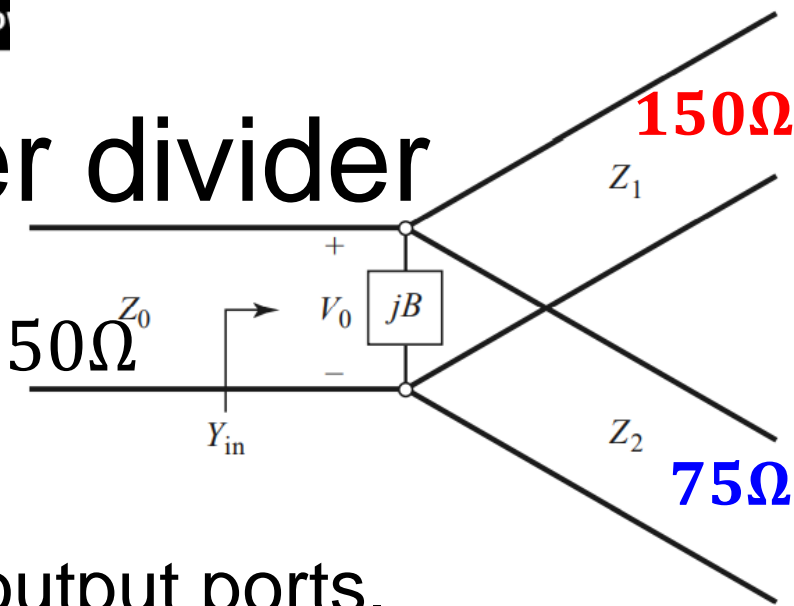6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.




- $Z_1 = 3Z_0 = 150\Omega$ $Z_2 = \frac{3Z_0}{2} = 75\Omega$

Input impedance at the transmission lines act as load to that line.

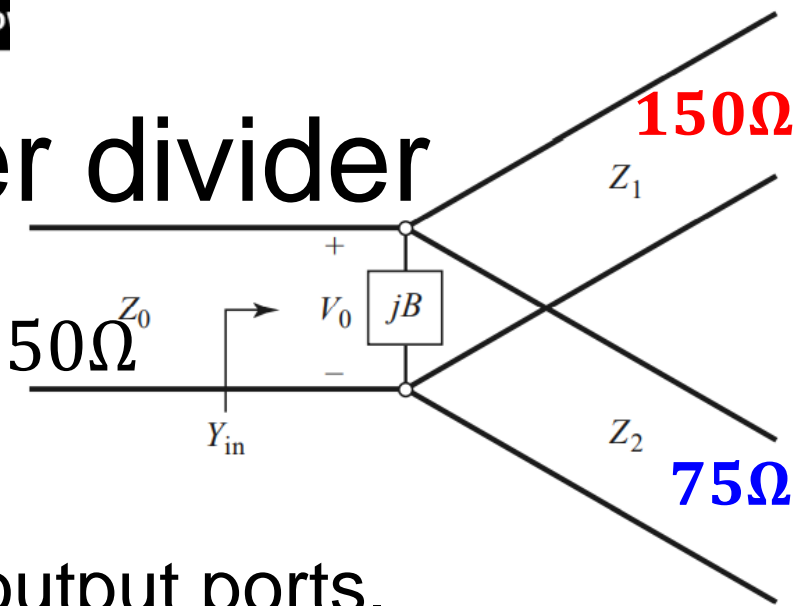6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.



- $$Z_1 = 3Z_0 = 150\Omega \quad Z_2 = \frac{3Z_0}{2} = 75\Omega$$


Input impedance at the transmission lines act as load to that line.

When seen from Z_1 , input impedance of $50 \parallel 75 = 30\Omega$

When seen from Z_2 , input impedance of $50 \parallel 150 = 37.5\Omega$

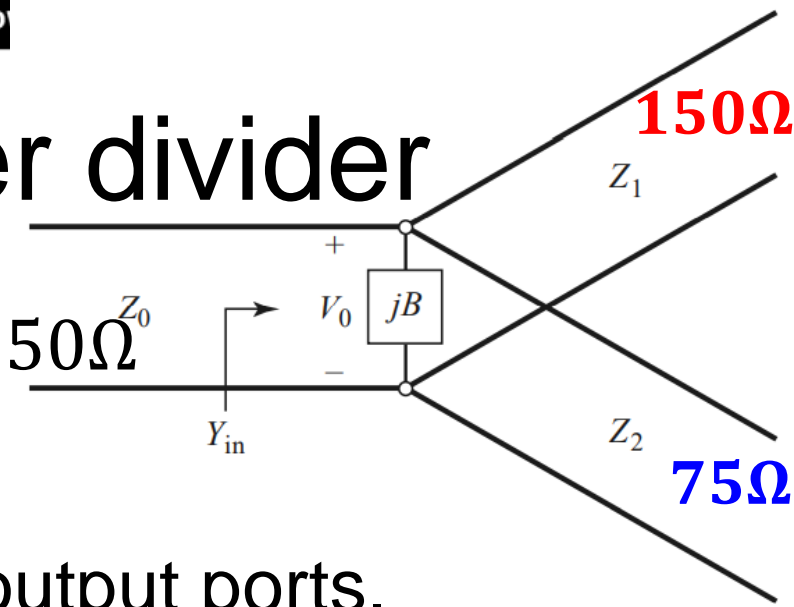6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.



- $$Z_1 = 3Z_0 = 150\Omega \quad Z_2 = \frac{3Z_0}{2} = 75\Omega$$

Input impedance at the transmission lines act as load to that line.

When seen from Z_1 , input impedance of $50 \parallel 75 = 30\Omega$


When seen from Z_2 , input impedance of $50 \parallel 150 = 37.5\Omega$

- The respective reflection coefficients seen looking into these ports are:

$$\Gamma_1 = \frac{Z_{in1} - Z_1}{Z_{in1} + Z_1} = \frac{30 - 150}{30 + 150} = -0.667 \quad \text{and}$$

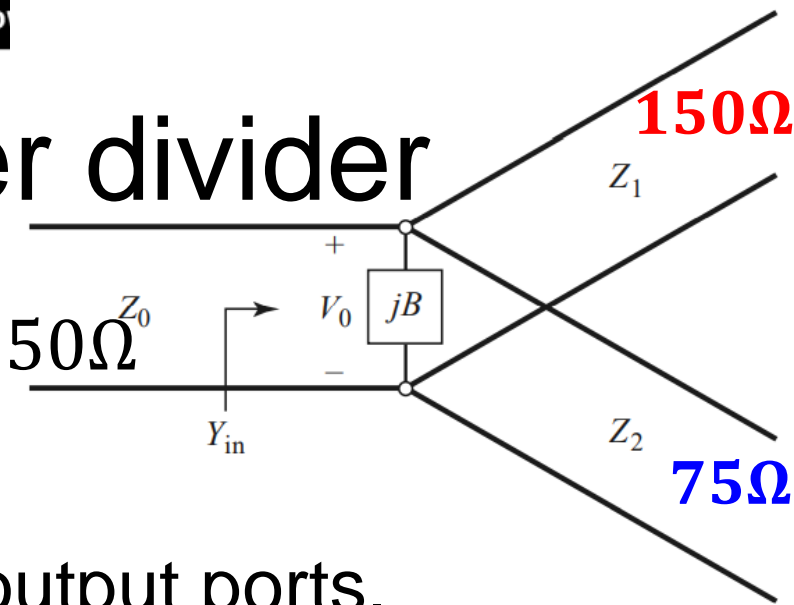6.2 Problem on T junction power divider

- A lossless T junction power divider – Source $Z_0 = 50\Omega$
For output powers in two ports to be in 2: 1 ratio,
Find output characteristic impedances.
Compute reflection coefficients seen looking into output ports.



- $$Z_1 = 3Z_0 = 150\Omega \quad Z_2 = \frac{3Z_0}{2} = 75\Omega$$

Input impedance at the transmission lines act as load to that line.

When seen from Z_1 , input impedance of $50 \parallel 75 = 30\Omega$

When seen from Z_2 , input impedance of $50 \parallel 150 = 37.5\Omega$

- The respective reflection coefficients seen looking into these ports are:


$$\Gamma_1 = \frac{Z_{in1} - Z_1}{Z_{in1} + Z_1} = \frac{30 - 150}{30 + 150} = -0.667 \quad \text{and} \quad \Gamma_2 = \frac{Z_{in2} - Z_2}{Z_{in2} + Z_2} = \frac{37.5 - 150}{37.5 + 150} = -0.333$$

6.3 Resistive divider

- **Three port divider contains lossy components**


Can be made to be matched at all ports

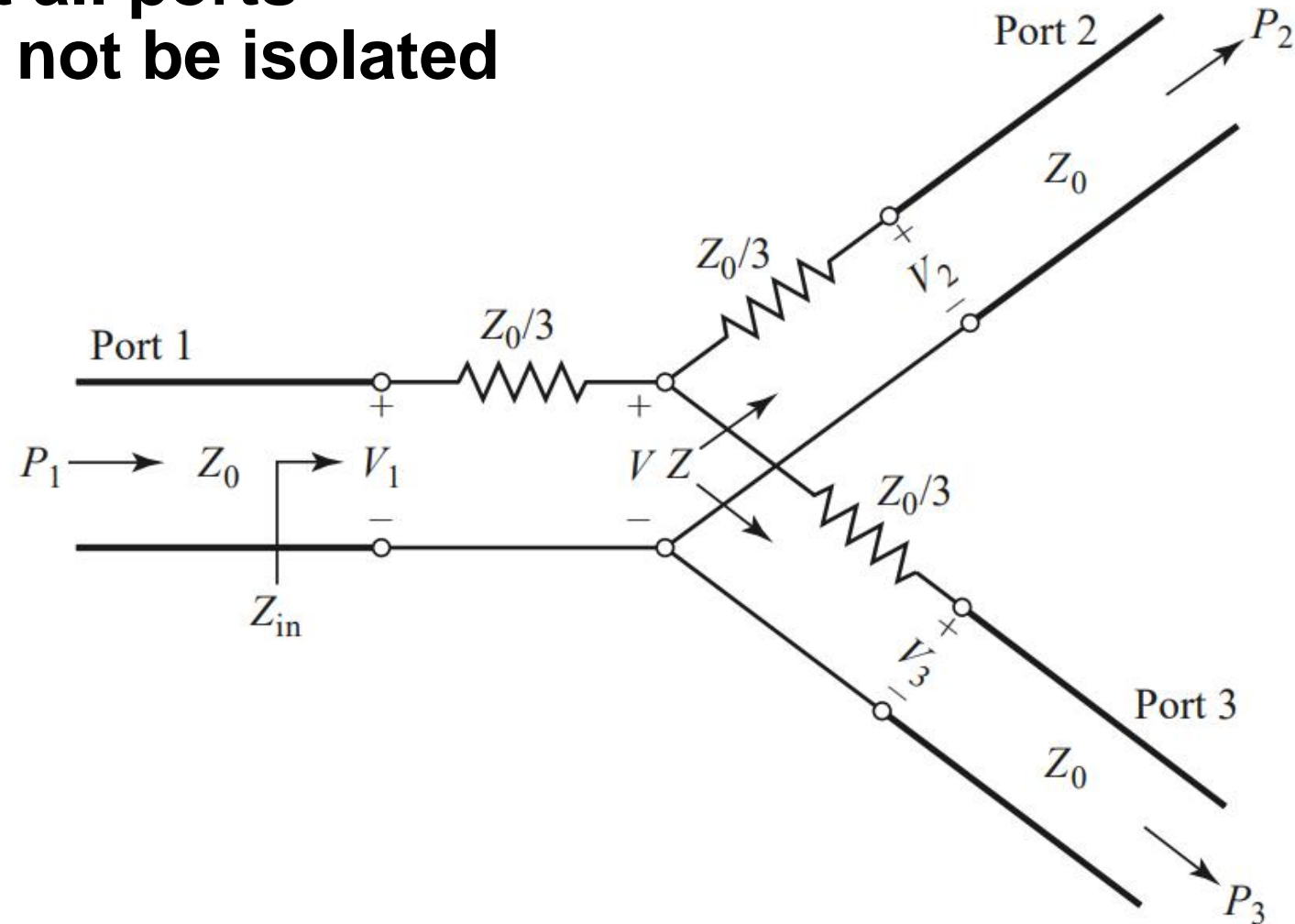Though **two output ports may not be isolated**



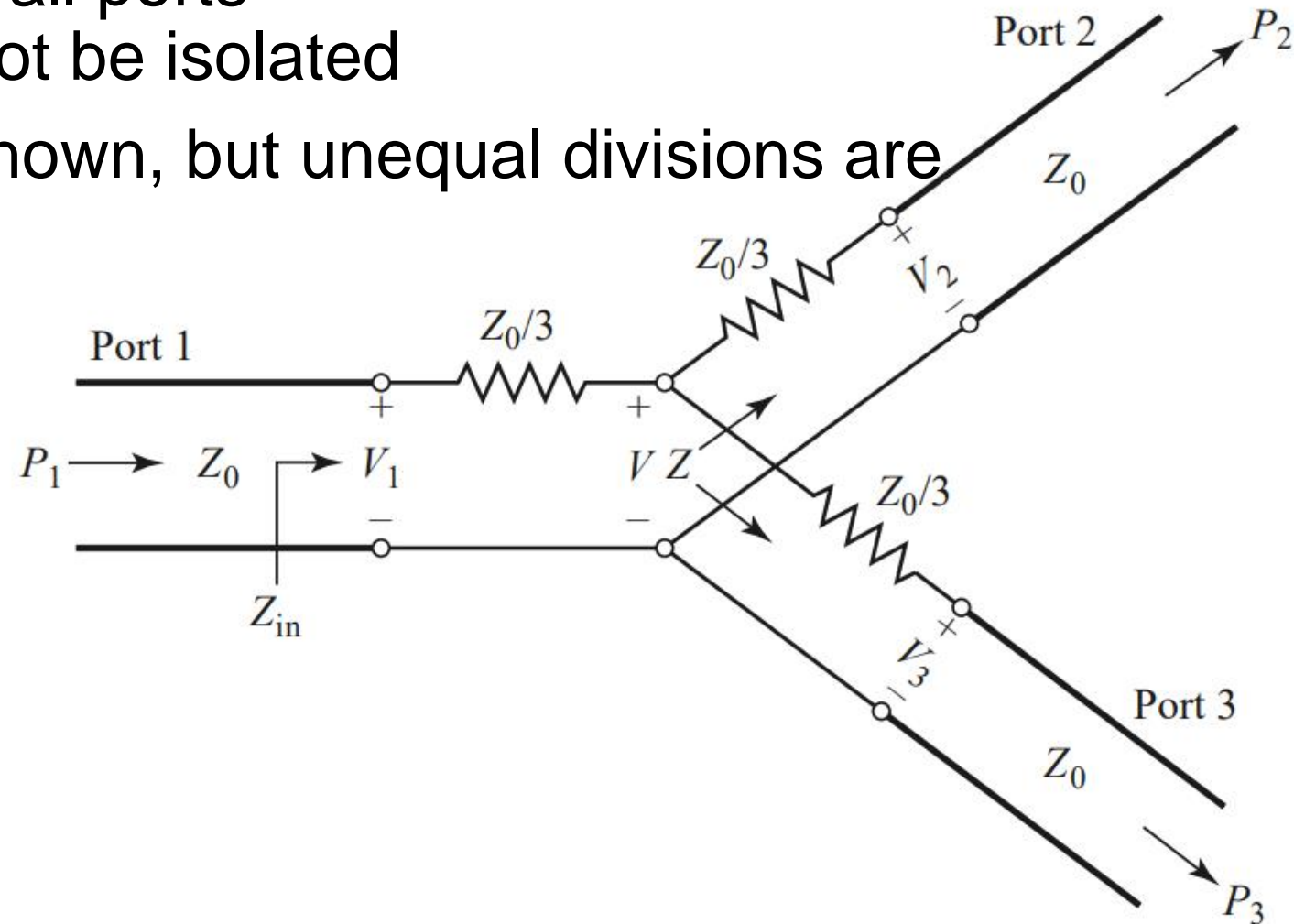
6.3 Resistive divider

- Three port divider contains lossy components
Can be made to be matched at all ports
Though two output ports may not be isolated
- **Equal split** ($-3dB$) divider is shown, but unequal divisions are possible.



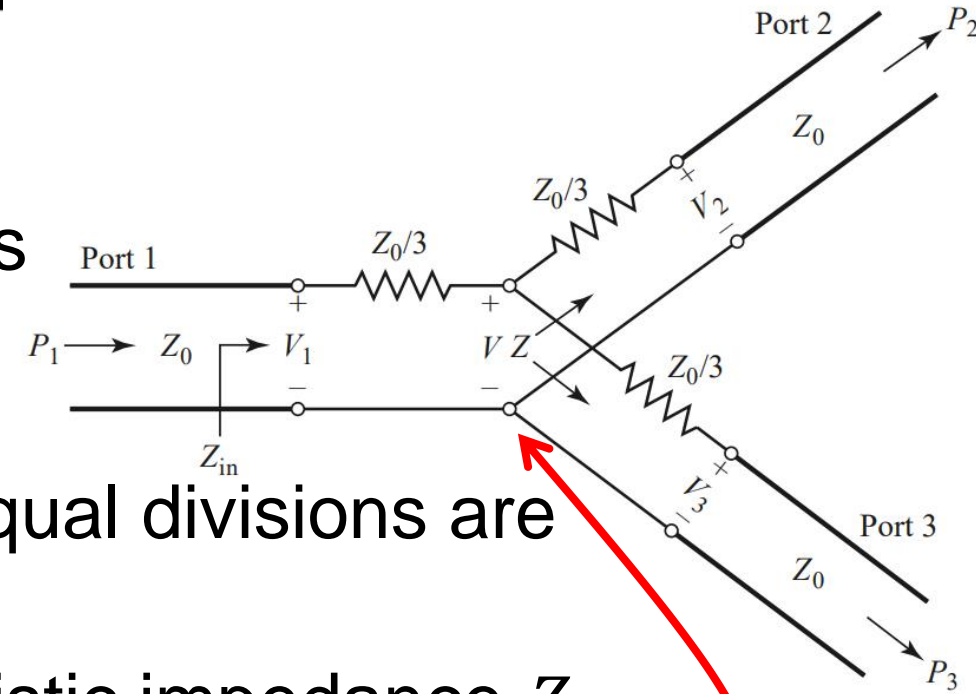
6.3 Resistive divider

- Three port divider contains lossy components
Can be made to be matched at all ports
Though two output ports may not be isolated
- Equal split ($-3dB$) divider is shown, but unequal divisions are possible.
- Assume all ports are terminated in characteristic impedance Z_0 .
With terminated output line, the impedance Z observed at junction is $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$



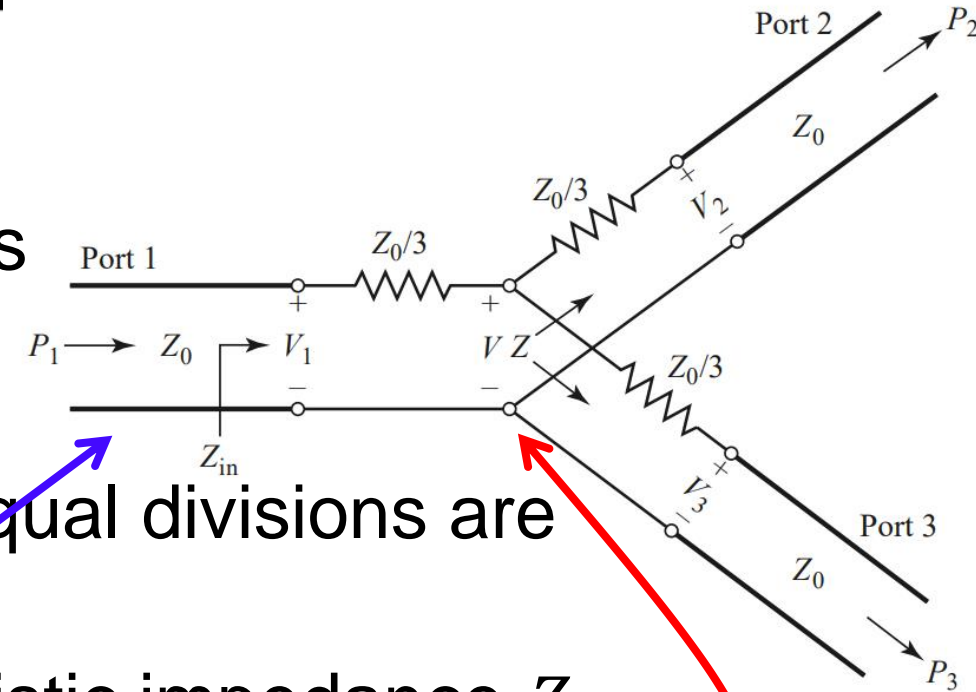
6.3 Resistive divider

- Three port divider contains lossy components
Can be made to be matched at all ports
Though two output ports may not be isolated
- Equal split ($-3dB$) divider is shown, but unequal divisions are possible.
- Assume all ports are terminated in characteristic impedance Z_0 .
With terminated output line, the impedance Z observed at junction is $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$
- At input, **Input impedance of the divider** $Z_{in} = \frac{Z_0}{3} + (Z \parallel Z)$



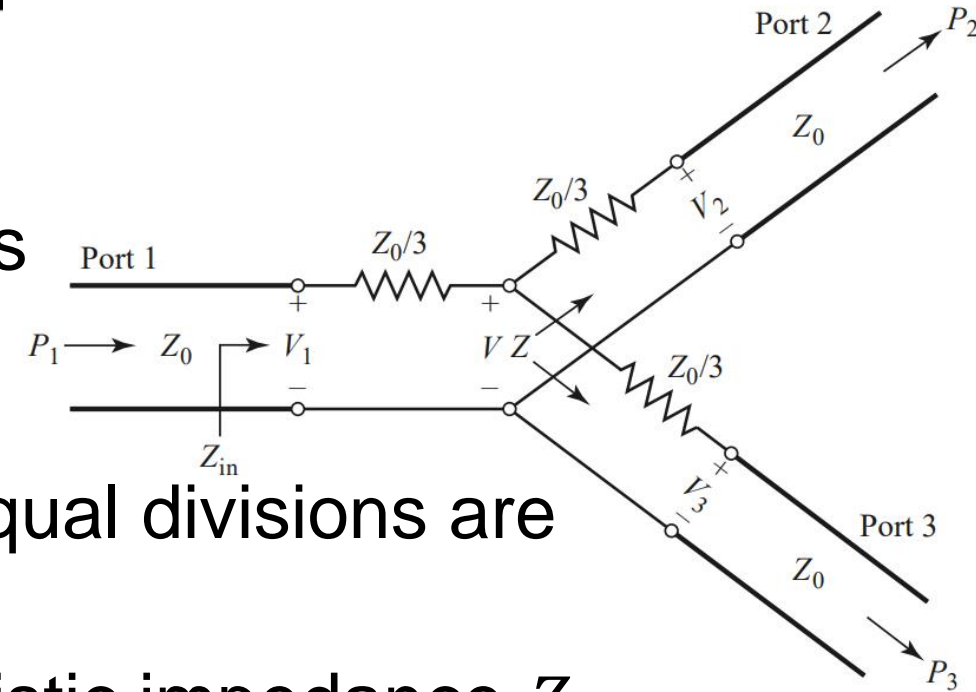6.3 Resistive divider

- Three port divider contains lossy components
Can be made to be matched at all ports
Though two output ports may not be isolated
- Equal split ($-3dB$) divider is shown, but unequal divisions are possible.
- Assume all ports are terminated in characteristic impedance Z_0 .
With terminated output line, the impedance Z observed at junction is $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$
- At input, Input impedance of the divider $Z_{in} = \frac{Z_0}{3} + (Z \parallel Z)$
 $Z_{in} = \frac{Z_0}{3} + \frac{2Z_0}{3} = Z_0$ (Input is matched to feed line).
- Same can be verified from all ports: $S_{11} = S_{22} = S_{33} = 0$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$

- Voltage at junction when looked from port 1
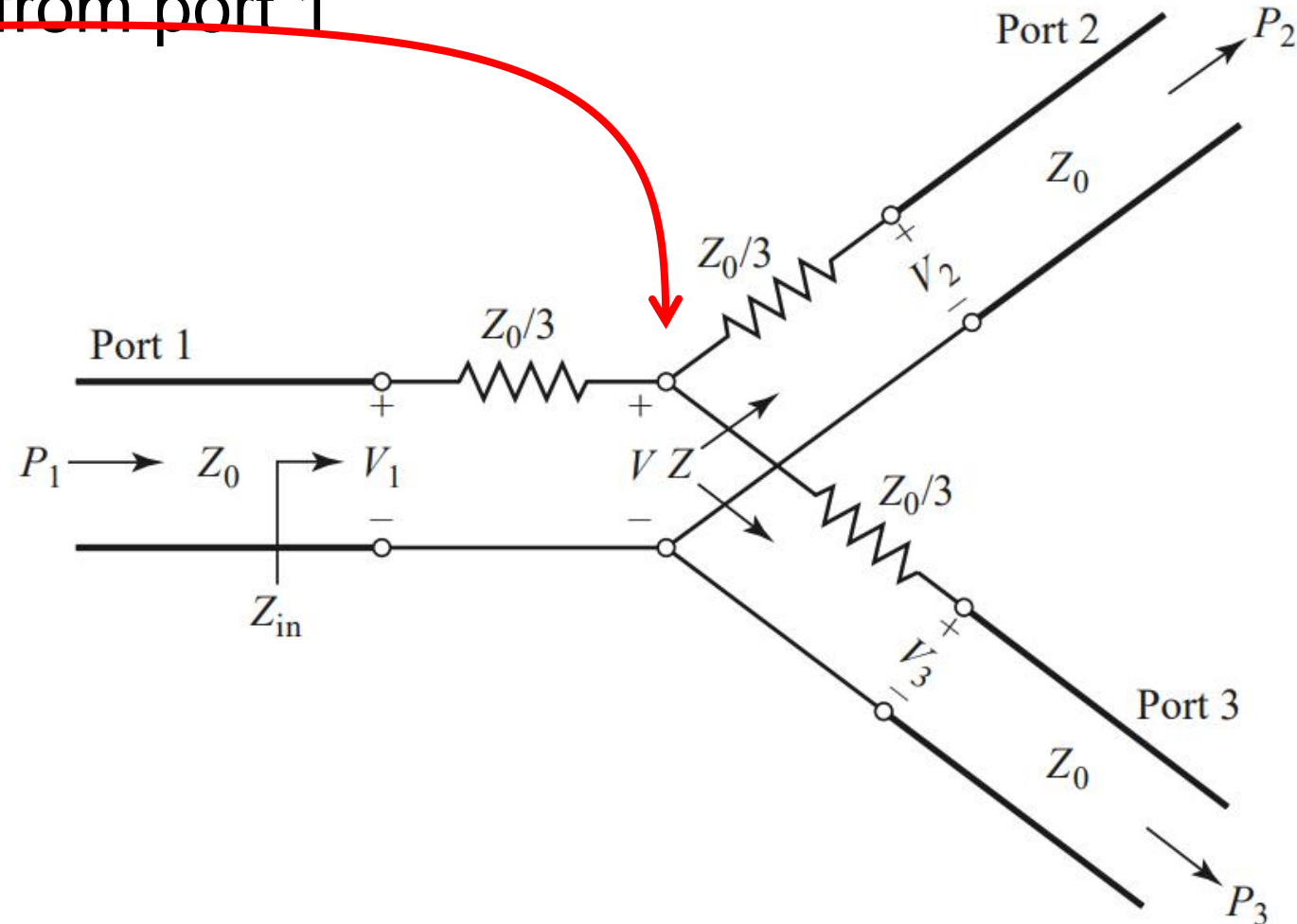
$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} =$$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$

- Voltage at junction when looked from port 1
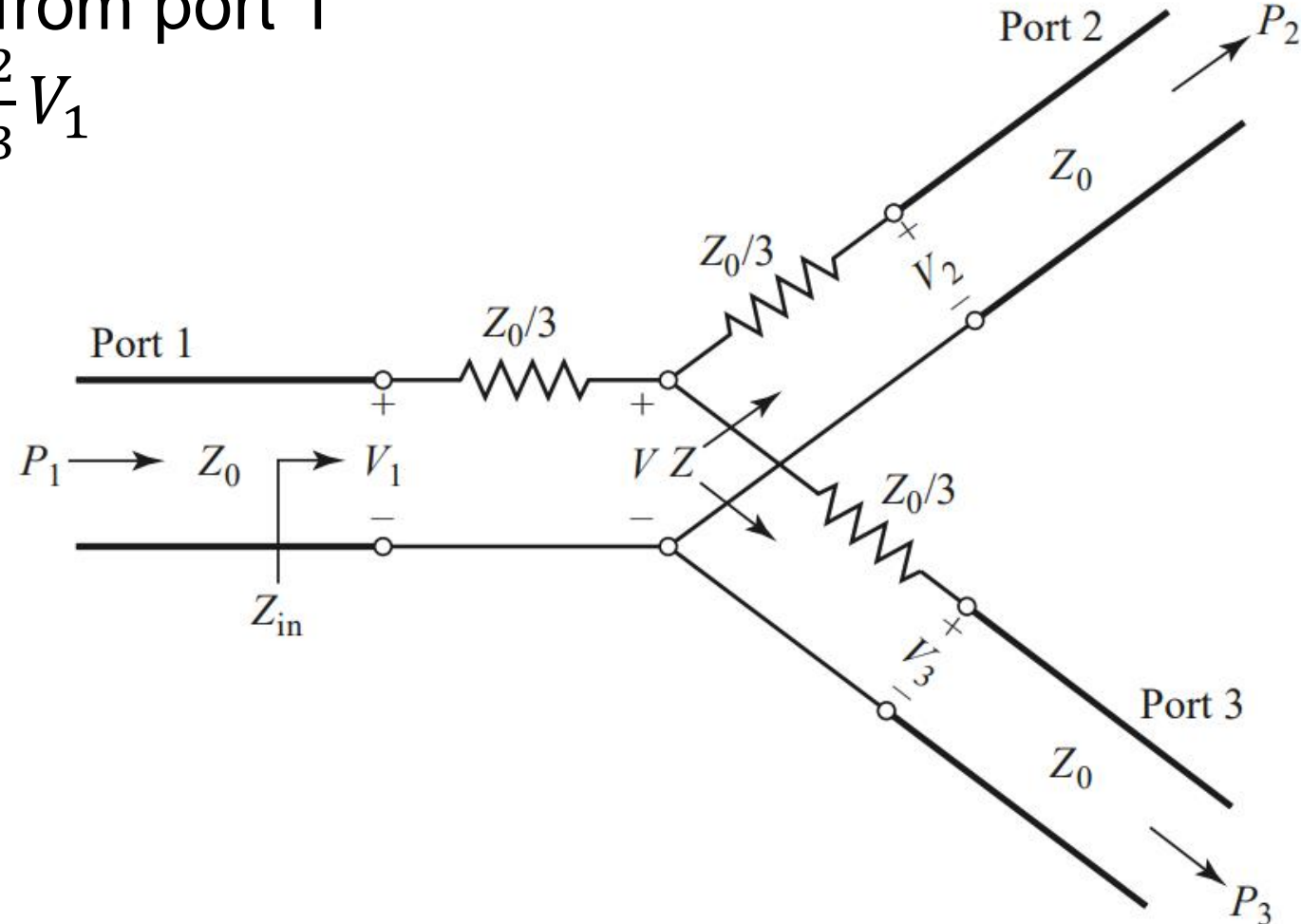
$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$



6.3 Resistive divider


- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$

- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$

- Output voltage at ports 2 and 3
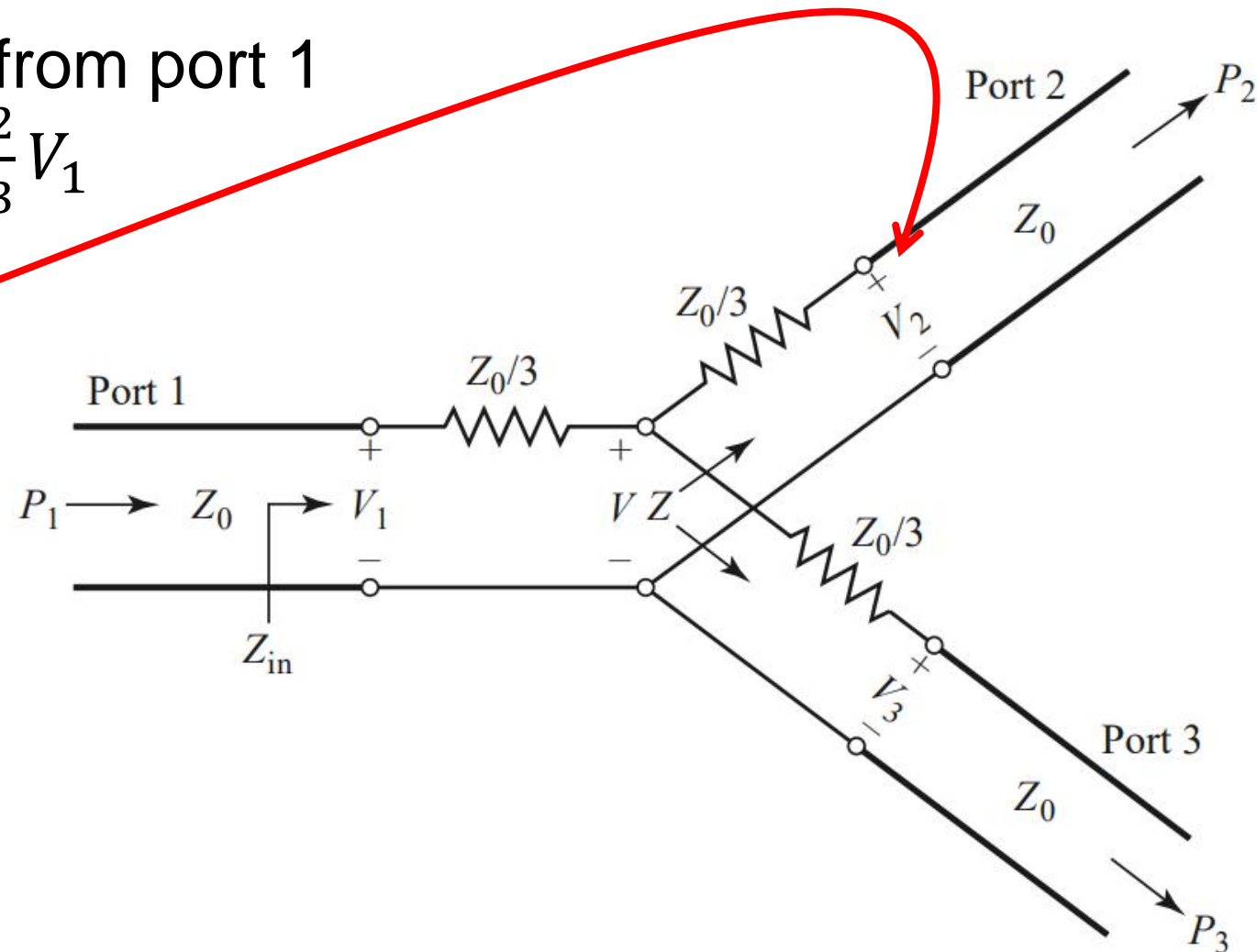
$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V =$$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$
- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$
- Output voltage at ports 2 and 3
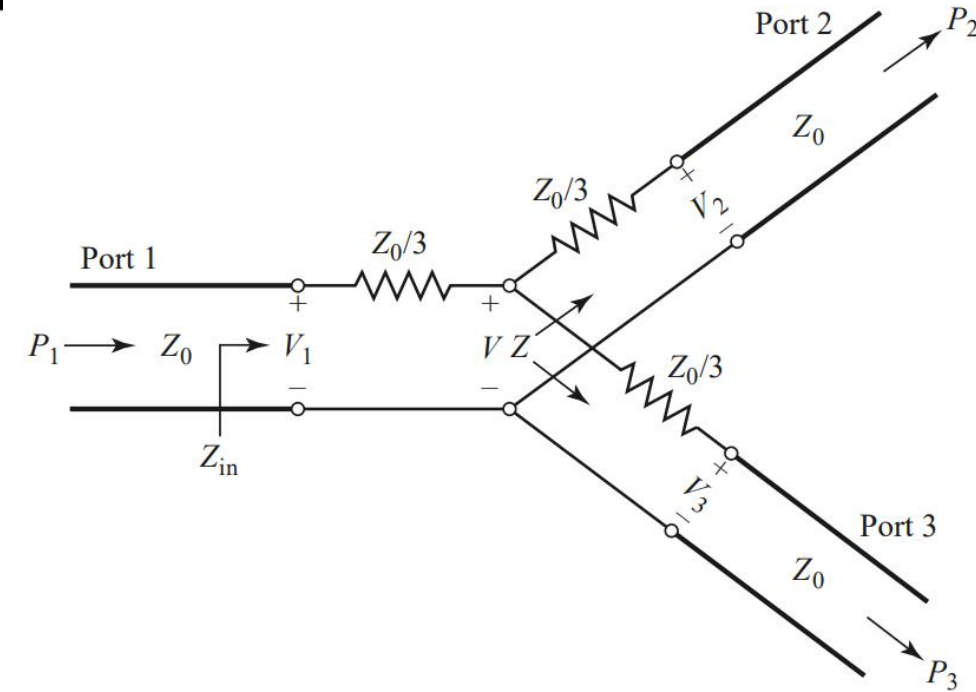
$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V = \frac{3}{4} \left(\frac{2}{3} V_1 \right) = \frac{1}{2} V_1$$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$
- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$
- Output voltage at ports 2 and 3
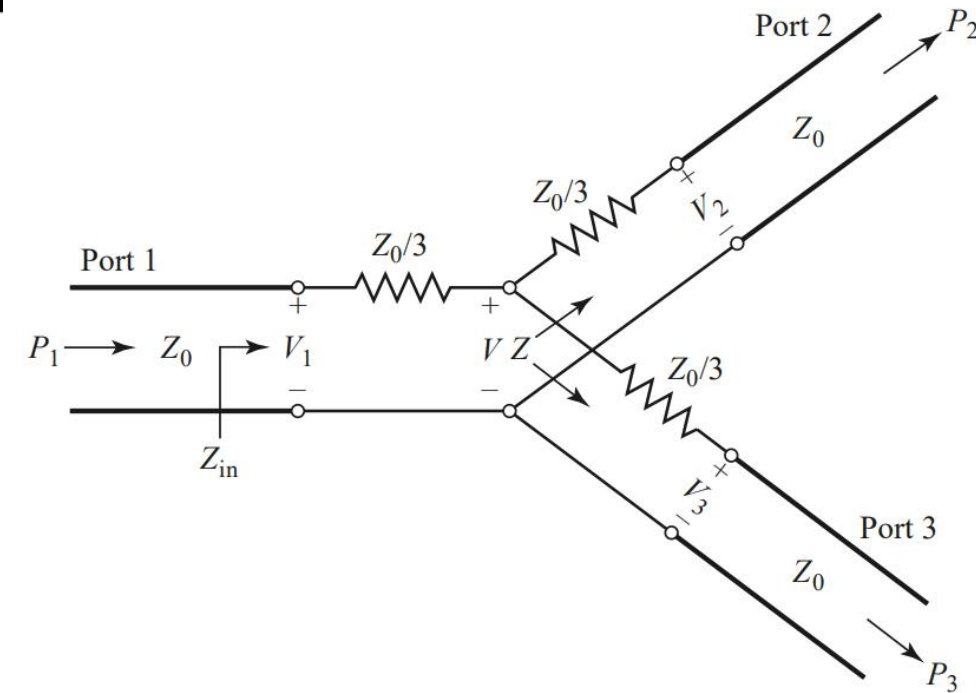
$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V = \frac{3}{4} \left(\frac{2}{3} V_1 \right) = \frac{1}{2} V_1$$
- *S parameters* $S_{21} = S_{31} = S_{23} = \frac{1}{2}$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$
- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$
- Output voltage at ports 2 and 3
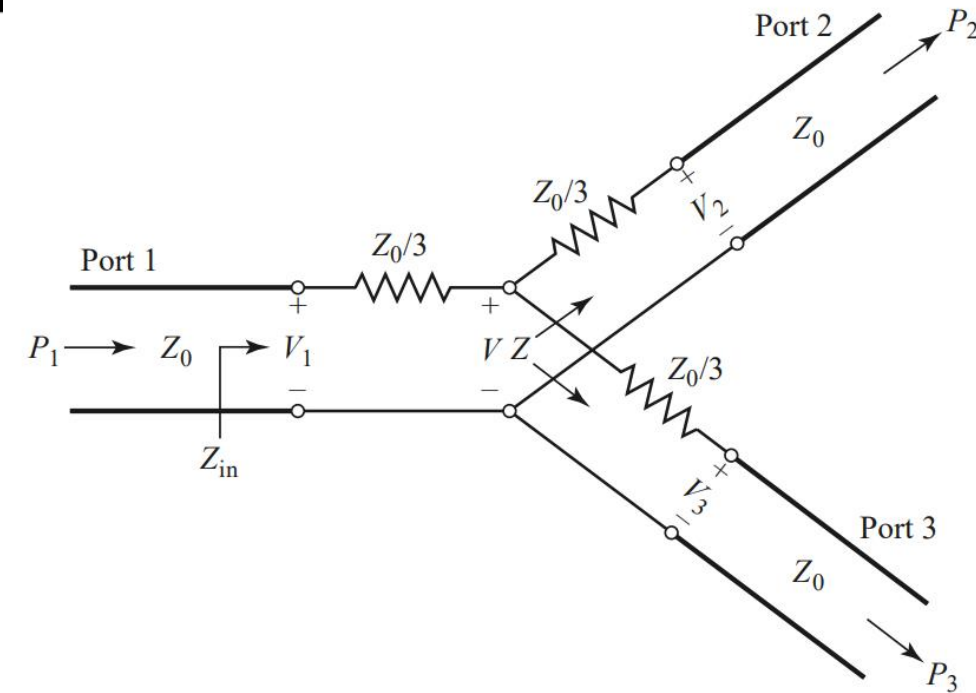
$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V = \frac{3}{4} \left(\frac{2}{3} V_1 \right) = \frac{1}{2} V_1$$
- *S parameters* $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
- *Reciprocal network:* $[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$




6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$
- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$
- Output voltage at ports 2 and 3

$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V = \frac{3}{4} \left(\frac{2}{3} V_1 \right) = \frac{1}{2} V_1$$
- *S parameters* $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
- *Reciprocal network:* $[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$
- With input at port 1, $P_1 = \frac{1}{2} \frac{V_1^2}{Z_0}$ $P_2 = P_3 = \frac{1}{2} \frac{V_2^2}{Z_0} = \frac{1}{4} P_1$ (6dB below input power level)

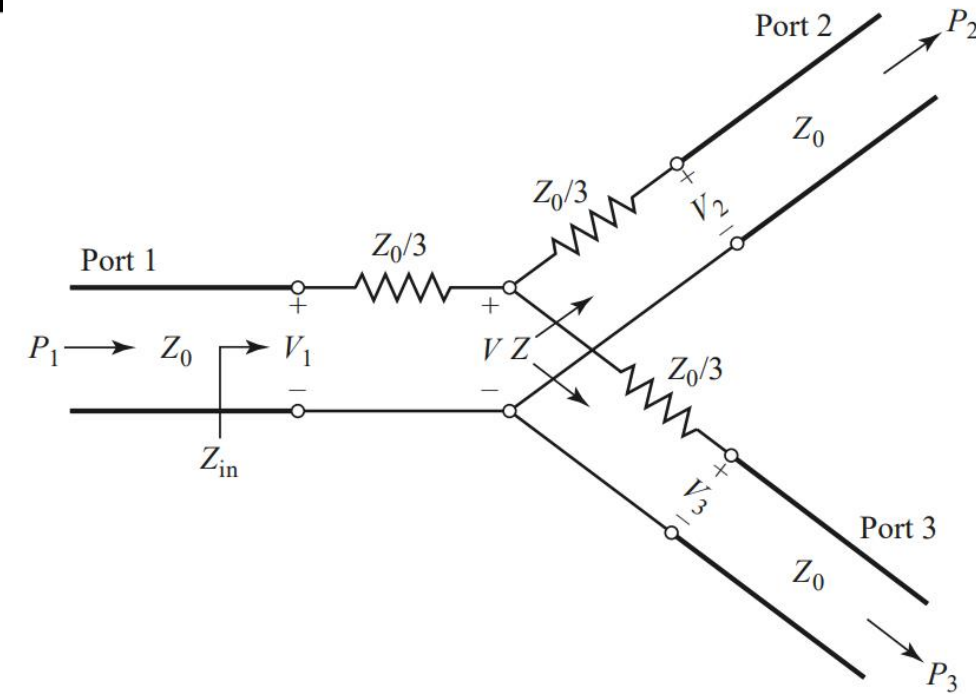


6.3 Resistive divider

- $Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$ $S_{11} = S_{22} = S_{33} = 0$
- Voltage at junction when looked from port 1

$$V = V_1 \frac{Z \parallel Z}{Z \parallel Z + Z_0/3} = V_1 \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} V_1$$
- Output voltage at ports 2 and 3
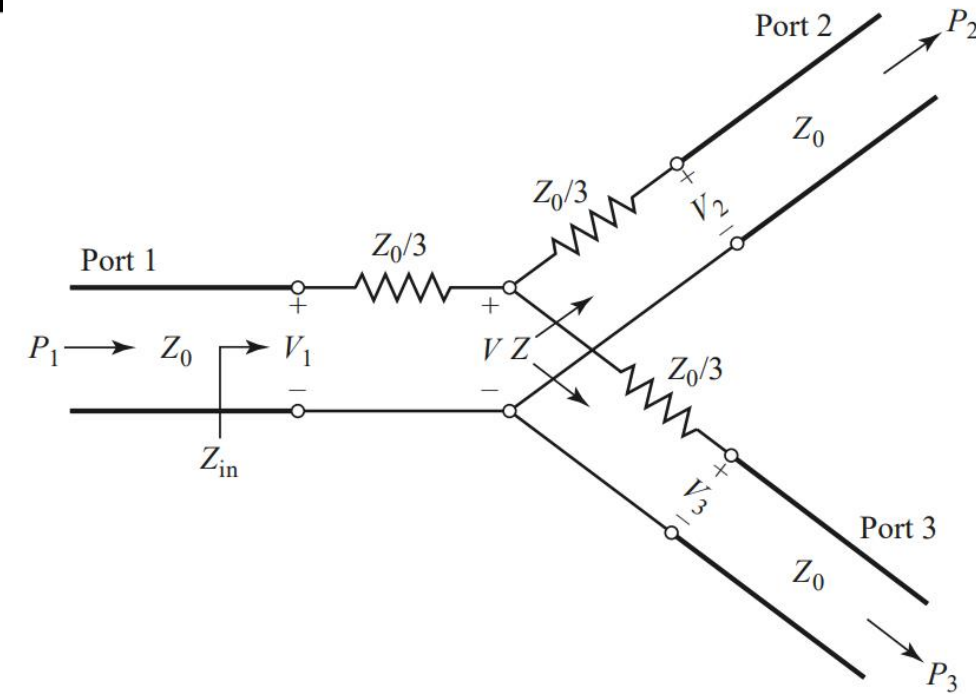
$$V_2 = V_3 = V \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} V = \frac{3}{4} \left(\frac{2}{3} V_1 \right) = \frac{1}{2} V_1$$
- *S parameters* $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
- *Reciprocal network:* $[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$
- With input at port 1, $P_1 = \frac{1}{2} \frac{V_1^2}{Z_0}$ (input power level)



Power delivered to ports = $P_2 + P_3 = \frac{1}{2} P_1$

The remaining power $\frac{1}{2} P_1$ is lost in the resistors.

$$P_2 = P_3 = \frac{1}{2} \frac{V_2^2}{Z_0} = \frac{1}{4} P_1 \text{ (6dB below input power level)}$$