

5.1a S Parameter Problem

Module:5 Microwave Passive components
Course: BECE305L – Antenna and Microwave Engineering

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: richards.stanislaus@vit.ac.in



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI


Module:5 Microwave Passive components

6 hours

- Microwave Networks - ABCD, 'S' parameter and its properties. E-Plane Tee, H-Plane Tee, Magic Tee and Multi-hole directional coupler. Principle of Faraday rotation, isolator, circulator and phase shifter.
- Source of the contents: Book by Pozar
-

Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

- $\frac{Z_1}{2} = \frac{17.12}{2} = 8.56$
- $S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$

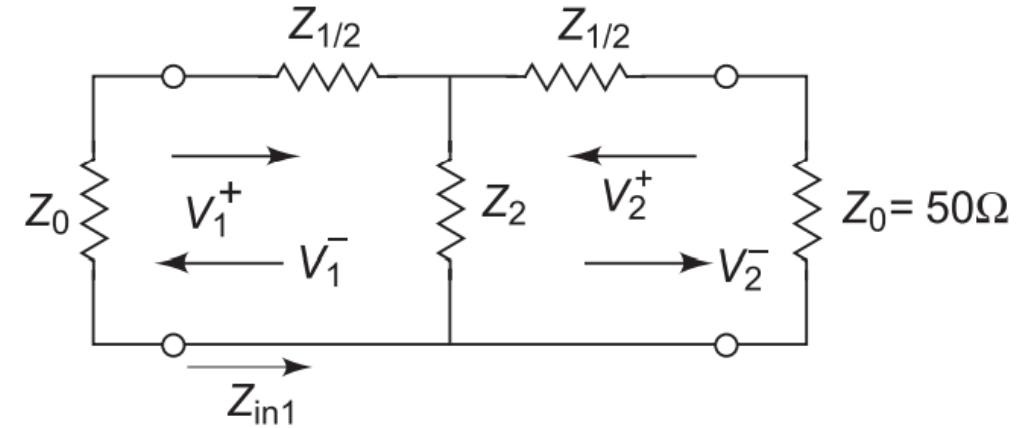


Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$\bullet \frac{Z_1}{2} = \frac{17.12}{2} = 8.56$$

$$\bullet S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$
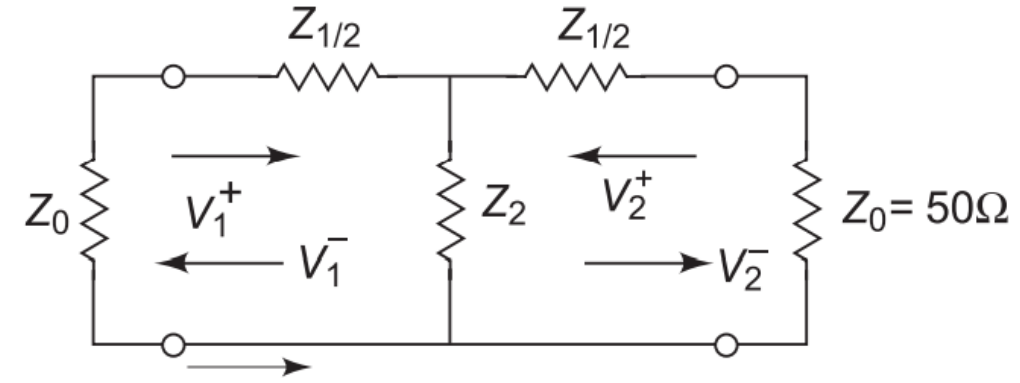
$$Z_{in1} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right) = 8.56 + \frac{141.78 \times (8.56 + 50)}{141.78 + (8.85 + 50)} = 50$$




Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$\bullet \frac{Z_1}{2} = \frac{17.12}{2} = 8.56$$

$$\bullet S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$

$$Z_{in1} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right) = 8.56 + \frac{141.78 \times (8.56 + 50)}{141.78 + (8.85 + 50)} = 50$$
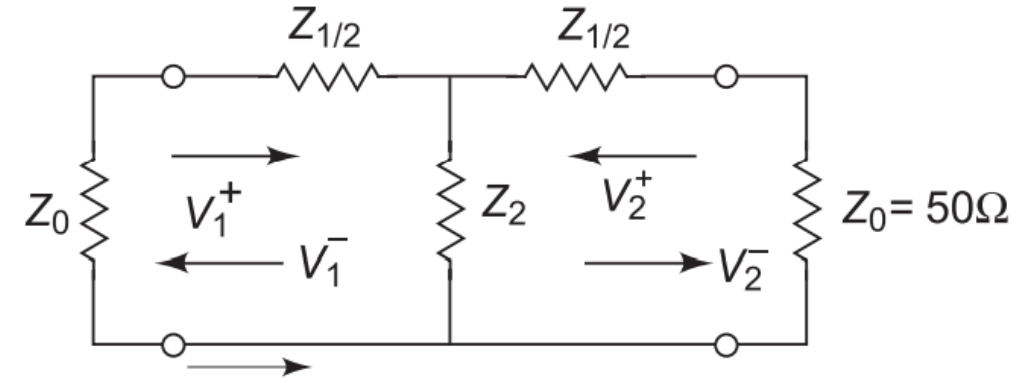
$$S_{11} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0} = \frac{50 - 50}{50 + 50} = 0$$



Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$


$$\bullet \frac{Z_1}{2} = \frac{17.12}{2} = 8.56$$

$$\bullet S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$

$$Z_{in1} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right) = 8.56 + \frac{141.78 \times (8.56 + 50)}{141.78 + (8.85 + 50)} = 50$$

$$S_{11} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0} = \frac{50 - 50}{50 + 50} = 0$$

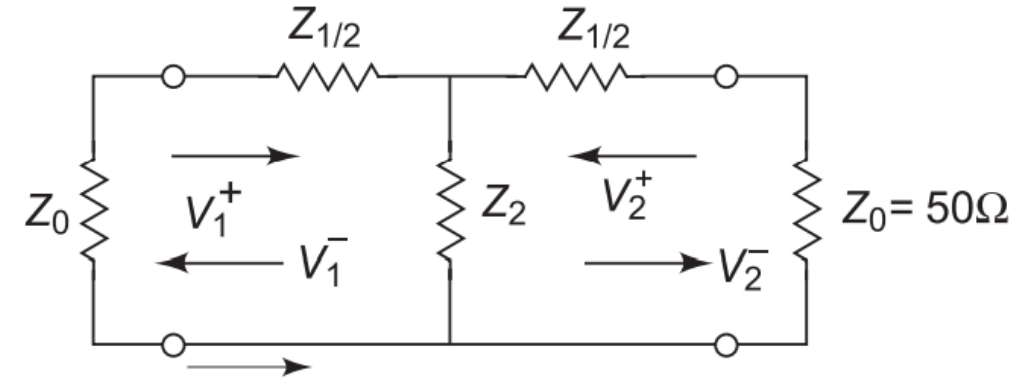For symmetry, matched network, $S_{22} = S_{11} = 0$, $V_1^- = 0$, $V_2^+ = 0$



Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$\bullet \frac{Z_1}{2} = \frac{17.12}{2} = 8.56$$


$$\bullet S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$

$$Z_{in1} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right) = 8.56 + \frac{141.78 \times (8.56 + 50)}{141.78 + (8.56 + 50)} = 50$$

$$S_{11} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0} = \frac{50 - 50}{50 + 50} = 0$$

For symmetry, matched network, $S_{22} = S_{11} = 0$, $V_1^- = 0$, $V_2^+ = 0$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

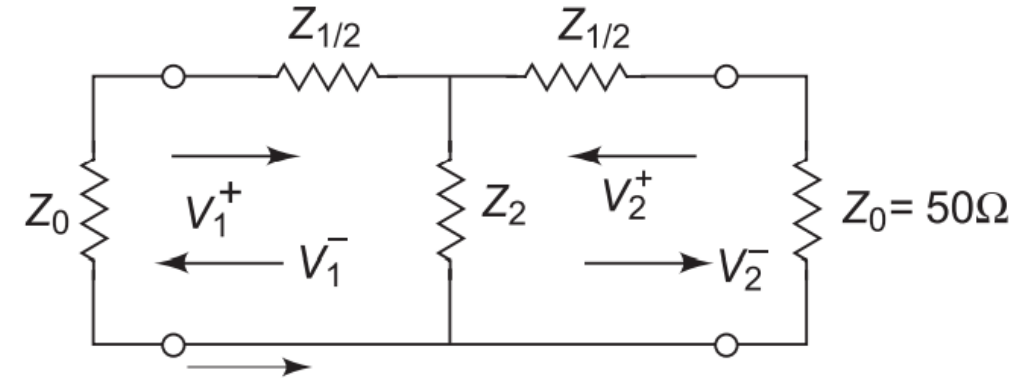

Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$\bullet \frac{Z_1}{2} = \frac{17.12}{2} = 8.56$$

$$\bullet S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{b_1}{a_1} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$


$$Z_{in1} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right) = 8.56 + \frac{141.78 \times (8.56 + 50)}{141.78 + (8.56 + 50)} = 50$$

$$S_{11} = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0} = \frac{50 - 50}{50 + 50} = 0$$

For symmetry, matched network, $S_{22} = S_{11} = 0$, $V_1^- = 0$, $V_2^+ = 0$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$
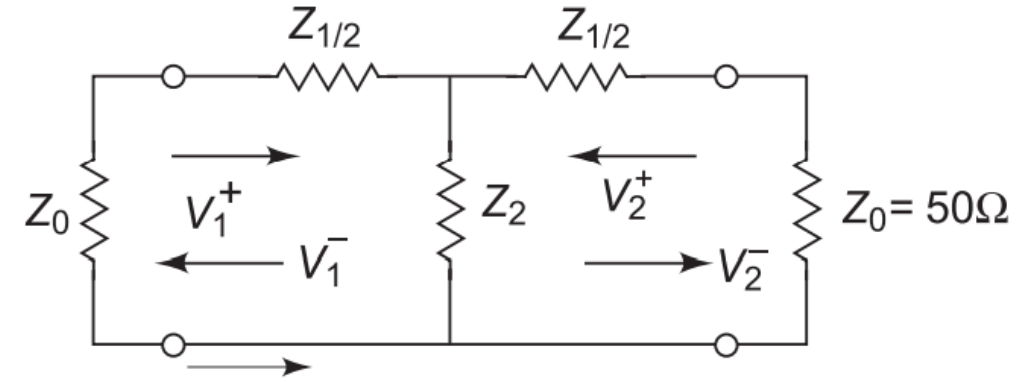
$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and} \quad V_2 = V_2^+ + V_2^- = V_2^-$$




Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

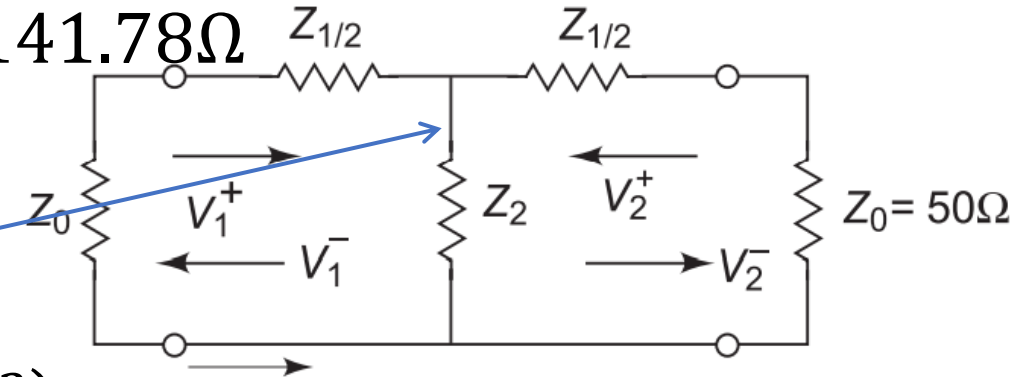Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$




Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$

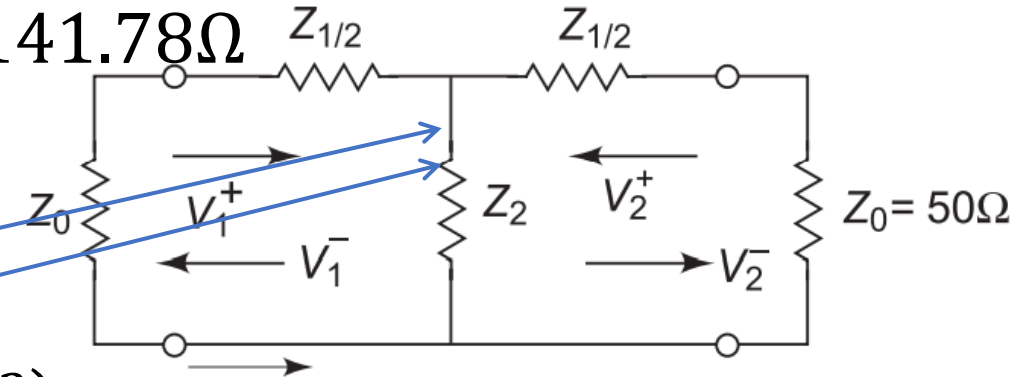Voltage at center: $V_1 \left(\frac{41.44}{41.44 + 8.56} \right)$




Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$

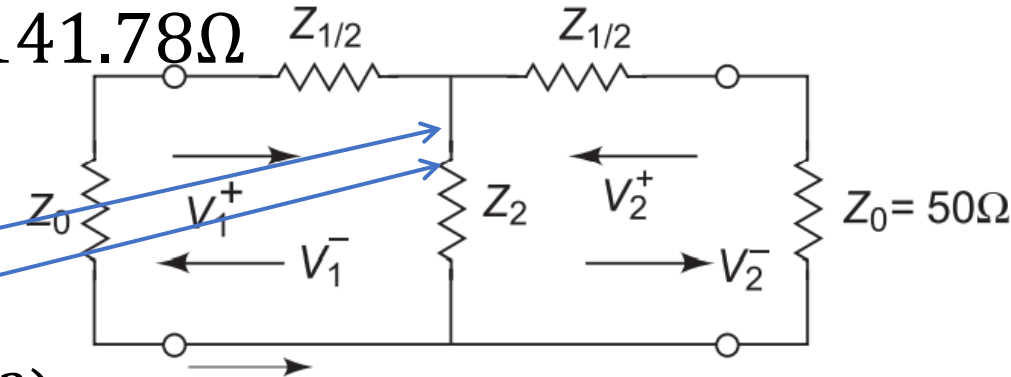
$$\text{Voltage at center: } V_1 \left(\frac{41.44}{41.44 + 8.56} \right)$$



Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

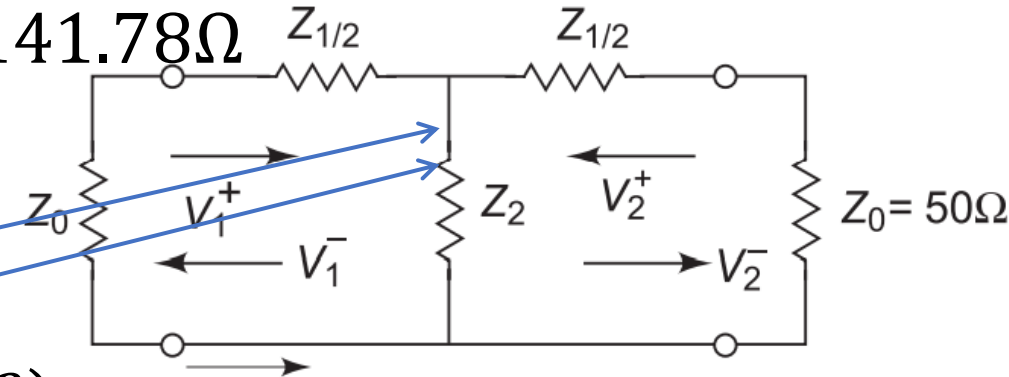

Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$


Voltage at center: $V_1 \left(\frac{41.44}{41.44 + 8.56} \right)$

$$V_2^- = V_2 = V_1 \left(\frac{41.44}{41.44 + 8.56} \right) \left(\frac{50}{50 + 8.56} \right) = 0.707V_1$$

Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

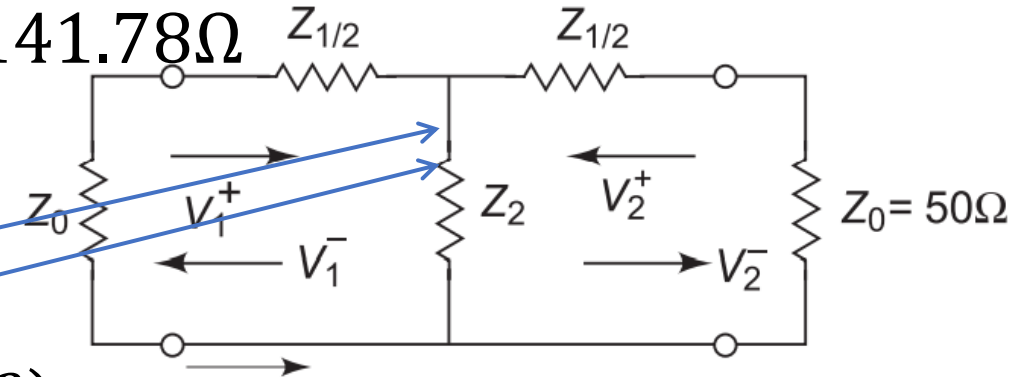

Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$

Voltage at center: $V_1 \left(\frac{41.44}{41.44 + 8.56}\right)$


$$V_2^- = V_2 = V_1 \left(\frac{41.44}{41.44 + 8.56}\right) \left(\frac{50}{50 + 8.56}\right) = 0.707V_1$$

$$S_{21} = \left.\frac{V_2^-}{V_1^+}\right|_{V_2^+ = 0} = 0.707 = S_{12}$$

Determine the S matrix of 3dB T network attenuator terminated in 50Ω matched load with $Z_1 = 17.12\Omega$ and $Z_2 = 141.78\Omega$

$$V_1 = V_1^+ + V_1^- = V_1^+ \quad \text{and}$$

$$V_2 = V_2^+ + V_2^- = V_2^-$$

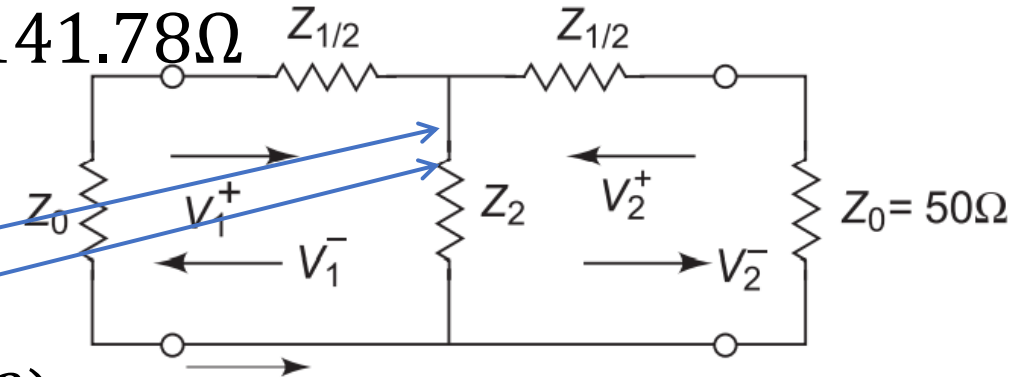

Again, Impedance seen at center = $\left(50 + \frac{17.12}{2}\right) \parallel 141.78 = 41.44$

Voltage at center: $V_1 \left(\frac{41.44}{41.44 + 8.56} \right)$

$$V_2^- = V_2 = V_1 \left(\frac{41.44}{41.44 + 8.56} \right) \left(\frac{50}{50 + 8.56} \right) = 0.707V_1$$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = 0.707 = S_{12}$$

$$[S] = \begin{bmatrix} 0 & 0.707 \\ 0.707 & 0 \end{bmatrix}$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

To check for lossless, $[S^*]^T [S] = [I]$ Unitary property

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

To check for lossless, $[S^*]^T [S] = [I]$ Unitary property

$$[S^*] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

$$[S^*]^T = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \quad (\text{Interchange rows and columns})$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

To check for lossless, $[S^*]^T [S] = [I]$ Unitary property

$$[S^*] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

$$[S^*]^T = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \quad (\text{Interchange rows and columns})$$

$$[S^*]^T [S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

$$=$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

To check for lossless, $[S^*]^T [S] = [I]$ Unitary property

$$[S^*] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

$$[S^*]^T = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \quad (\text{Interchange rows and columns})$$

$$\begin{aligned} [S^*]^T [S] &= \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix} \\ &= \begin{bmatrix} 0.4 + 0.36 & 0.12j - 0.6j \\ -0.12j + 0.6j & 0.1 \end{bmatrix} = \end{aligned}$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

To check for lossless, $[S^*]^T [S] = [I]$ Unitary property

$$[S^*] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

$$[S^*]^T = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \quad (\text{Interchange rows and columns})$$

$$\begin{aligned} [S^*]^T [S] &= \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle -90^\circ \\ 0.6\angle -90^\circ & 0.1\angle 0^\circ \end{bmatrix} \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix} \\ &= \begin{bmatrix} 0.4 + 0.36 & 0.12j - 0.6j \\ -0.12j + 0.6j & 0.1 \end{bmatrix} = \begin{bmatrix} 0.76 & 0.6j \\ -0.6j & 0.1 \end{bmatrix} \neq \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \end{aligned}$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

$$[S^*]^T [S] \neq [I] \quad \textbf{Not lossless}$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

$$[S^*]^T [S] \neq [I] \quad \text{Not lossless}$$

$$\text{Input reflection coefficient } \Gamma_1 = S_{11} + \frac{S_{12}^2 \Gamma_2}{1 - S_{22} \Gamma_2}$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

$$[S^*]^T [S] \neq [I] \quad \text{Not lossless}$$

$$\text{Input reflection coefficient } \Gamma_1 = S_{11} + \frac{S_{12}^2 \Gamma_2}{1 - S_{22} \Gamma_2}$$

Γ_2 for short circuit is -1.

$$\Gamma_1 = S_{11} + \frac{S_{12}^2 (-1)}{1 - S_{22} (-1)} =$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

$$[S^*]^T [S] \neq [I] \quad \text{Not lossless}$$

$$\text{Input reflection coefficient } \Gamma_1 = S_{11} + \frac{S_{12}^2 \Gamma_2}{1 - S_{22} \Gamma_2}$$

Γ_2 for short circuit is -1.

$$\Gamma_1 = S_{11} + \frac{S_{12}^2 (-1)}{1 - S_{22} (-1)} = 0.2 + \frac{(0.6j)^2 (-1)}{1 - 0.1(-1)} = 0.2 + \frac{0.36}{1.1} = 0.5273$$

2. S matrix of a two port network is

$$[S] = \begin{bmatrix} 0.2\angle 0^\circ & 0.6\angle 90^\circ \\ 0.6\angle 90^\circ & 0.1\angle 0^\circ \end{bmatrix}$$

Prove that network is reciprocal but not lossless.

Find return loss at port 1 when port 2 is short circuited.

a) $[S]$ is symmetric and hence network is reciprocal.

$$[S^*]^T [S] \neq [I] \quad \text{Not lossless}$$

$$\text{Input reflection coefficient } \Gamma_1 = S_{11} + \frac{S_{12}^2 \Gamma_2}{1 - S_{22} \Gamma_2}$$

Γ_2 for short circuit is -1.

$$\Gamma_1 = S_{11} + \frac{S_{12}^2 (-1)}{1 - S_{22} (-1)} = 0.2 + \frac{(0.6j)^2 (-1)}{1 - 0.1(-1)} = 0.2 + \frac{0.36}{1.1} = 0.5273$$

$$\text{Return loss} = -20 \log_{10} |\Gamma_1| = -20 \log_{10} (0.5273) = 5.56 \text{ dB}$$

1. A four port network has the scattering matrix shown below.
- a) Is the network lossless?
 - b) Is the network reciprocal?
 - c) Find return loss at port 1 when all other ports are terminated with matched loads.
 - d) Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
 - e) Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
 - f) Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

1. A four port network has the scattering matrix shown below.

- Is the network lossless?
- Is the network reciprocal?
- Find return loss at port 1 when all other ports are terminated with matched loads.
- Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
- Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
- Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

a) For Lossless

$[S]$ must be unitary

First row

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2$$

$$= 0.178^2 + 0.6^2 + 0.4^2 + 0$$

$$= 0.552 \neq 1$$

The network is not lossless

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

1. A four port network has the scattering matrix shown below.

- a) Is the network lossless?
- b) Is the network reciprocal?
- c) Find return loss at port 1 when all other ports are terminated with matched loads.
- d) Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
- e) Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
- f) Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

b) For Reciprocal

$[S]$ must be Symmetric

Given matrix is symmetric and hence it is reciprocal

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

1. A four port network has the scattering matrix shown below.

- a) Is the network lossless?
- b) Is the network reciprocal?
- c) Find return loss at port 1 when all other ports are terminated with matched loads.
- d) Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
- e) Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
- f) Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

c) When ports 2,3,4 are matched, $\Gamma = S_{11}$

$$\begin{aligned}\text{Return loss} &= -20 \log_{10} |\Gamma| \\ &= -20 \log_{10} |0.178| \\ &= 15 \text{ dB}\end{aligned}$$

$$[S] = \begin{bmatrix} 0.178 \angle 90^\circ & 0.6 \angle 45^\circ & 0.4 \angle 45^\circ & 0 \\ 0.6 \angle 45^\circ & 0 & 0 & 0.3 \angle -45^\circ \\ 0.4 \angle 45^\circ & 0 & 0 & 0.5 \angle -45^\circ \\ 0 & 0.3 \angle -45^\circ & 0.5 \angle -45^\circ & 0 \end{bmatrix}$$

1. A four port network has the scattering matrix shown below:

- Is the network lossless?
- Is the network reciprocal?
- Find return loss at port 1 when all other ports are terminated with matched loads.
- Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
- Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
- Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

d) When ports 1 and 3 are matched with Z_0 , $V_1^+ = 0$
 $V_3^+ = 0$. $V_4^- = S_{42}V_2^+$

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

$$\begin{aligned} \text{Insertion loss } IL &= -20 \log_{10} |S_{42}| \\ &= -20 \log_{10} |0.3| \\ &= 10.45 \text{ dB} \end{aligned}$$

e) Phase delay = $+45^\circ$

1. A four port network has the scattering matrix shown below.

- Is the network lossless?
- Is the network reciprocal?
- Find return loss at port 1 when all other ports are terminated with matched loads.
- Find insertion loss between Ports 2 and 4 when all other ports are terminated with matched load.
- Find phase delay between Ports 2 and 4 when all other ports are terminated with matched load.
- Find reflection coefficient seen at port 1 if a short circuit is placed at terminal plane of port 3 and all other ports are terminated with matched load.

f) Ports 2 and 4 are matched

$$V_2^+ = V_4^+ = 0$$

$$\text{Short at port 3: } V_3^+ = -V_3^-$$

$$V_1^- = S_{11}V_1^+ + S_{13}V_3^+$$

$$= S_{11}V_1^+ - S_{13}V_3^-$$

$$V_3^- = S_{31}V_1^+$$

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

$$\begin{aligned} \Gamma^{(1)} &= \frac{V_1^-}{V_1^+} = S_{11} - S_{13}S_{31} = 0.178j - (0.4\angle 45^\circ)(0.4\angle 45^\circ) \\ &= 0.018\angle 90^\circ \end{aligned}$$