

6.2 Wilkinson Power divider

Module:6 Microwave Passive circuits
Course: BECE305L – Antenna and Microwave Engineering

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: richards.stanislaus@vit.ac.in



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI

Module:6 Microwave Passive circuits 7 hours

- T junction and resistive power divider, Wilkinson power divider, branch line coupler (equal & unequal), Rat Race Coupler, Filter design: Low pass filter (Butterworth and Chebyshev) - Richards transformation and stepped impedance methods.
- .
- Source of the contents: Pozar

6.4 Need for Wilkinson Power divider

- Lossless T junction divider : Not matched at all ports
No isolation between output ports

6.4 Need for Wilkinson Power divider

- Lossless T junction divider : Not matched at all ports
No isolation between output ports
- Resistive divider: Matched at all ports
Not lossless
Isolation is not achieved

6.4 Need for Wilkinson Power divider


- Lossless T junction divider : Not matched at all ports
No isolation between output ports
- Resistive divider: Matched at all ports
Not lossless
Isolation is not achieved
- Wilkinson power divider:
 - Lossy three port network
 - Lossless when output ports are matched
 - Reflected power from output ports is dissipated.
 -
 -
 -

6.4 Need for Wilkinson Power divider

- Lossless T junction divider : Not matched at all ports
No isolation between output ports
- Resistive divider: Matched at all ports
Not lossless
Isolation is not achieved
- Wilkinson power divider:
 - Lossy three port network
 - Lossless when output ports are matched
 - Reflected power from output ports is dissipated.
 - All ports matched
 - Isolation between output ports
 - Arbitrary power division is possible

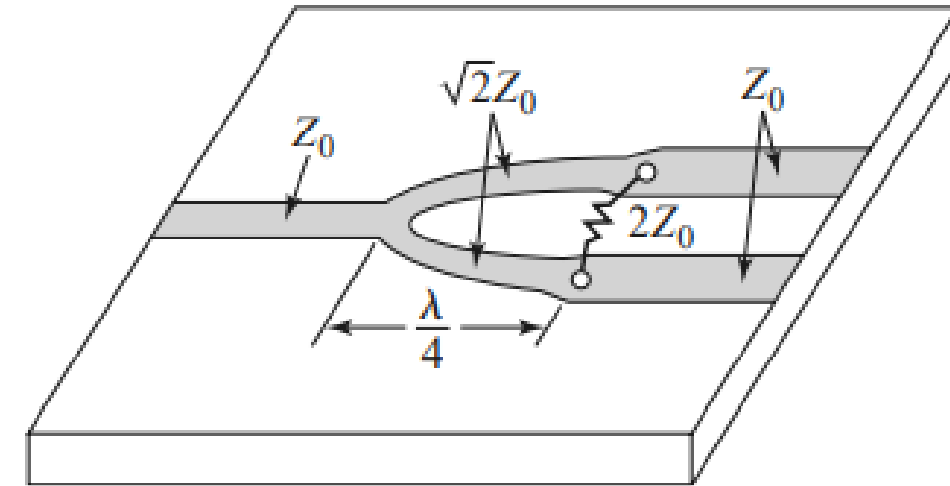6.4 Need for Wilkinson Power divider


- Wilkinson power divider: (Initially 3dB case – equal split)
Microstrip transmission line/stripline



6.4 Need for Wilkinson Power divider



- Wilkinson power divider: (Initially 3dB case – equal split)
Microstrip transmission line/stripline

Transmission line equivalent circuit:

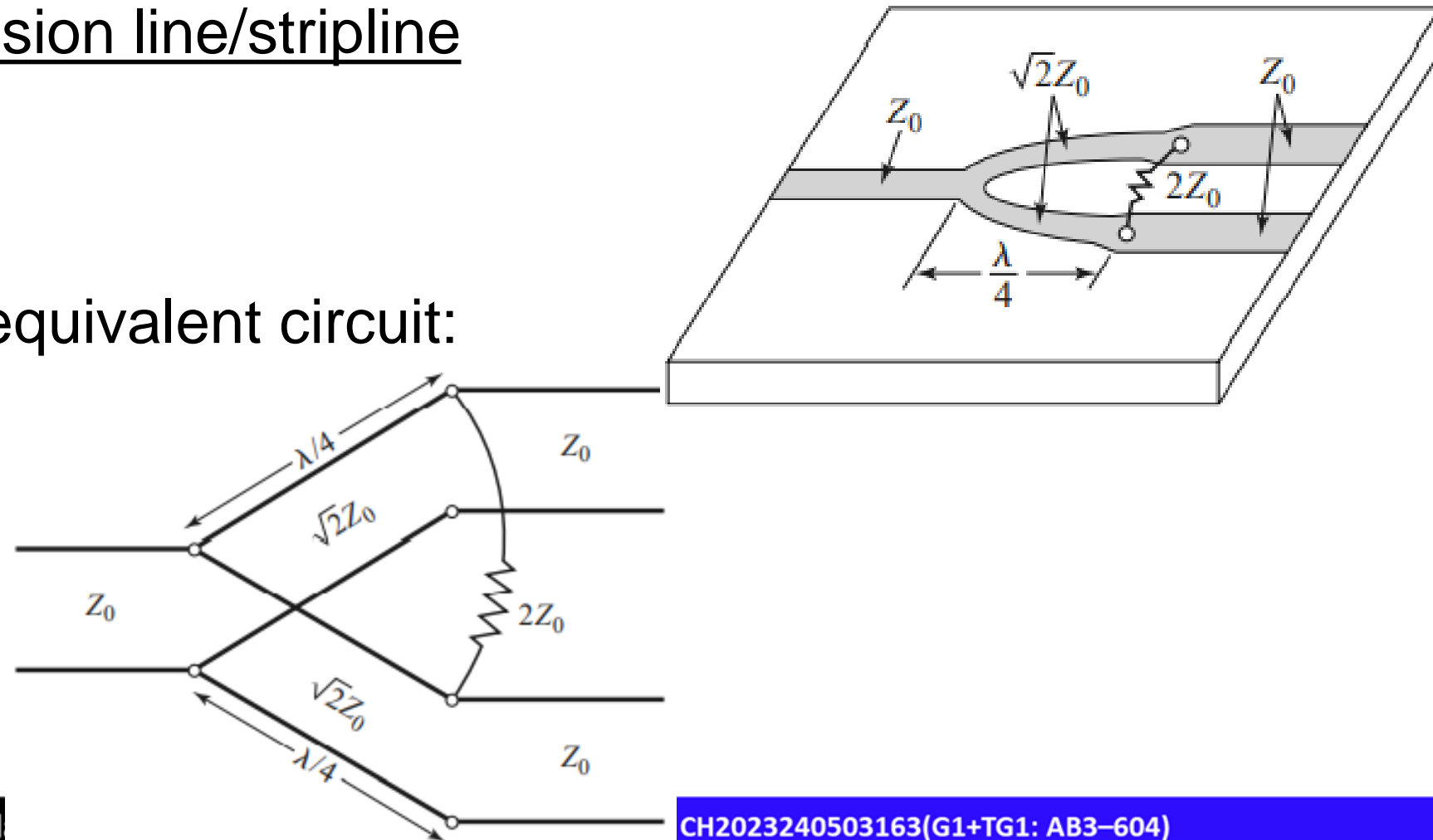

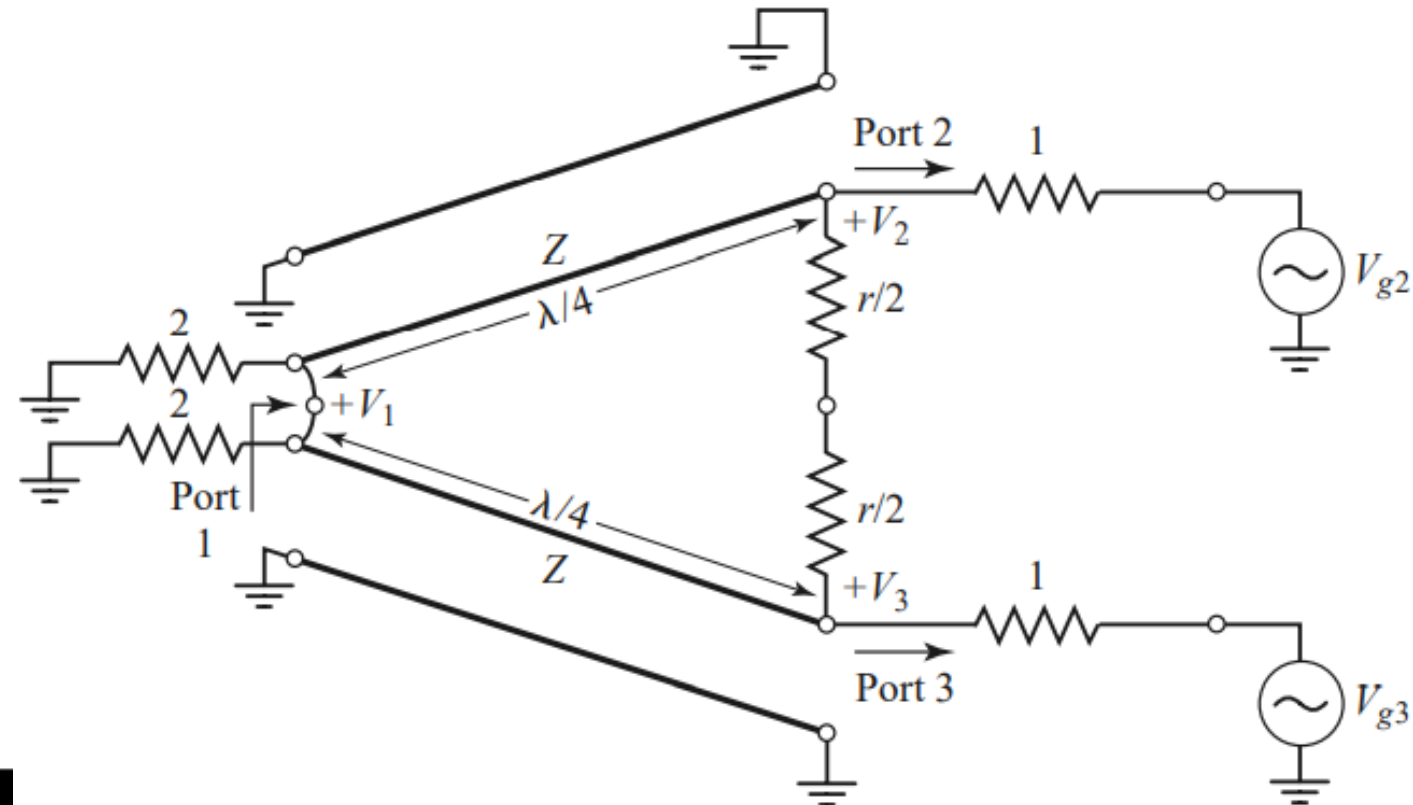
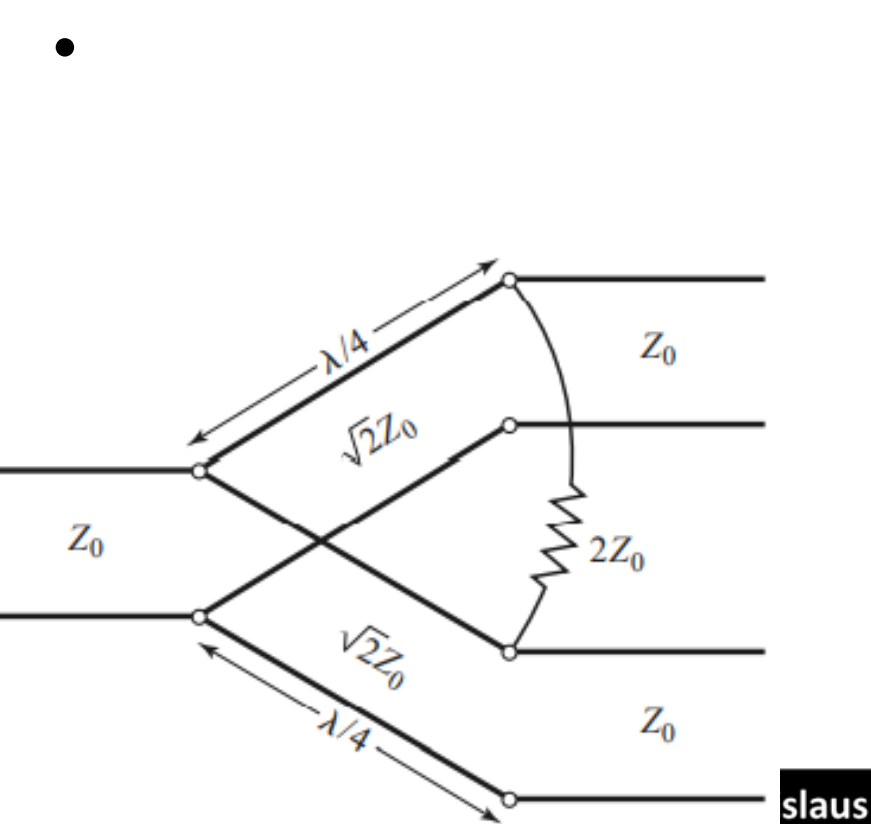
6.4a Construction of Wilkinson Power divider

- (Initially 3dB case – equal split) **Symmetric across the midplane**
Two source resistors of $2Z_0$ combine in parallel to give resistor value:
 $1Z_0$
Quarter wave lines have normalized characteristic impedance Z .



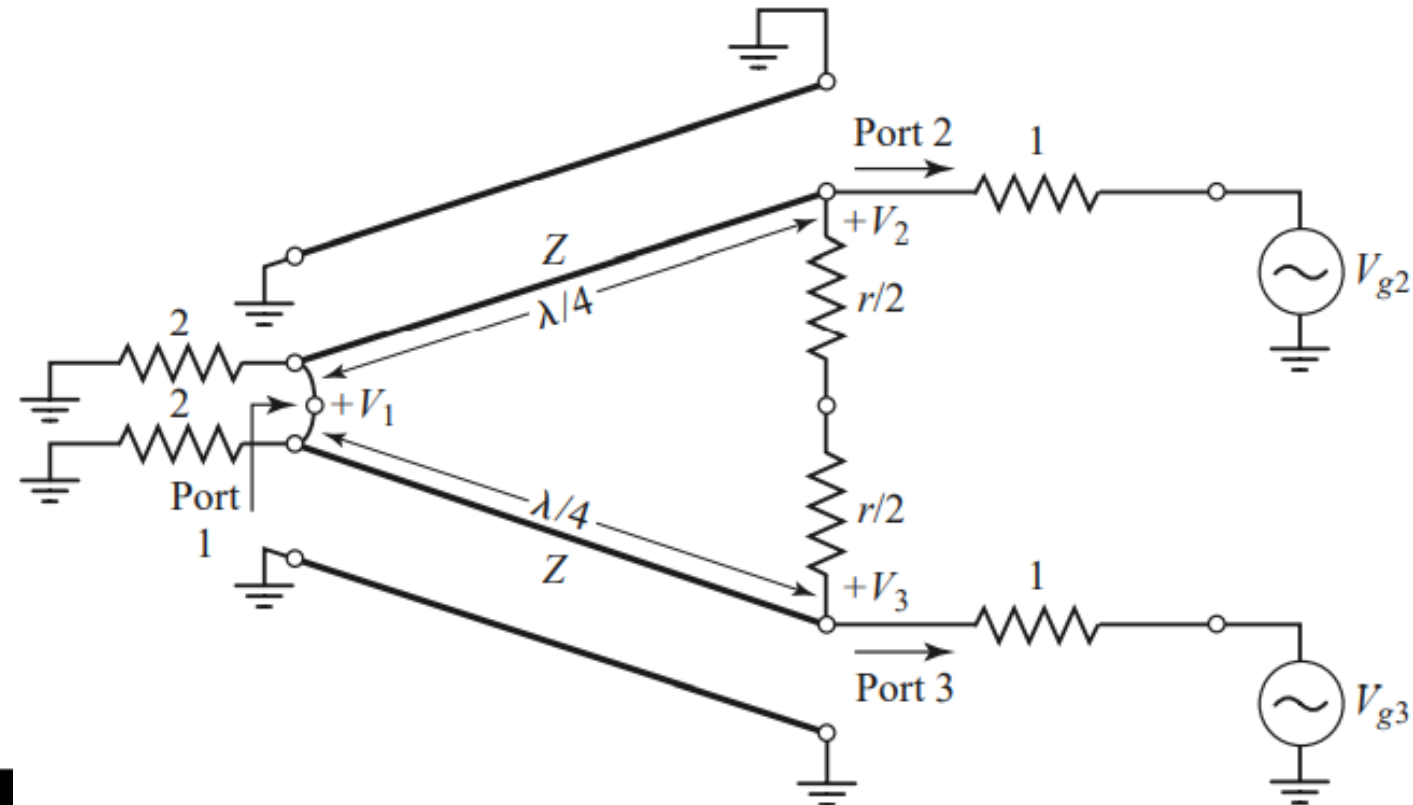
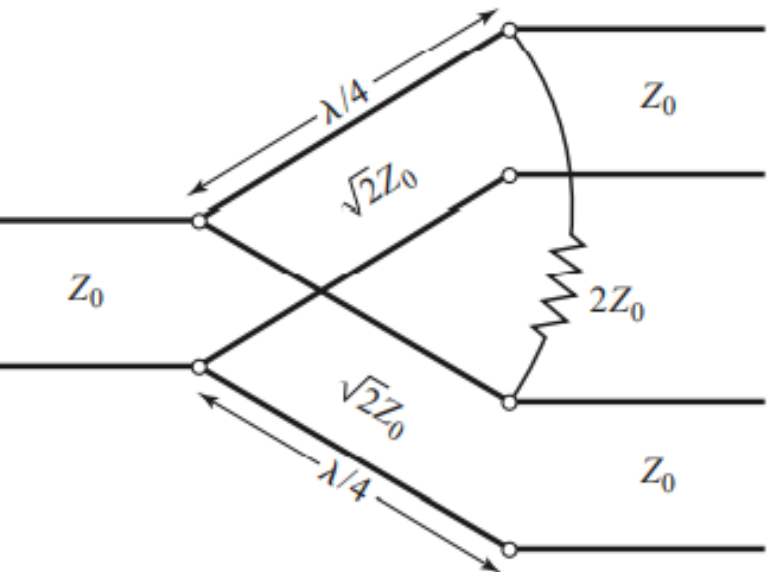
6.4a Construction of Wilkinson Power divider

- (Initially 3dB case – equal split) Symmetric across the midplane
Two source resistors of $2Z_0$ combine in parallel to give resistor value: $1Z_0$
Quarter wave lines have normalized characteristic impedance Z .
- **Shunt resistor has normalized value of r .**



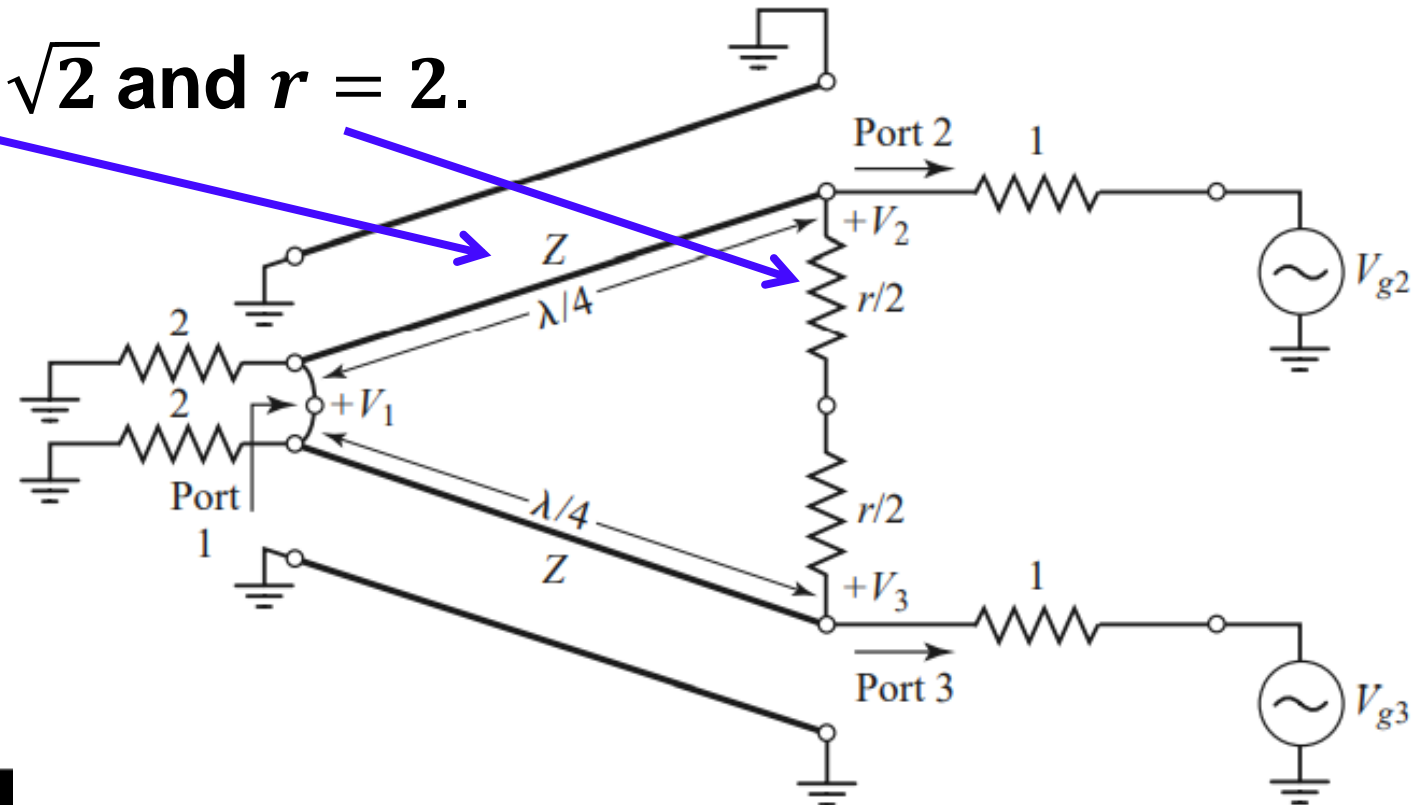
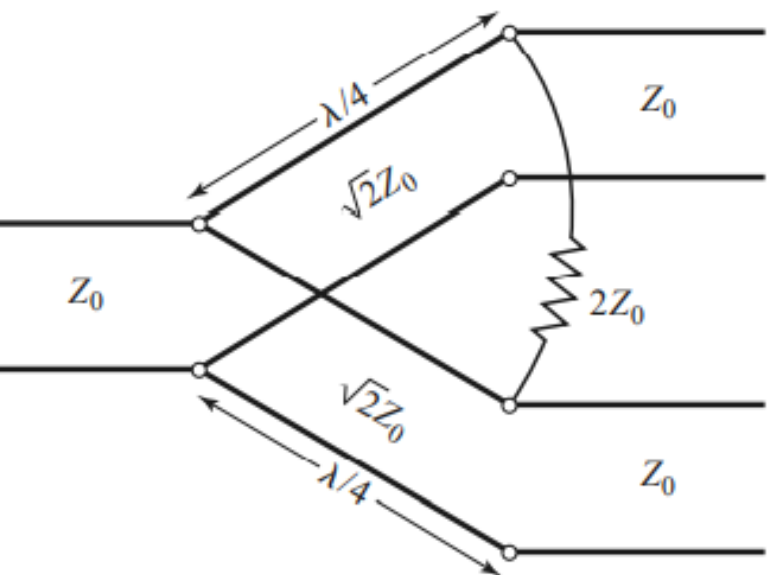
6.4a Construction of Wilkinson Power divider

- (Initially 3dB case – equal split) Symmetric across the midplane
Two source resistors of $2Z_0$ combine in parallel to give resistor value: $1Z_0$
Quarter wave lines have normalized characteristic impedance Z .
- Shunt resistor has normalized value of r .
- For equal power divider, $Z = \sqrt{2}$ and $r = 2$.



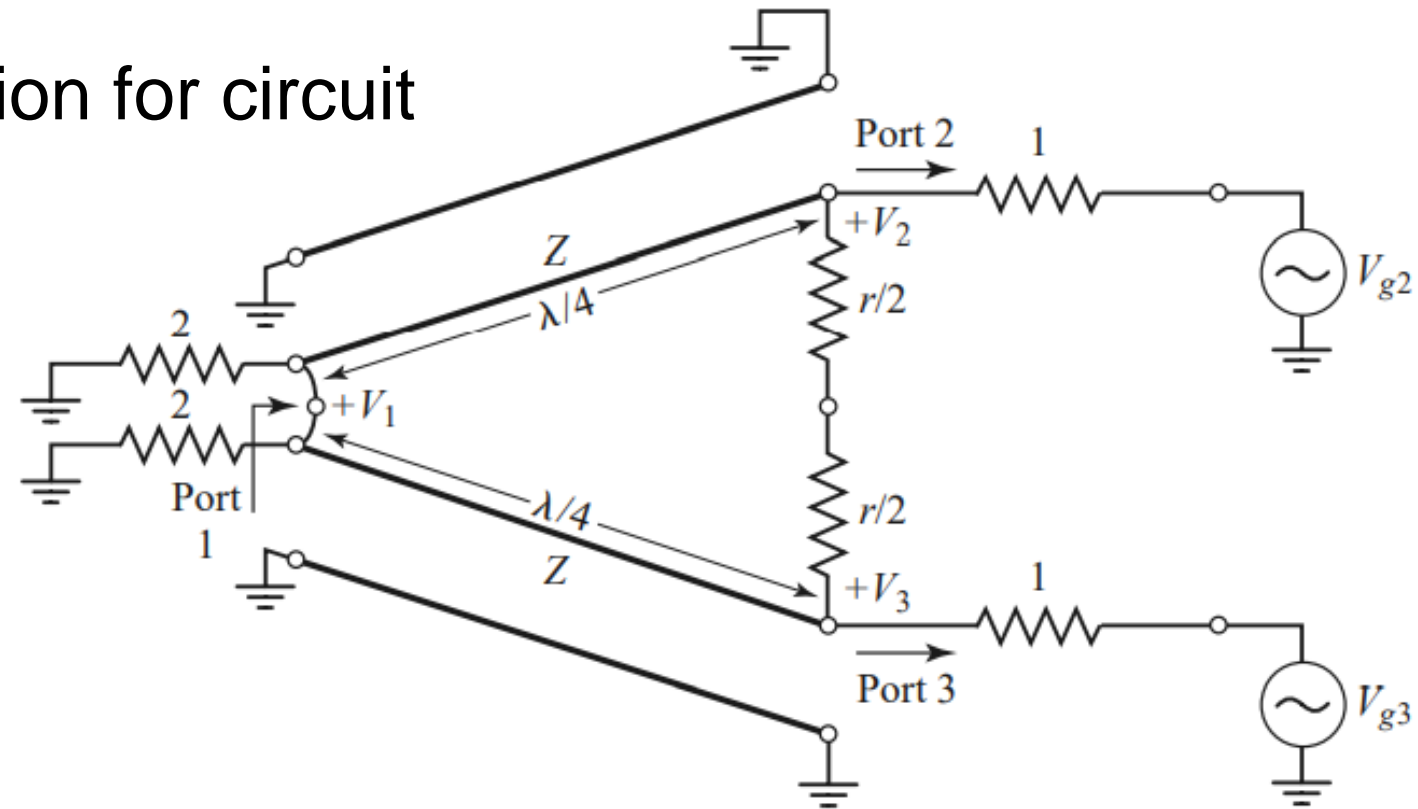
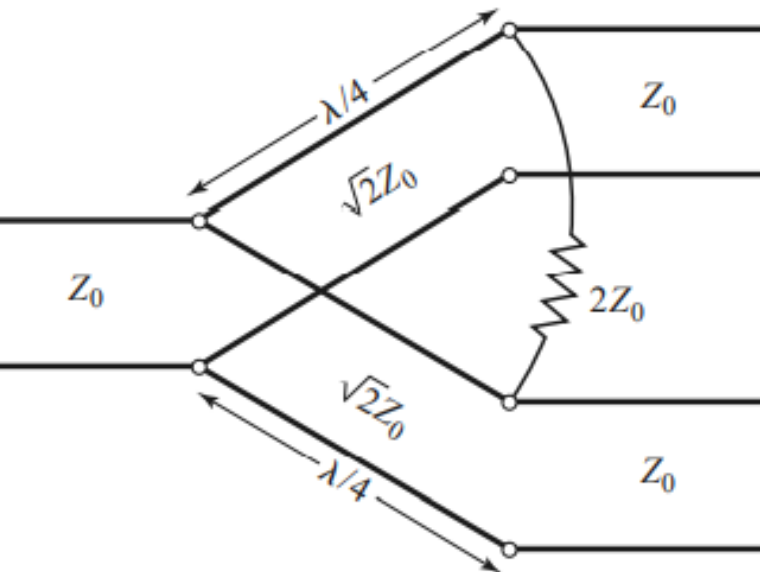
6.4b Modes of operation in Wilkinson Power divider

- Two separate modes of excitation for circuit
- Even mode: $V_{g2} = V_{g3} = 2V_0$
-



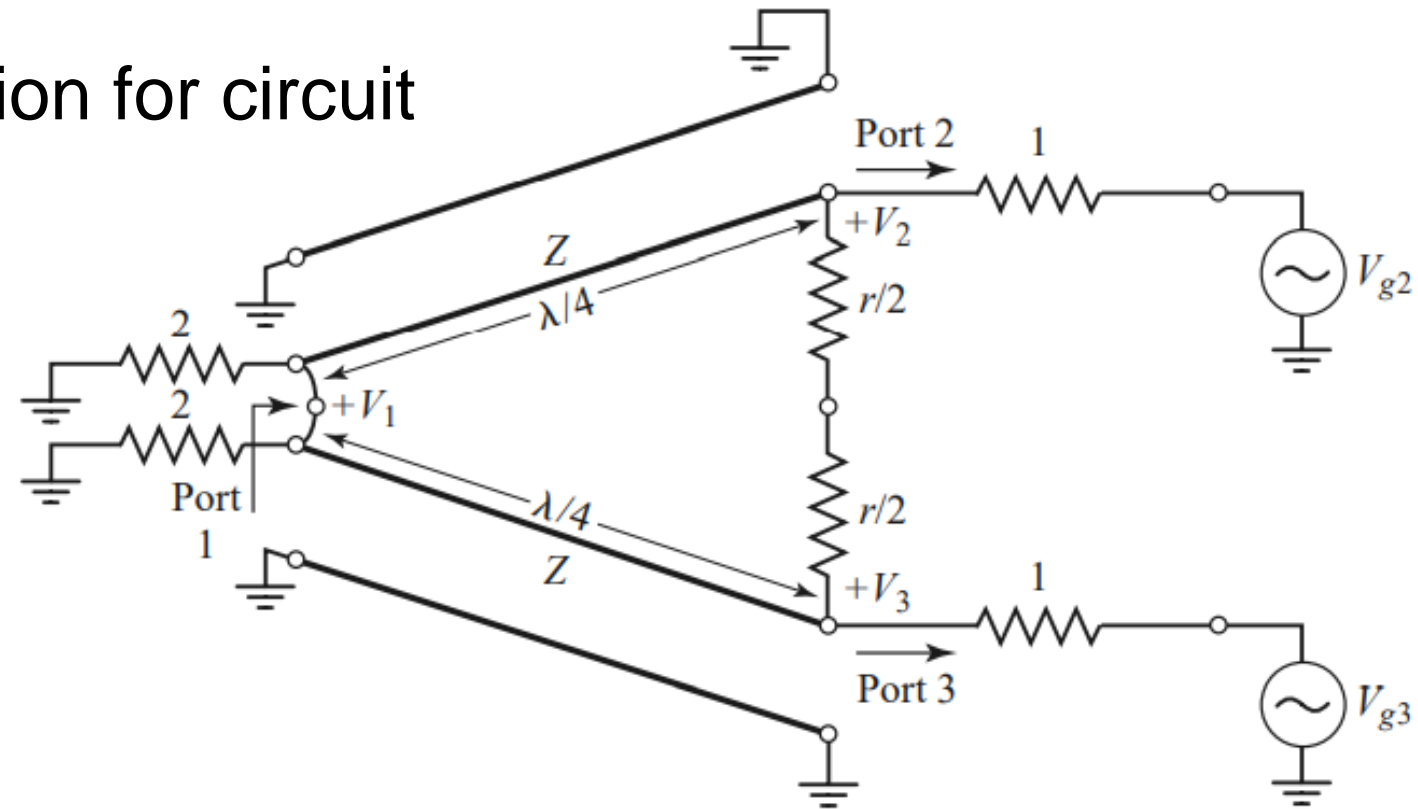
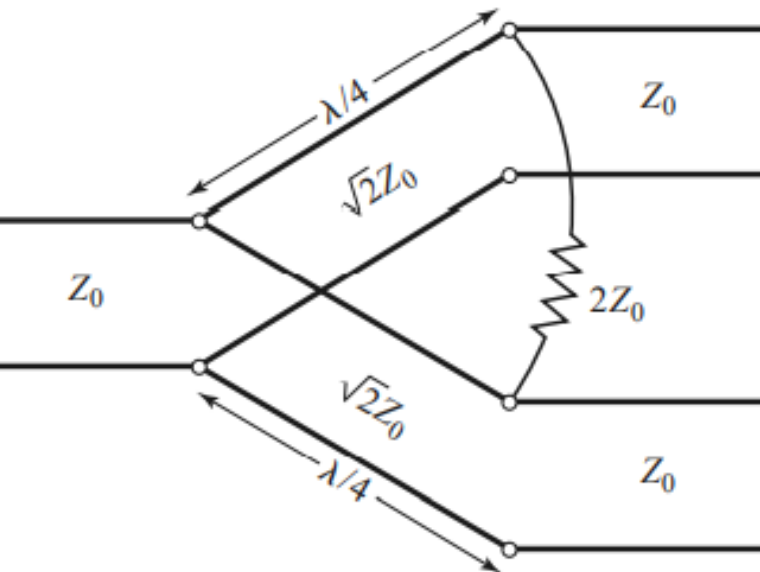
6.4b Modes of operation in Wilkinson Power divider

- Two separate modes of excitation for circuit
- Even mode: $V_{g2} = V_{g3} = 2V_0$
- Odd mode: $V_{g2} = -V_{g3} = 2V_0$
-



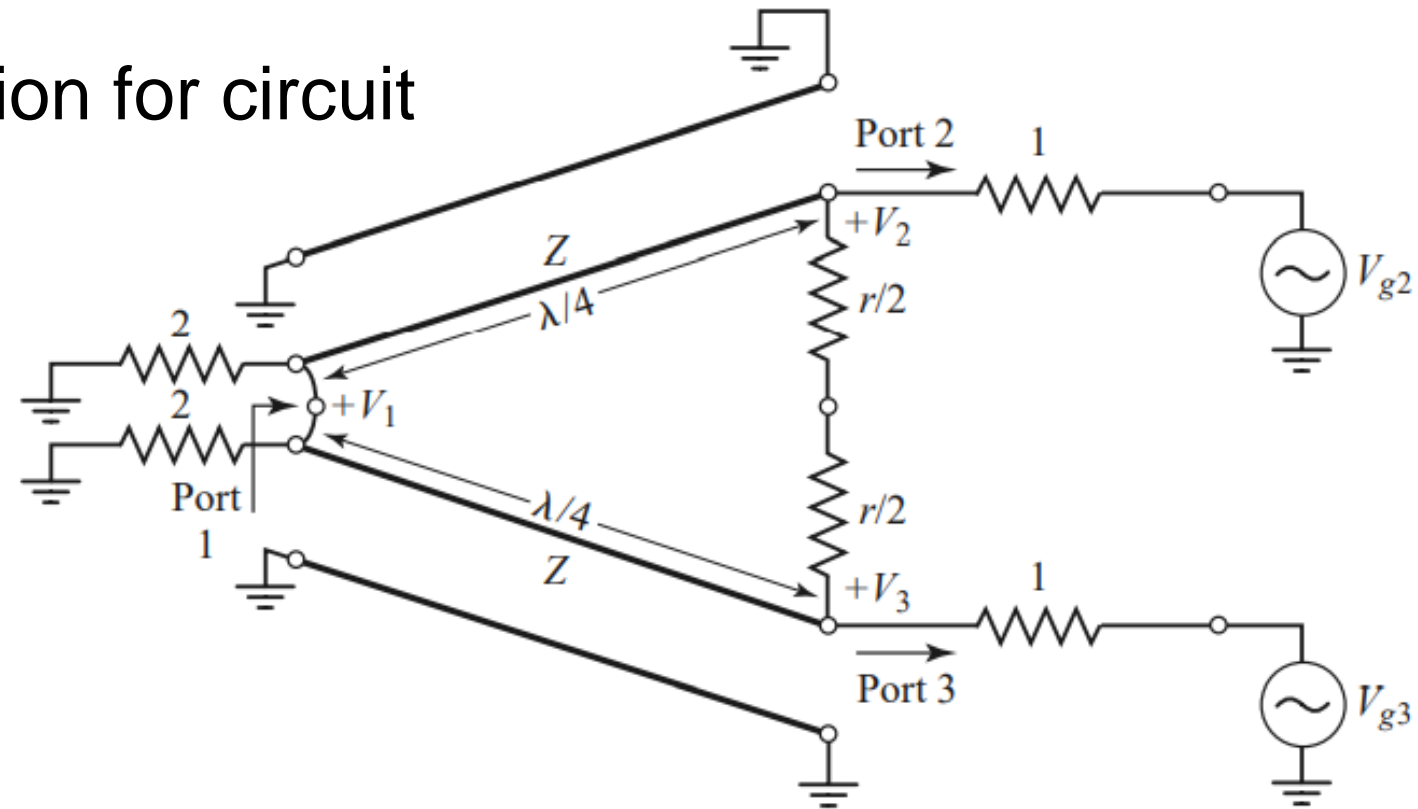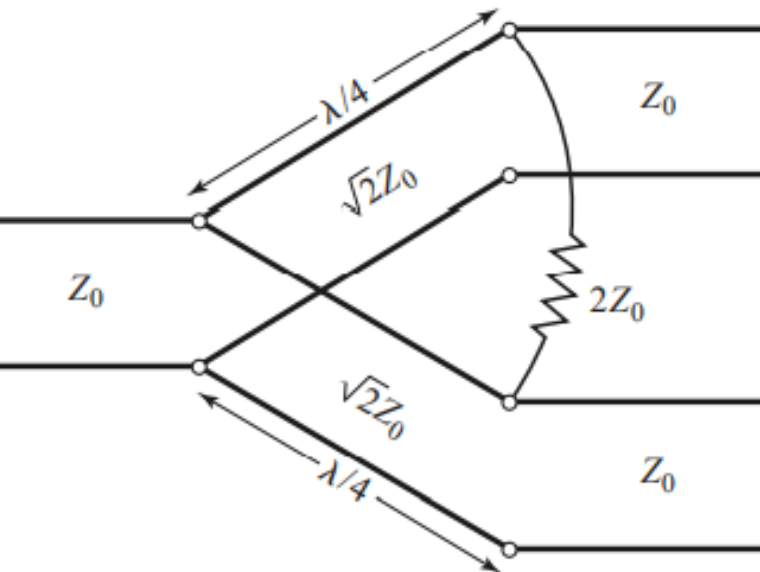
6.4b Modes of operation in Wilkinson Power divider

- Two separate modes of excitation for circuit
- **Even mode:** $V_{g2} = V_{g3} = 2V_0$
- **Odd mode:** $V_{g2} = -V_{g3} = 2V_0$
- **Superposition:** $V_{g2} = 4V_0$
 $V_{g3} = 0$



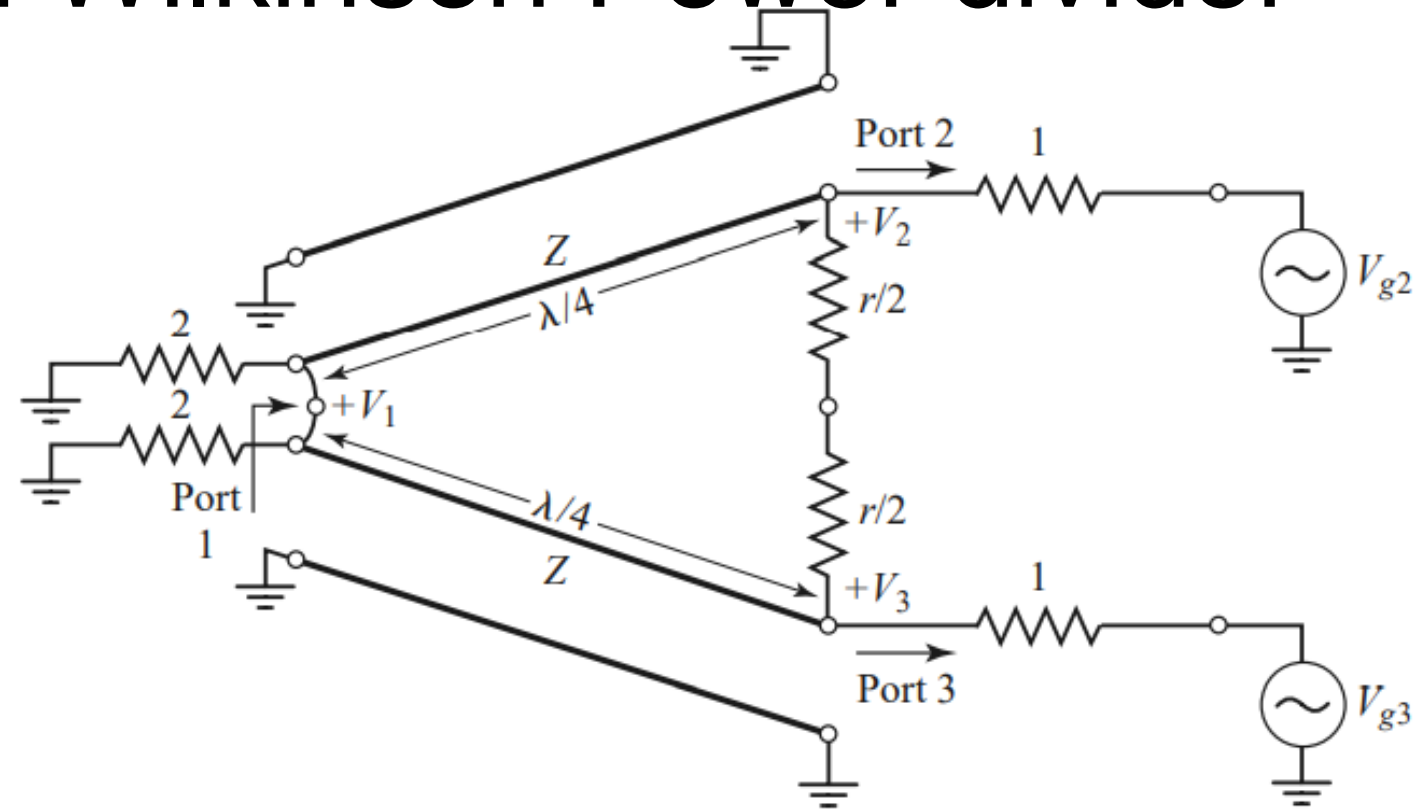
6.4c **Even mode** in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$
- Port 2: $V_2^e = V_3^e$: Port 3
- .




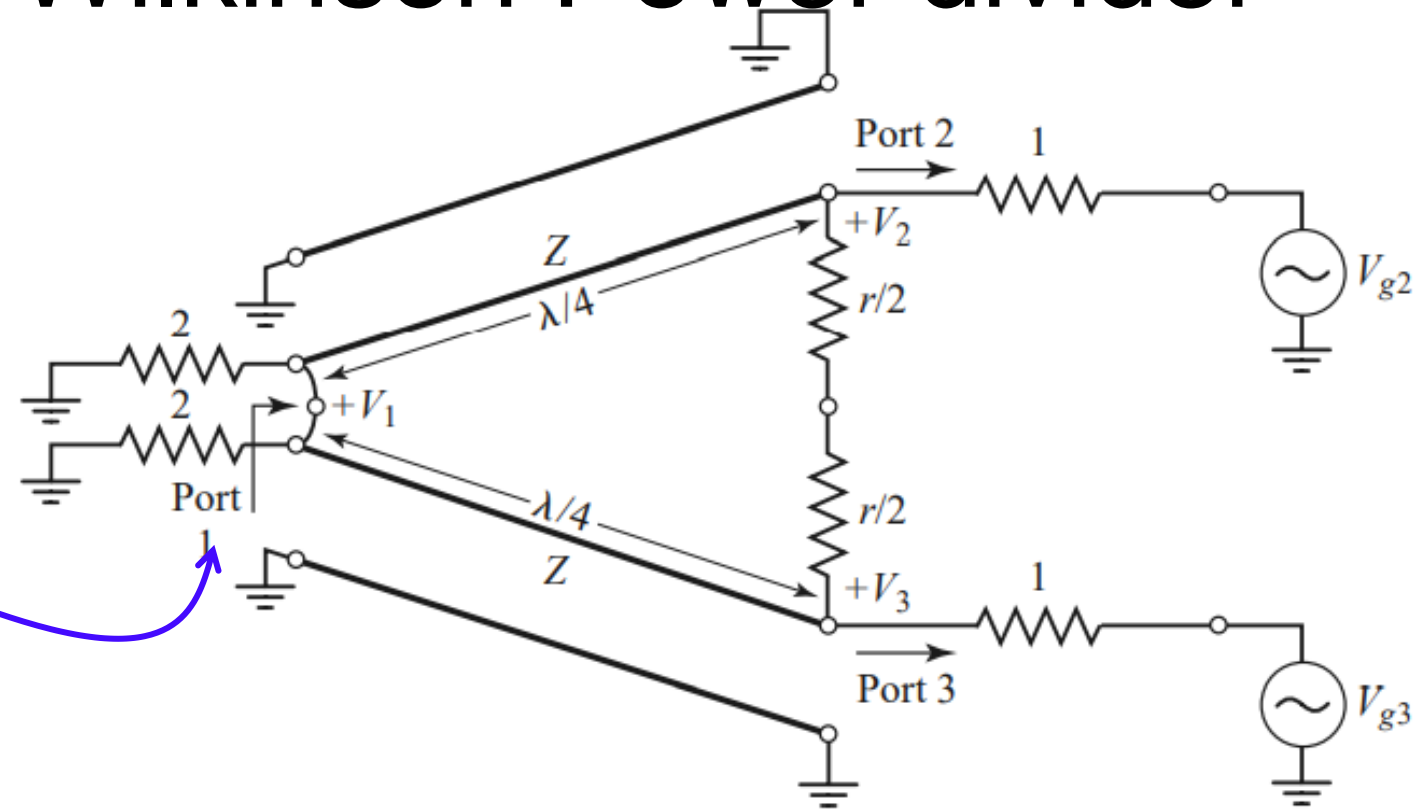
6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$
- Port 2: $V_2^e = V_3^e$: Port 3
- **Voltage at port 1 is zero**
as voltage will be equal
after $\lambda/4$ long transmission line.
- (No current in circuit)



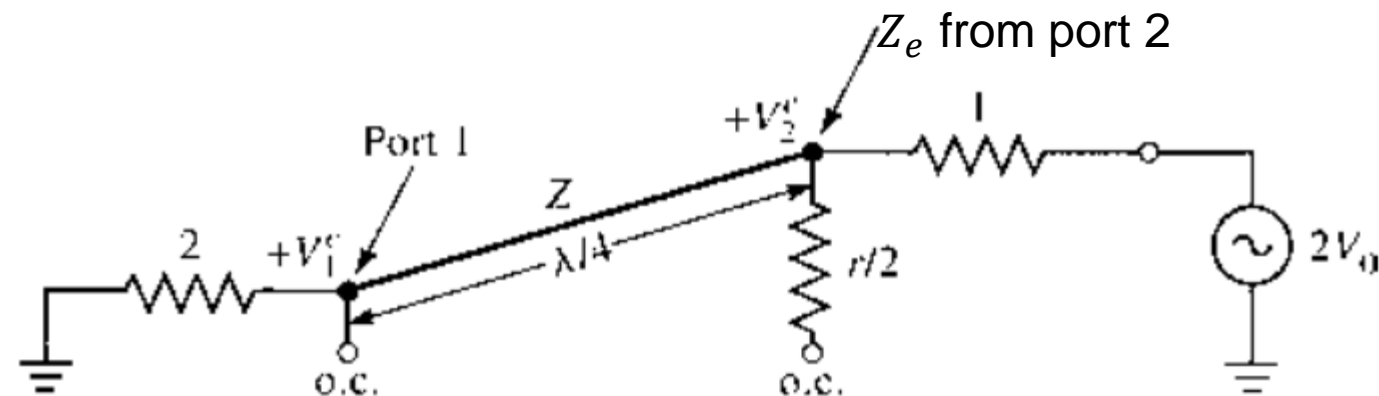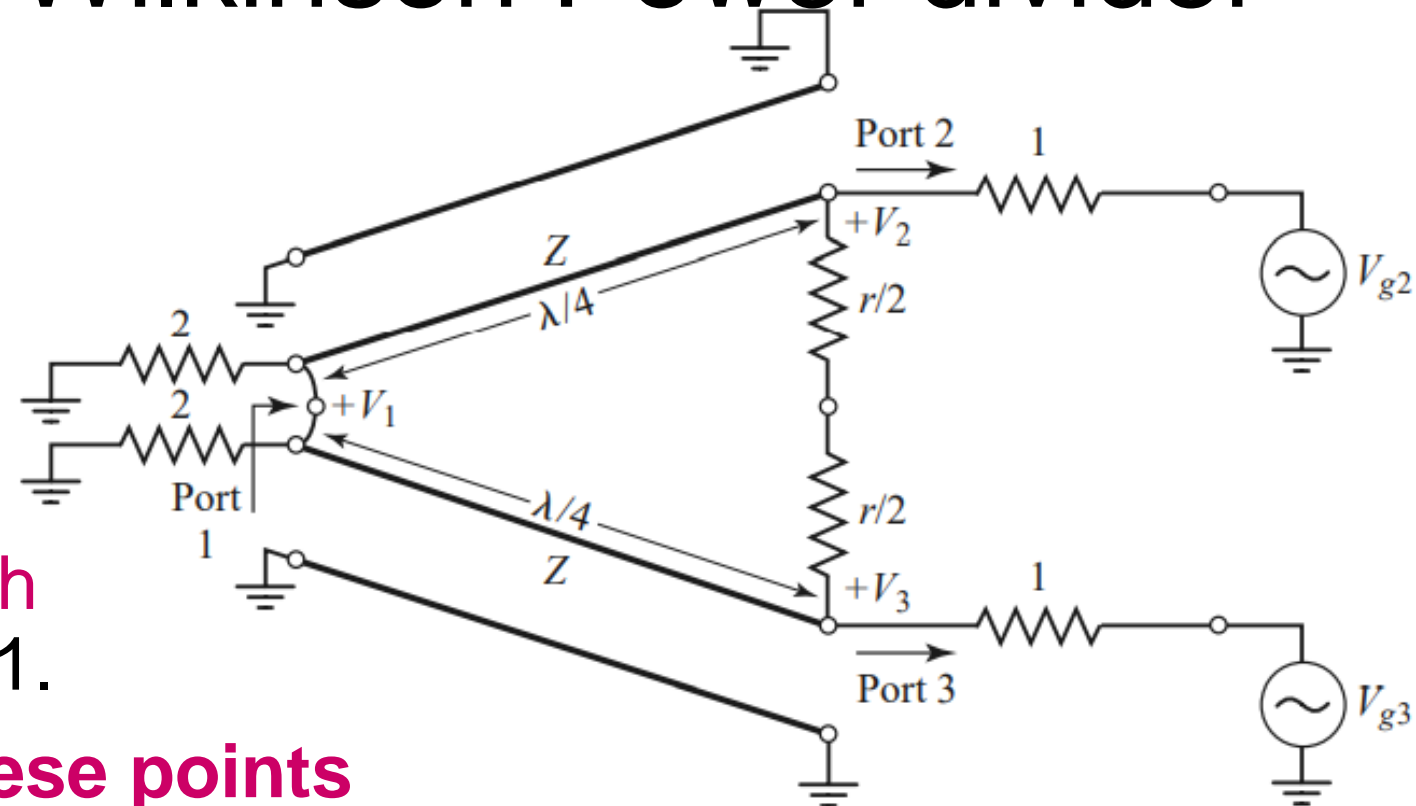6.4c Even mode in Wilkinson Power divider



- Even mode: $V_{g2} = V_{g3} = 2V_0$
- Port 2: $V_2^e = V_3^e$: Port 3
- Voltage at port 1 is zero as voltage will be equal after $\lambda/4$ long transmission line.
- Hence, **no current flows through resistor r** and the short at port 1.
- Equivalent: **Open circuit at these points**



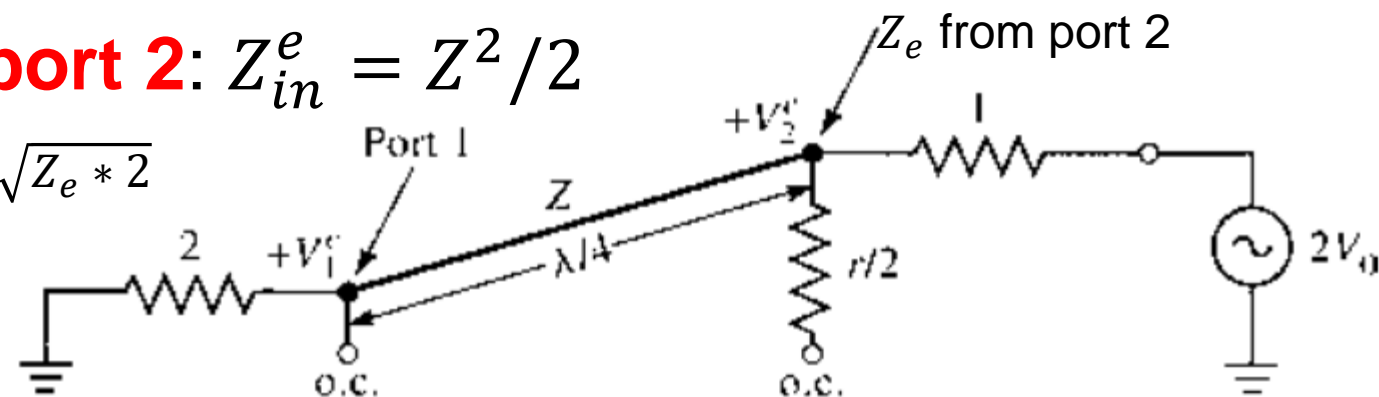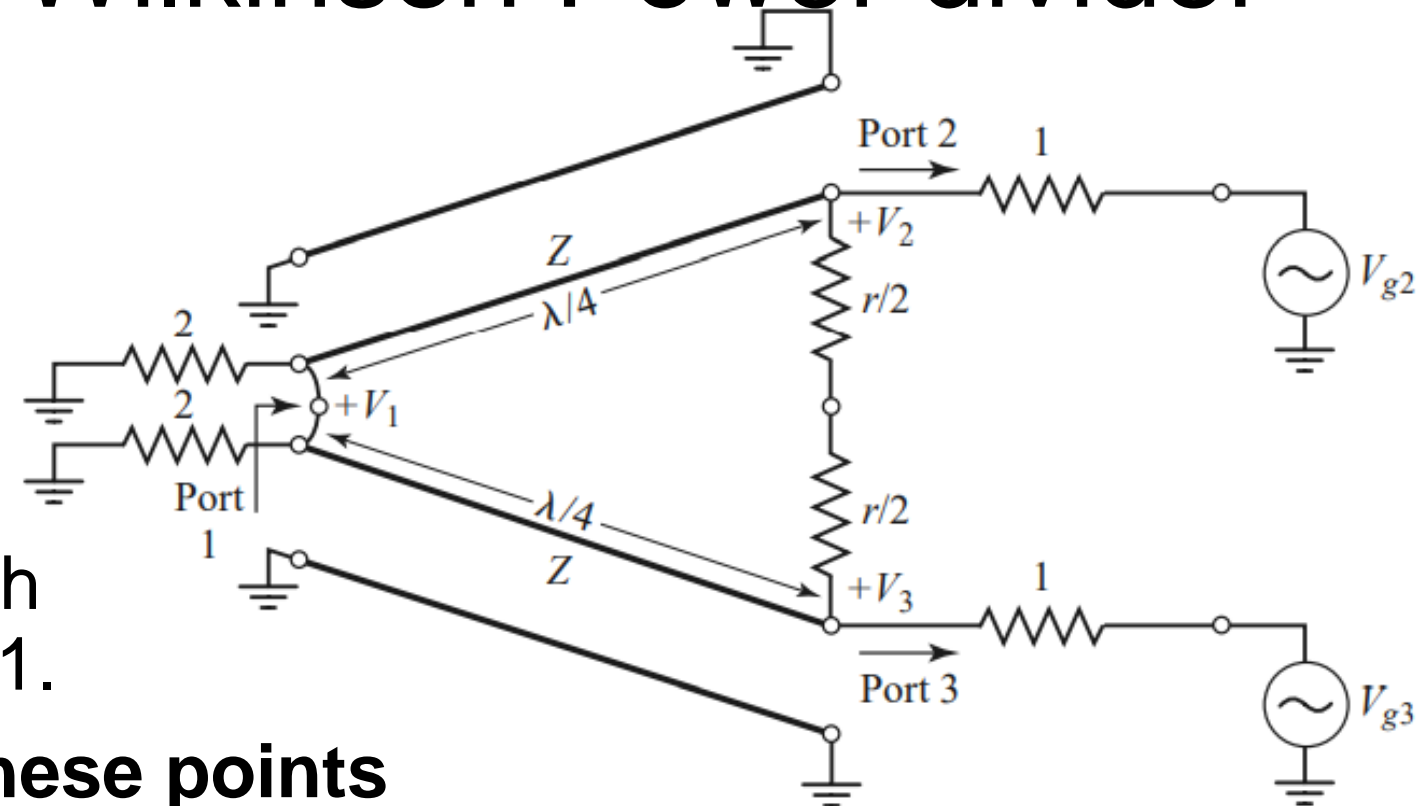6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$
- Port 2: $V_2^e = V_3^e$: Port 3
- Voltage at port 1 is zero as voltage will be equal after $\lambda/4$ long transmission line.
- Hence, no current flows through resistor r and the short at port 1.
- **Equivalent: Open circuit at these points**
- **Impedance Z_e from port 2:** $Z_{in}^e = Z^2/2$


Quarter wave transformer $Z = \sqrt{Z_e * 2}$



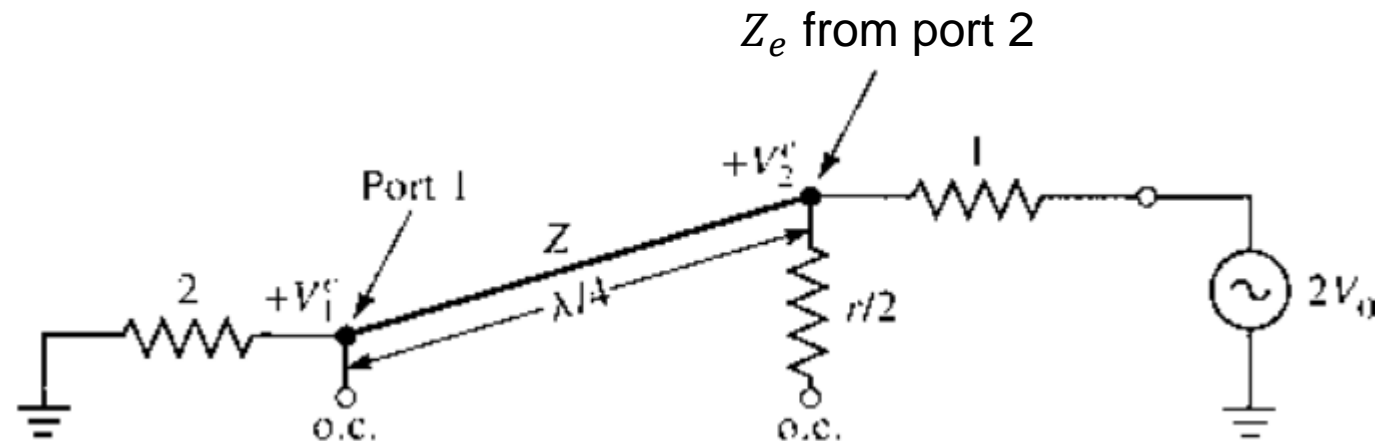6.4c Even mode in Wilkinson Power divider


- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ $[Z_{in}^e = Z \frac{2 + jZ \tan \frac{\beta\lambda}{4}}{Z + j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}]$

Quarter wave transformer $Z = \sqrt{Z_e * 2}$



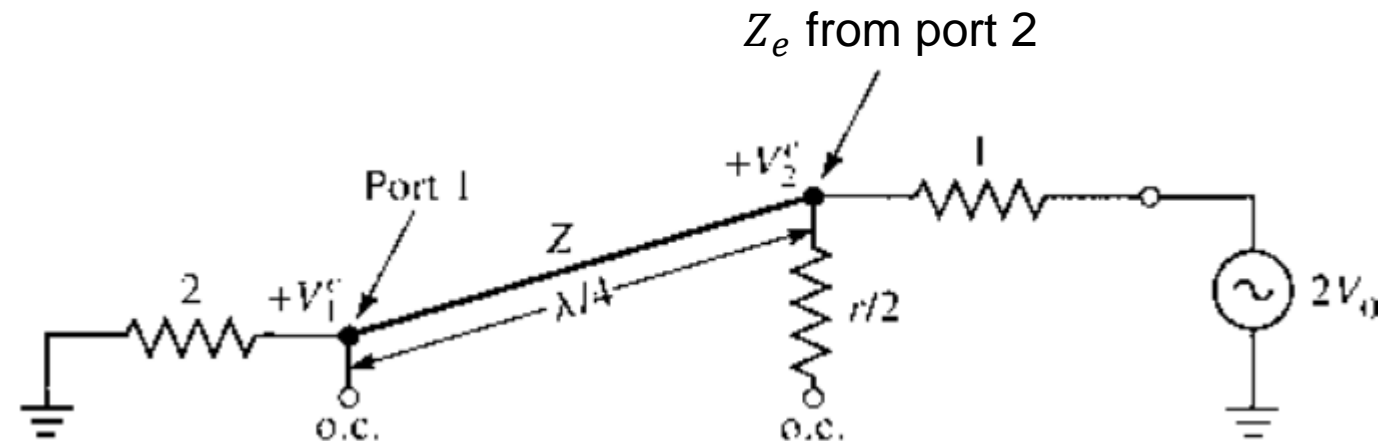6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ [$Z_{in}^e = Z \frac{2 + jZ \tan \frac{\beta\lambda}{4}}{Z + j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}$]
- Like quarter wave transformer, **If $Z = \sqrt{2}$, port 2 will be matched for even mode excitation** $Z_{in}^e = 2/2 = 1$ (1 is impedance at port 2)




6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ [$Z_{in}^e = Z \frac{2+jZ \tan \frac{\beta\lambda}{4}}{Z+j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}$]
- Like quarter wave transformer, If $Z = \sqrt{2}$, port 2 will be matched for even mode excitation $Z_{in}^e = 2/2=1$ (1 is impedance at port 2)

If $x = 0$ at port 1, and $x = -\lambda/4$ at port 2,
 $V(x) = V^+ (e^{-j\beta x} + \Gamma e^{j\beta x})$

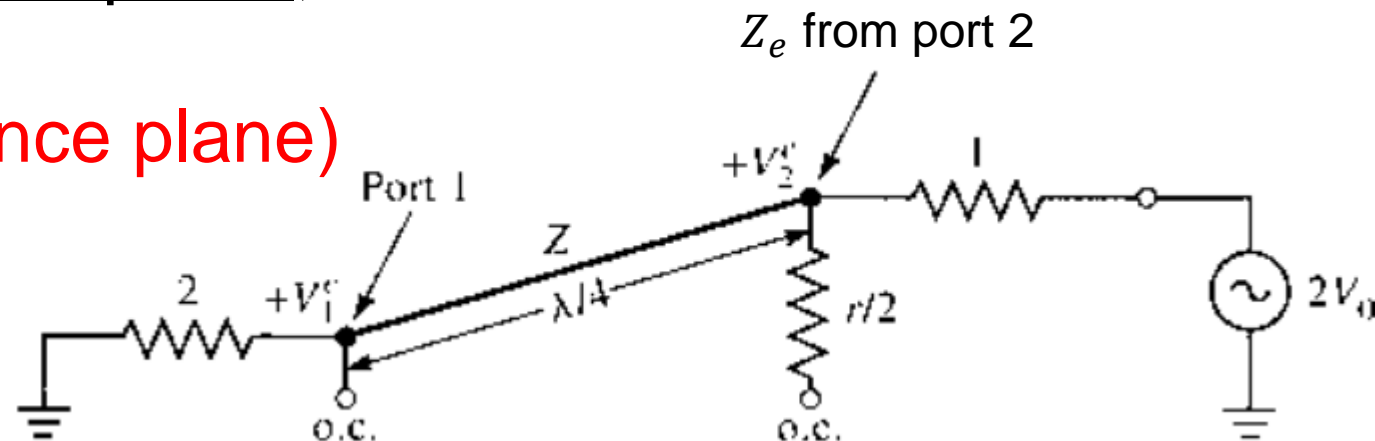(Phase shift due to shift in reference plane)



6.4c Even mode in Wilkinson Power divider


- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ [$Z_{in}^e = Z \frac{2+jZ \tan \frac{\beta\lambda}{4}}{Z+j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}$]
- Like quarter wave transformer, If $Z = \sqrt{2}$, port 2 will be matched for even mode excitation $Z_{in}^e = 2/2=1$ (1 is impedance at port 2)

If $x = 0$ at port 1, and $x = -\lambda/4$ at port 2,

$$V(x) = V^+ (e^{-j\beta x} + \Gamma e^{j\beta x})$$

$$V_2^e = V\left(-\frac{\lambda}{4}\right) = V^+ [0 + j + \Gamma(0 - j)]$$

$$= jV^+(1 - \Gamma) = V_0$$

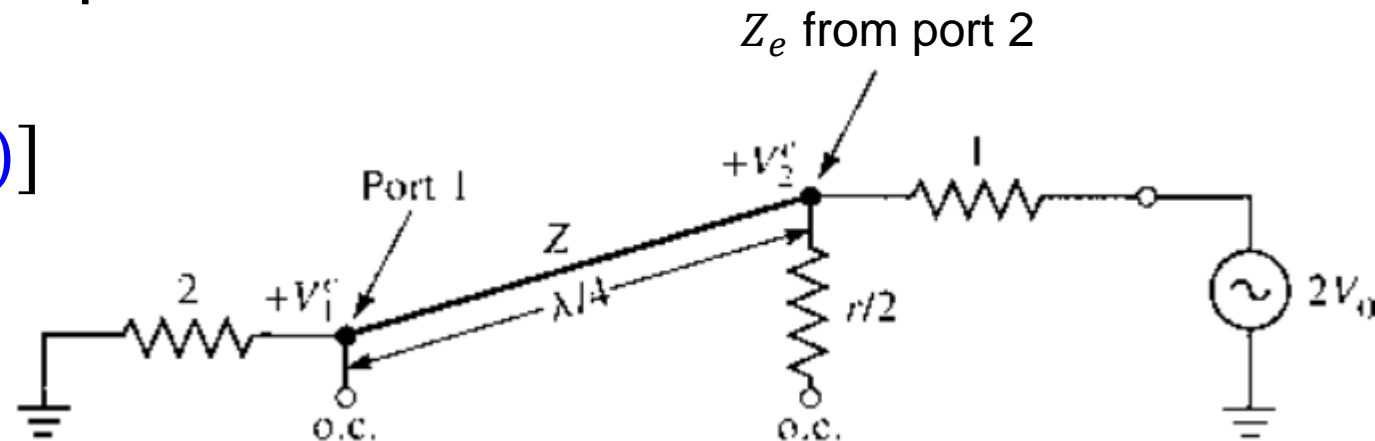

6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ [$Z_{in}^e = Z \frac{2+jZ \tan \frac{\beta\lambda}{4}}{Z+j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}$]
- Like quarter wave transformer, If $Z = \sqrt{2}$, port 2 will be matched for even mode excitation $Z_{in}^e = 2/2=1$ (1 is impedance at port 2)


If $x = 0$ at port 1, and $x = -\lambda/4$ at port 2,

$$V(x) = V^+ (e^{-j\beta x} + \Gamma e^{j\beta x})$$

$$V_2^e = V\left(-\frac{\lambda}{4}\right) = V^+ [0 + j + \Gamma(0 - j)]$$

$$= jV^+(1 - \Gamma) = V_0$$
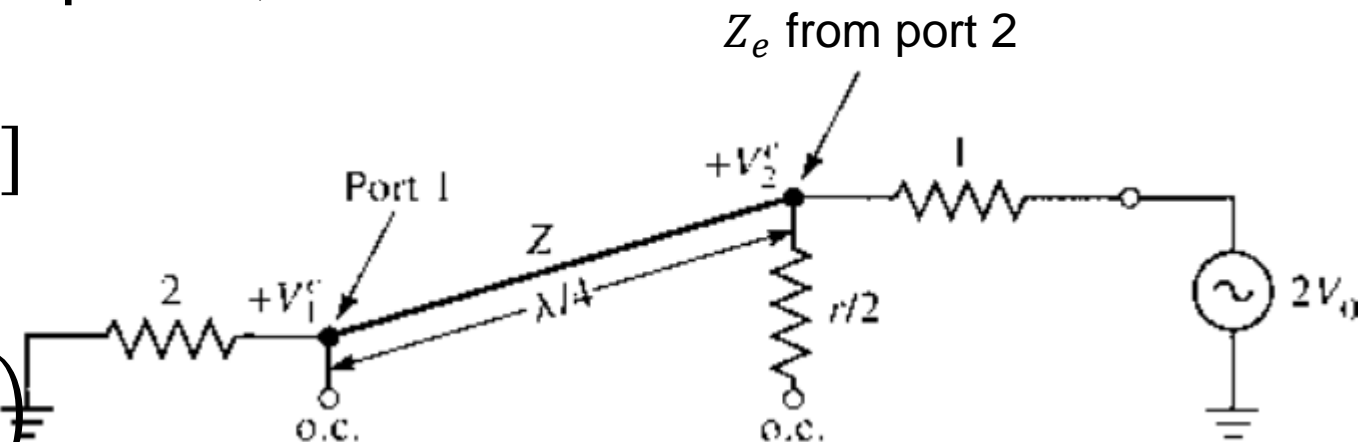
$$V_1^e = V(0) = jV^+ (1 + \Gamma) = jV_0 \left(\frac{\Gamma+1}{\Gamma-1} \right)$$



6.4c Even mode in Wilkinson Power divider

- Even mode: $V_{g2} = V_{g3} = 2V_0$ Port 2: $V_2^e = V_3^e$: Port 3
- Impedance Z_e from port 2: $Z_{in}^e = Z^2/2$ [$Z_{in}^e = Z \frac{2+jZ \tan \frac{\beta\lambda}{4}}{Z+j2 \tan \frac{\beta\lambda}{4}}$ with $\frac{\beta\lambda}{4} = \frac{\pi}{2}$]
- If $Z = \sqrt{2}$, port 2 will be matched for even mode excitation $Z_{in}^e = 2/2=1$ (1 is impedance at port 2)


$$V_2^e = jV^+(1 - \Gamma) = V_0$$

$$V_1^e = V(0) = jV^+(1 + \Gamma) = jV_0 \left(\frac{\Gamma+1}{\Gamma-1} \right)$$

Reflection coefficient at port 1



$$\Gamma = \frac{2-Z}{2+Z} = \frac{2-\sqrt{2}}{2+\sqrt{2}} \quad \text{and} \quad V_1^e = -jV_0\sqrt{2}$$

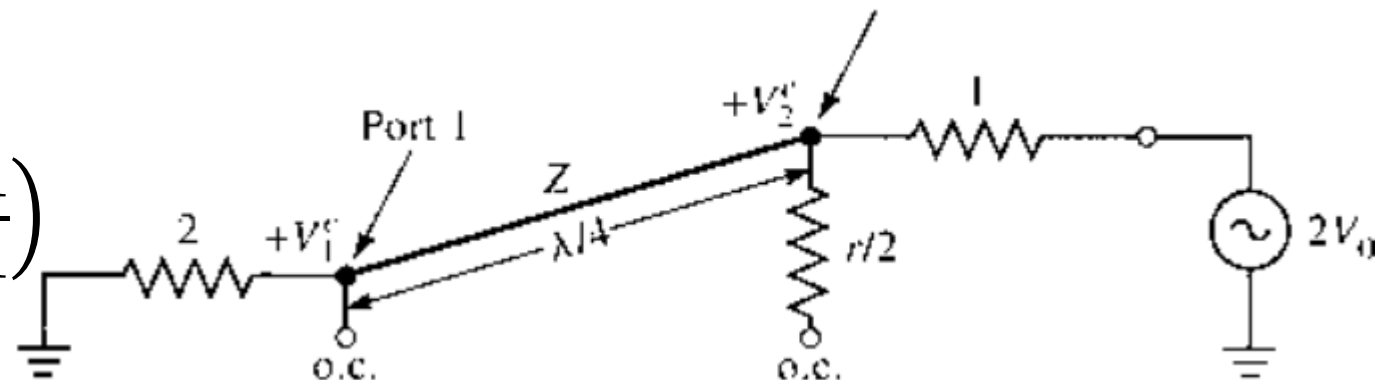Note: $\Gamma = \frac{Z_{in}-Z_0}{Z_{in}+Z_0}$



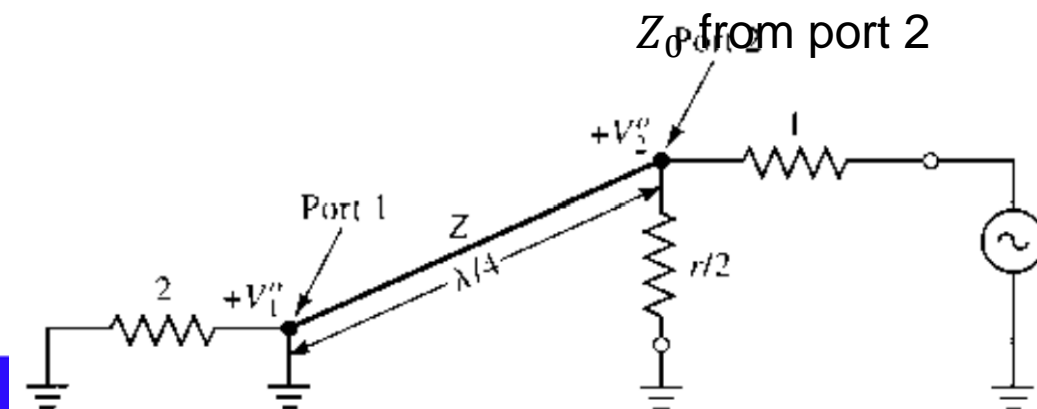
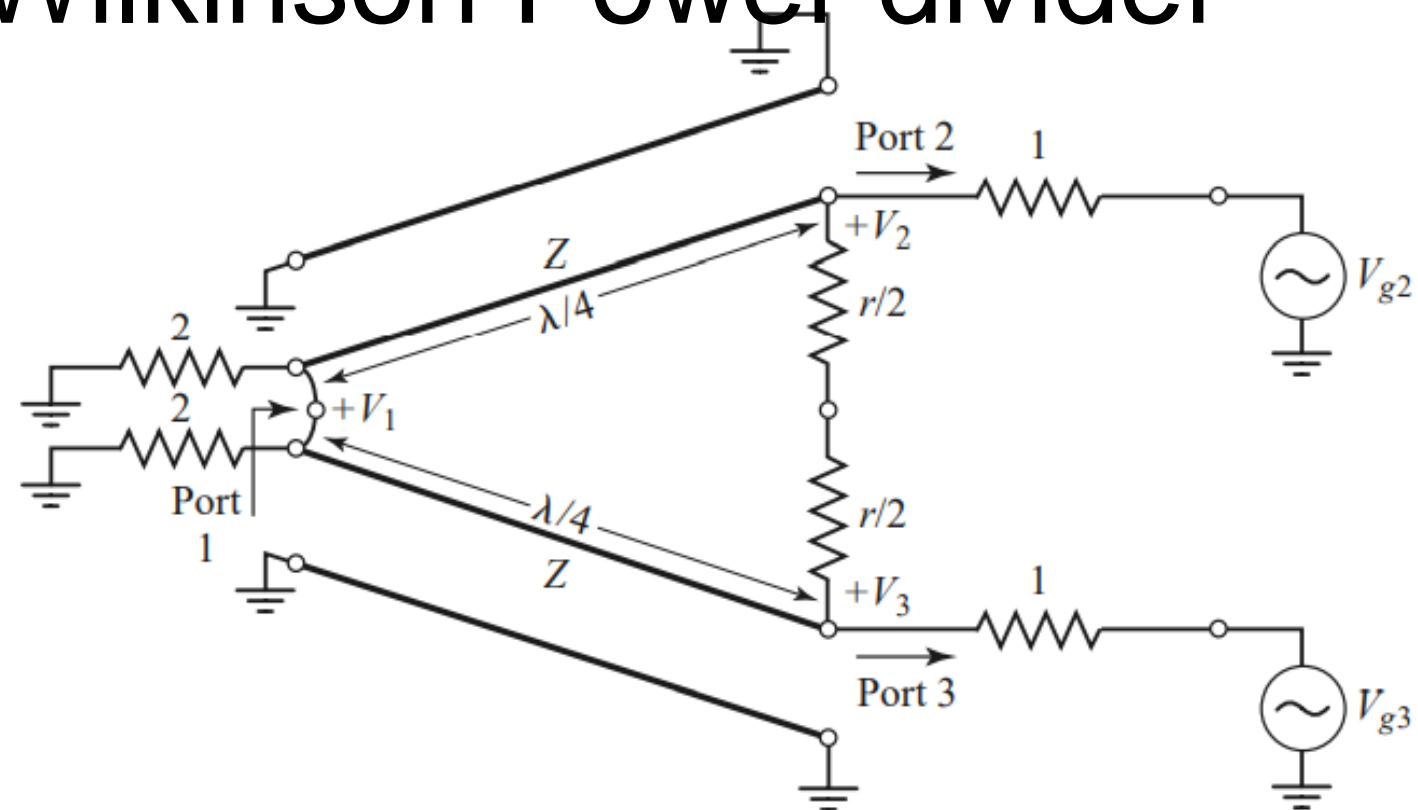
6.4d Odd mode in Wilkinson Power divider

- **Odd mode**: $V_{g2} = -V_{g3} = 2V_0$
- Port 2: $V_2^0 = -V_3^0$: Port 3



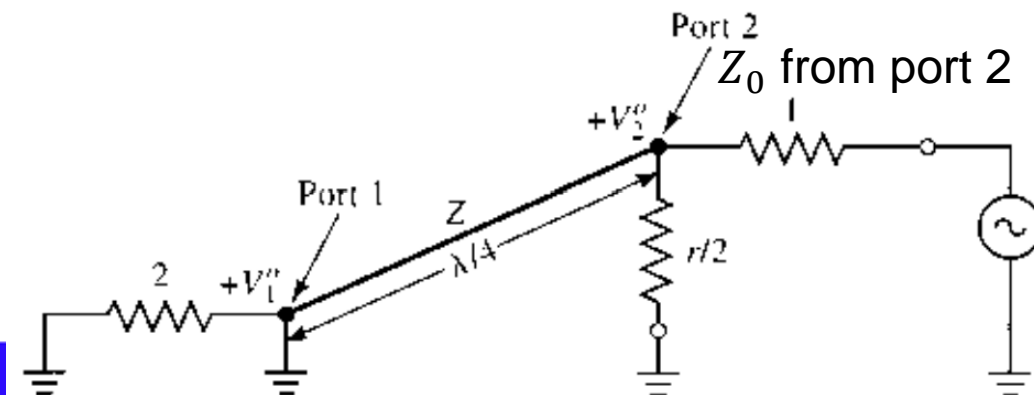
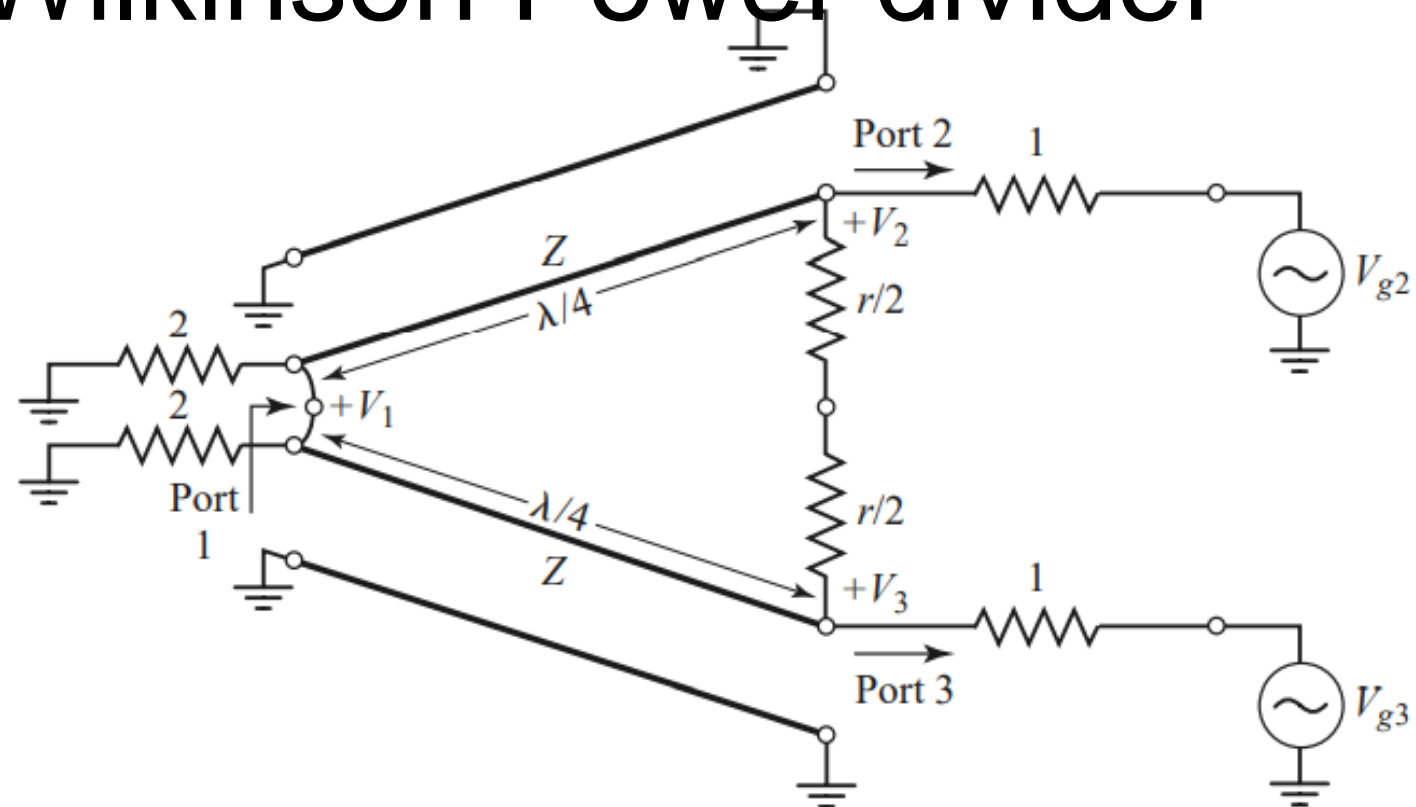
6.4d Odd mode in Wilkinson Power divider

- Odd mode: $V_{g2} = -V_{g3} = 2V_0$
- Port 2: $V_2^0 = -V_3^0$: Port 3
- **Voltage at port 1 is Opposite** as voltage will be opposite after $\lambda/4$ long transmission line.



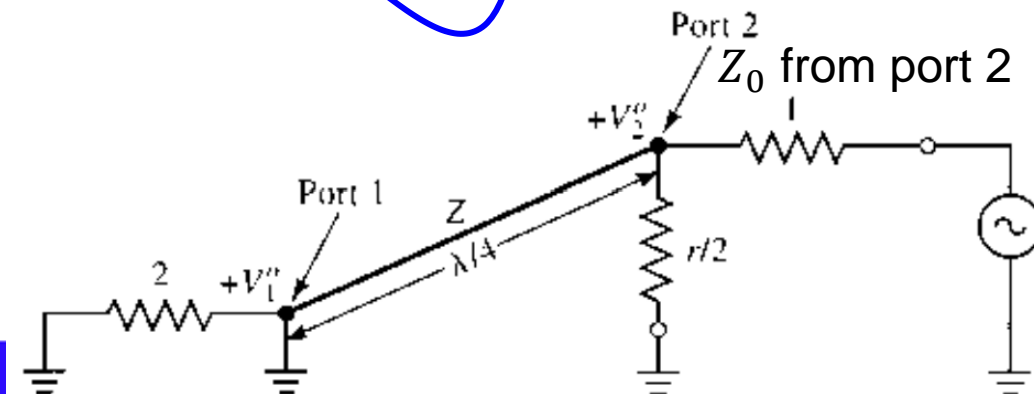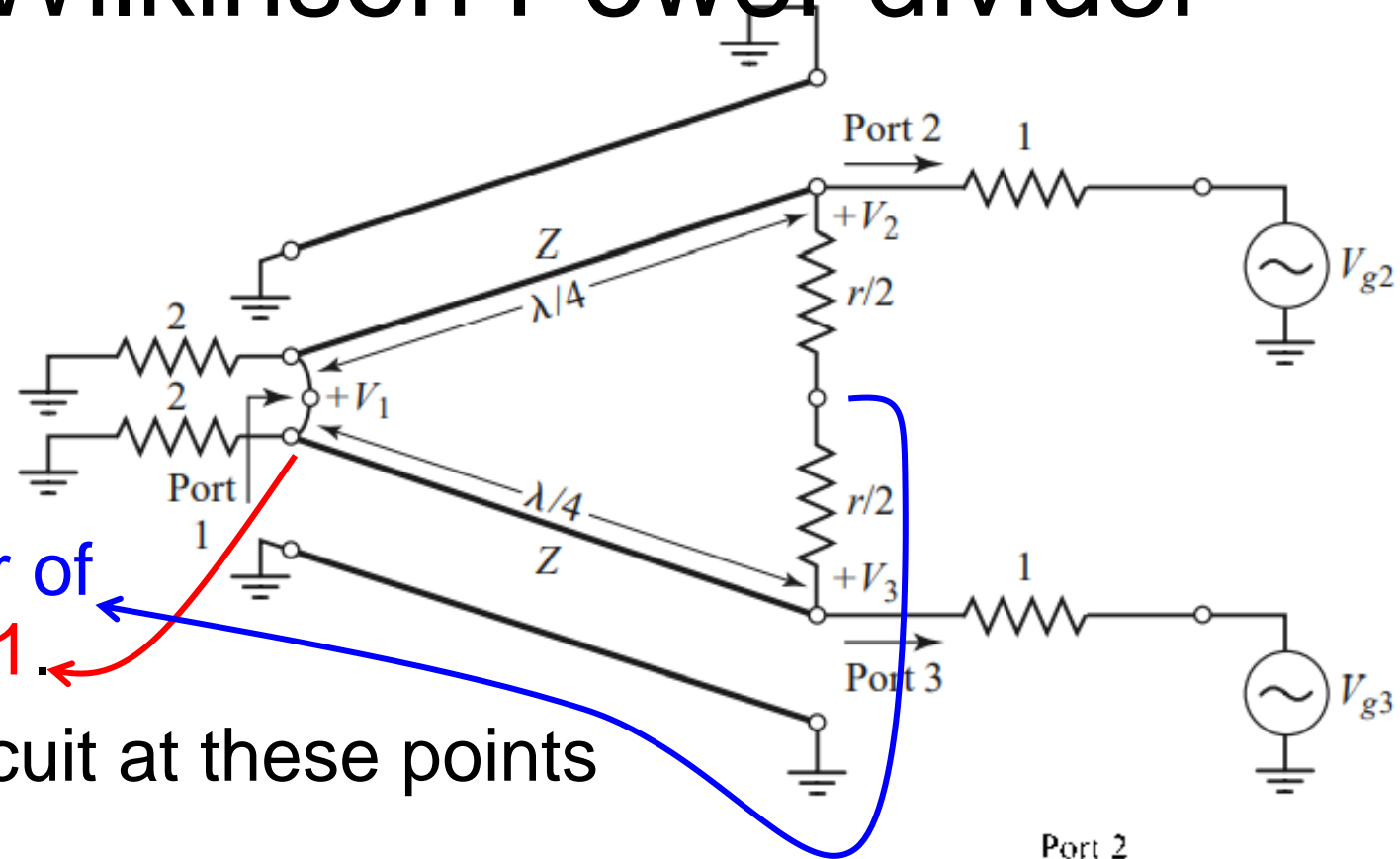6.4d Odd mode in Wilkinson Power divider



- Odd mode: $V_{g2} = -V_{g3} = 2V_0$
- Port 2: $V_2^0 = -V_3^0$: Port 3
- Voltage at port 1 is Opposite as voltage will be opposite after $\lambda/4$ long transmission line.
- Hence, **Center is zero at center of resistor r and the short at port 1.**
- Equivalent: Short to ground circuit at these points



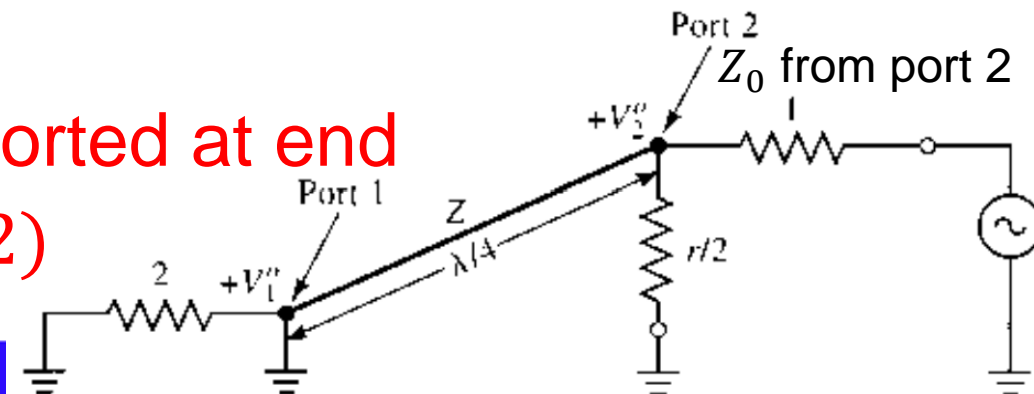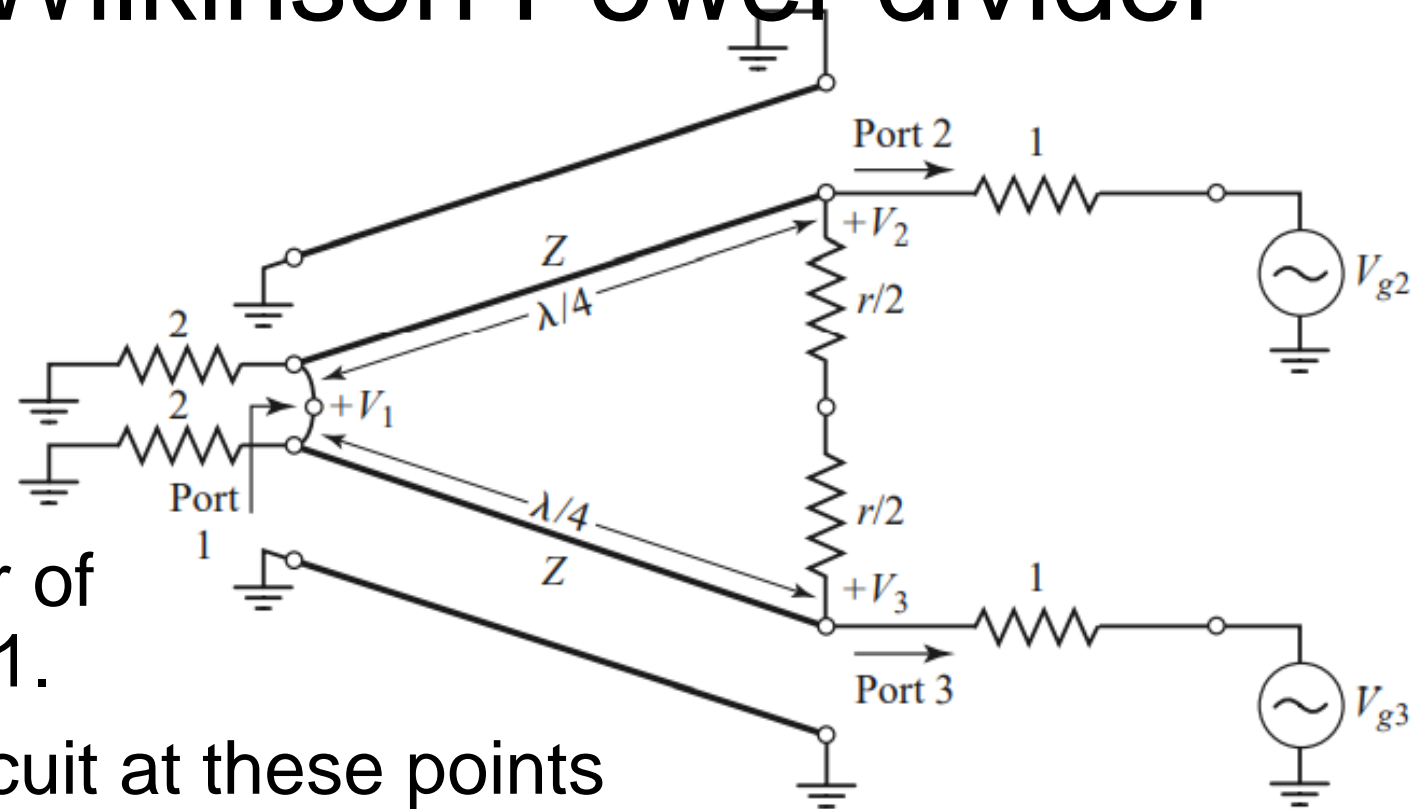6.4d Odd mode in Wilkinson Power divider



- Odd mode: $V_{g2} = -V_{g3} = 2V_0$
- Port 2: $V_2^0 = -V_3^0$: Port 3
- Voltage at port 1 is Opposite as voltage will be opposite after $\lambda/4$ long transmission line.
- Hence, Center is zero at center of resistor r and the short at port 1.
- Equivalent: Short to ground circuit at these points
- Impedance Z_0 from port 2:

$Z_{in}^0 = r/2$ parallel to $\frac{\lambda}{4}$ transmission line shorted at end
(Open tx line at port 2)



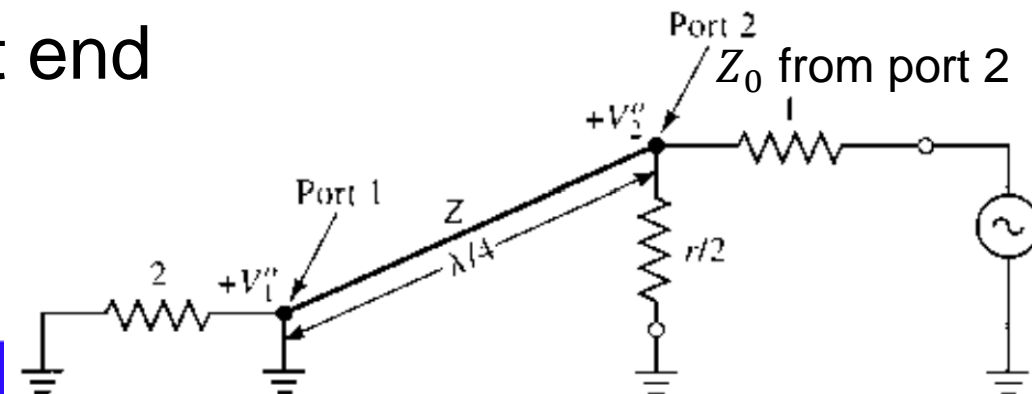
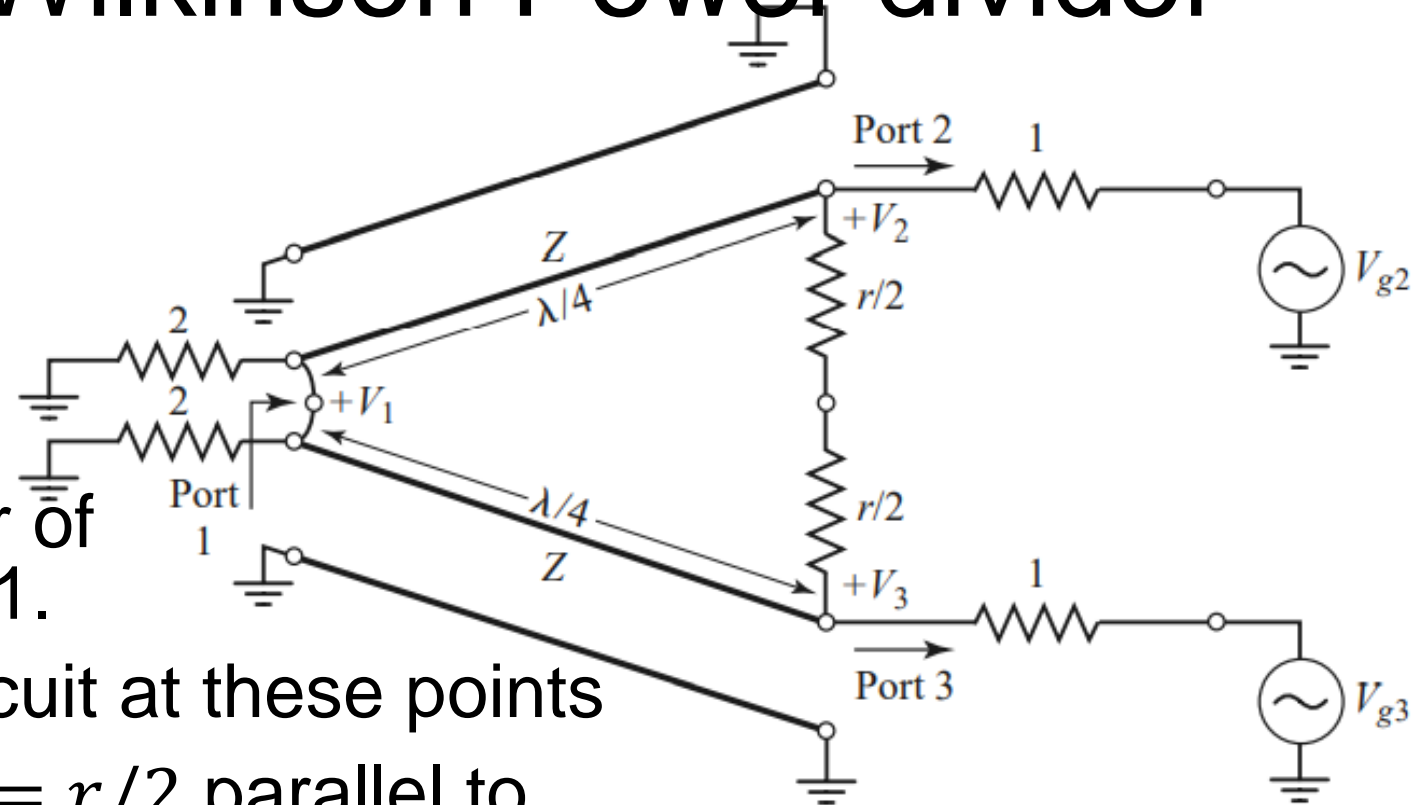
6.4d Odd mode in Wilkinson Power divider

- Odd mode: $V_{g2} = -V_{g3} = 2V_0$
- Port 2: $V_2^0 = -V_3^0$: Port 3
- Voltage at port 1 is Opposite as voltage will be opposite after $\lambda/4$ long transmission line.
- Hence, Center is zero at center of resistor r and the short at port 1.
- Equivalent: Short to ground circuit at these points
- Impedance Z_o from port 2: $Z_{in}^0 = r/2$ parallel to $\frac{\lambda}{4}$ transmission line shorted at end
(Open tx line at port 2)
- $Z_{in} = \frac{1}{2}(\sqrt{2})^2 = 1$



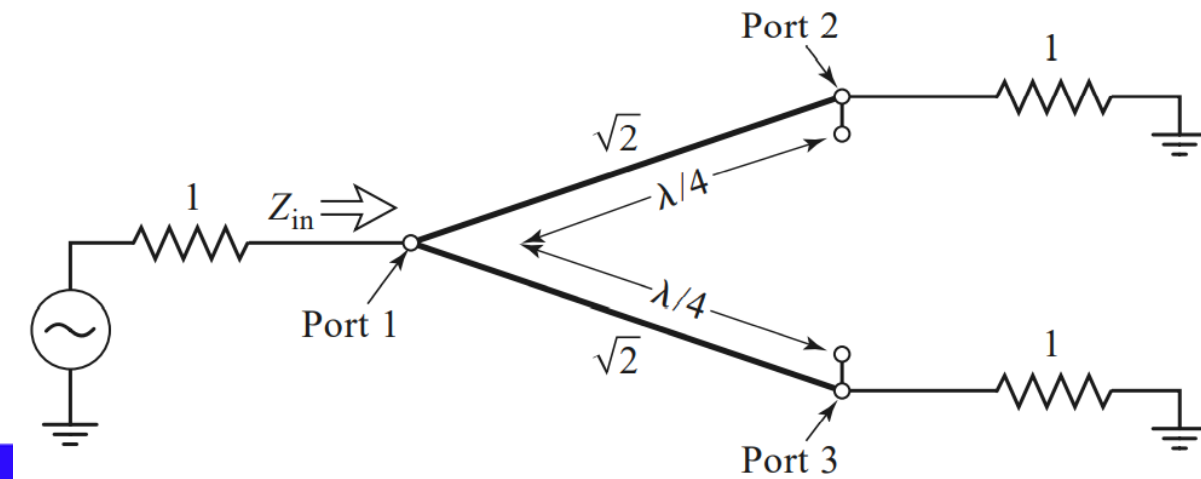
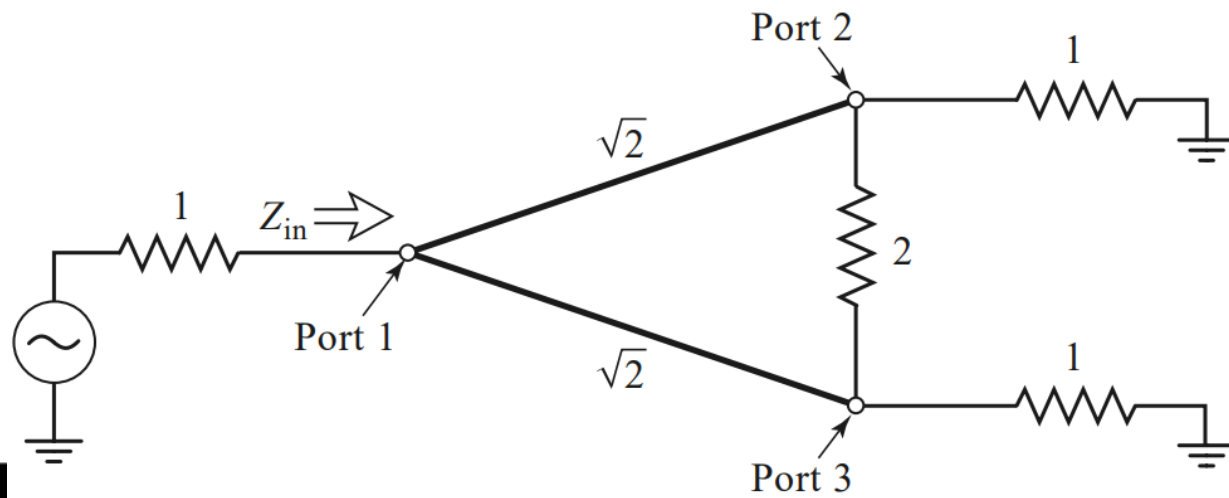
6.5 Summary Wilkinson Power divider

- $S_{11} = 0$ $Z_{in} = 1$ at port 1
- $S_{22} = S_{33} = 0$ (port 2 and port 3 matched for even and odd modes
as $Z_{in}^e = 1 = Z_{in}^o$)



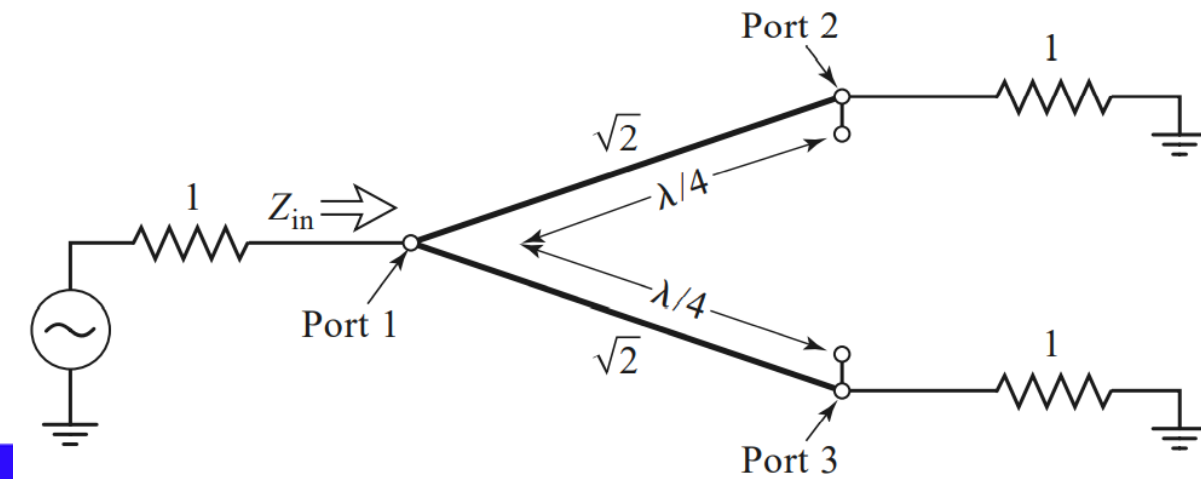
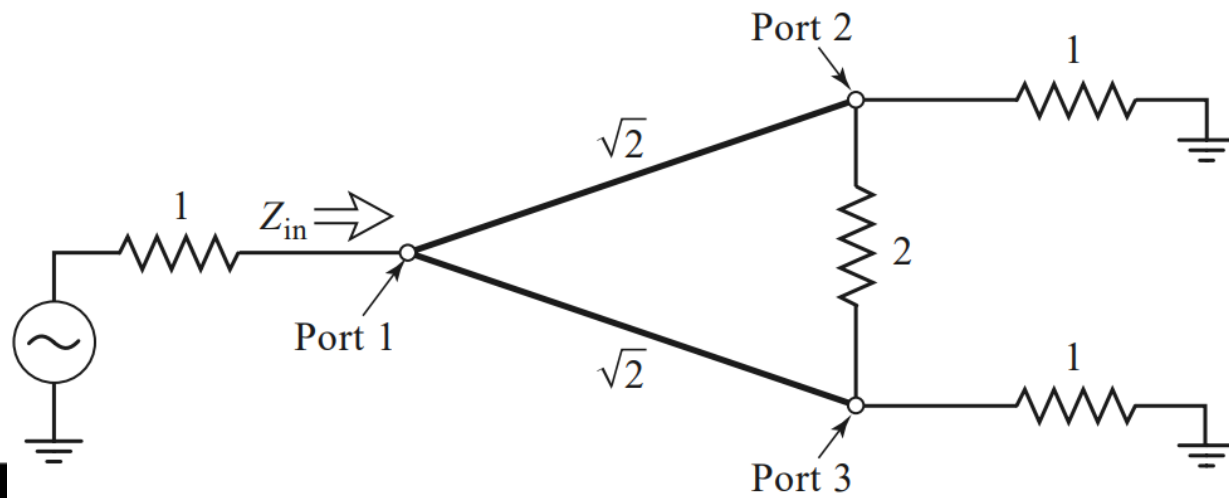
6.5 Summary Wilkinson Power divider

- $S_{11} = 0$ $Z_{in} = 1$ at port 1
- $S_{22} = S_{33} = 0$ (port 2 and port 3 matched for even and odd modes)
- $S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = -j/\sqrt{2}$ (symmetry due to reciprocity - all matched ports)



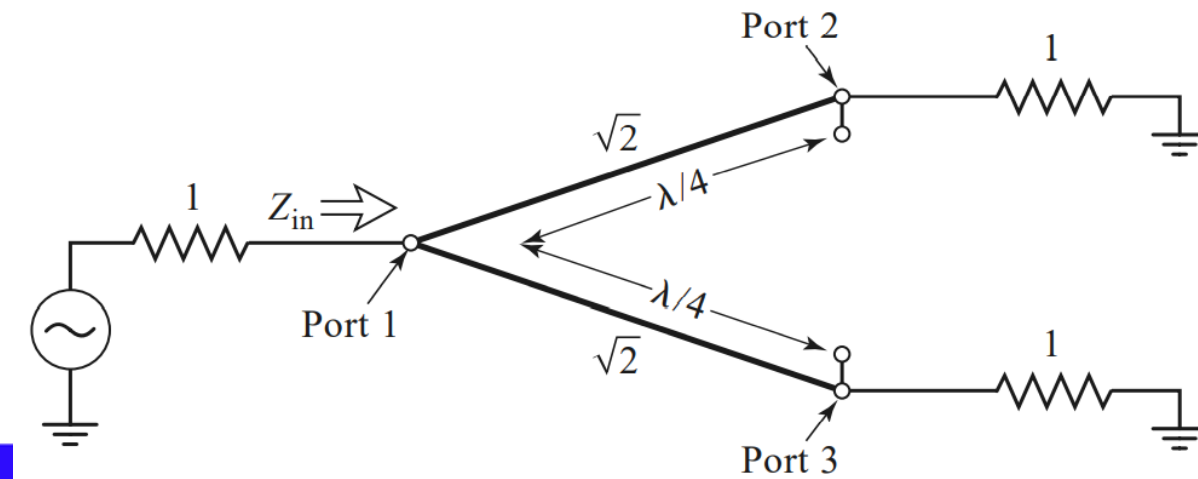
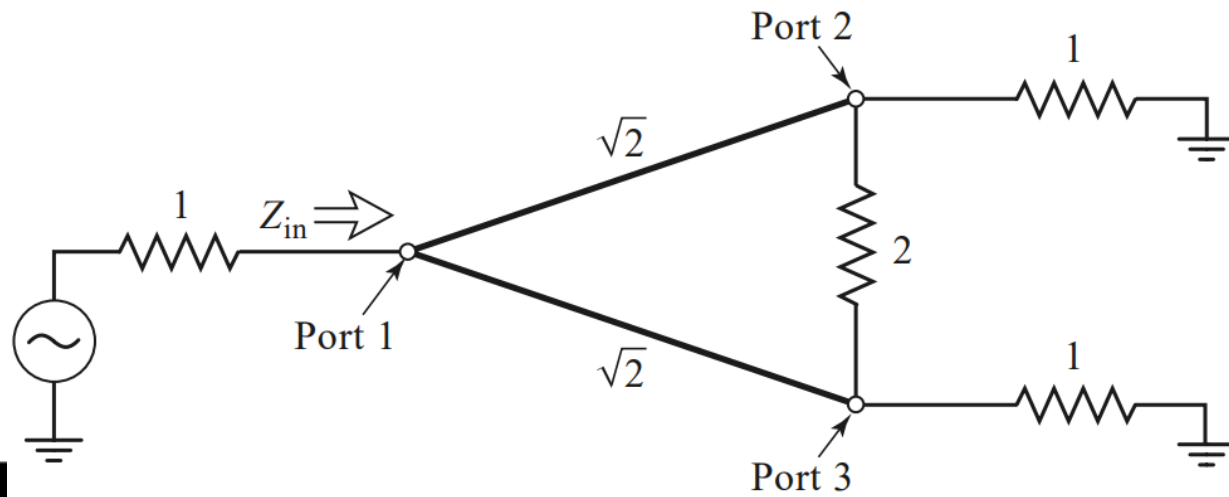
6.5 Summary Wilkinson Power divider

- $S_{11} = 0$ $Z_{in} = 1$ at port 1
- $S_{22} = S_{33} = 0$ (port 2 and port 3 matched for even and odd modes)
- $S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = -j/\sqrt{2}$ (symmetry due to reciprocity – all matched ports)
- $S_{13} = S_{31} = -j/\sqrt{2}$ (symmetry of ports 2 and 3)
- $S_{23} = S_{32} = 0$ (due to short or open at bisection)



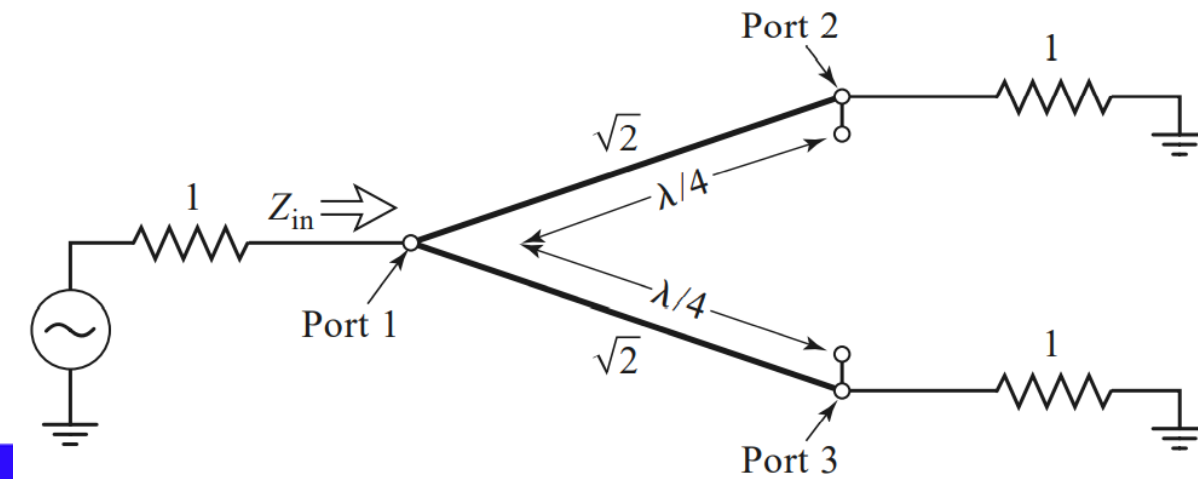
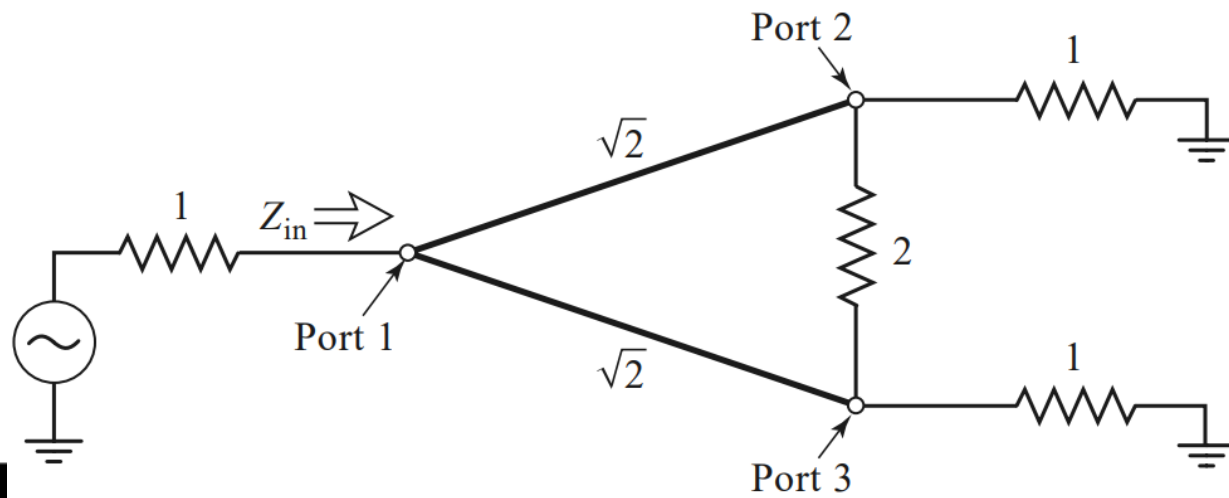
6.5 Summary Wilkinson Power divider

- Divider driven at port 1: **Outputs are matched:**
No power is dissipated in resistor.
Divider is lossless when outputs are matched.



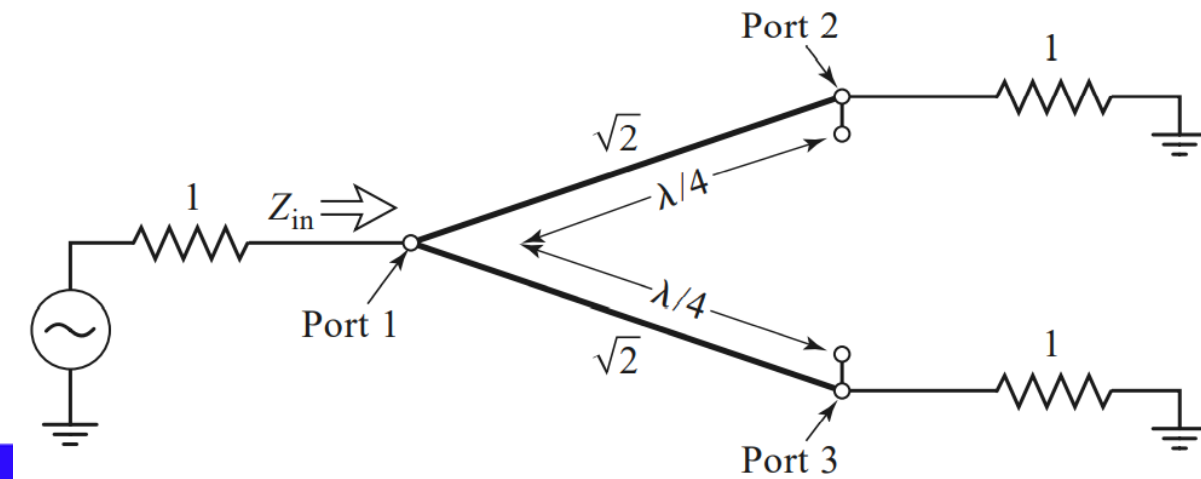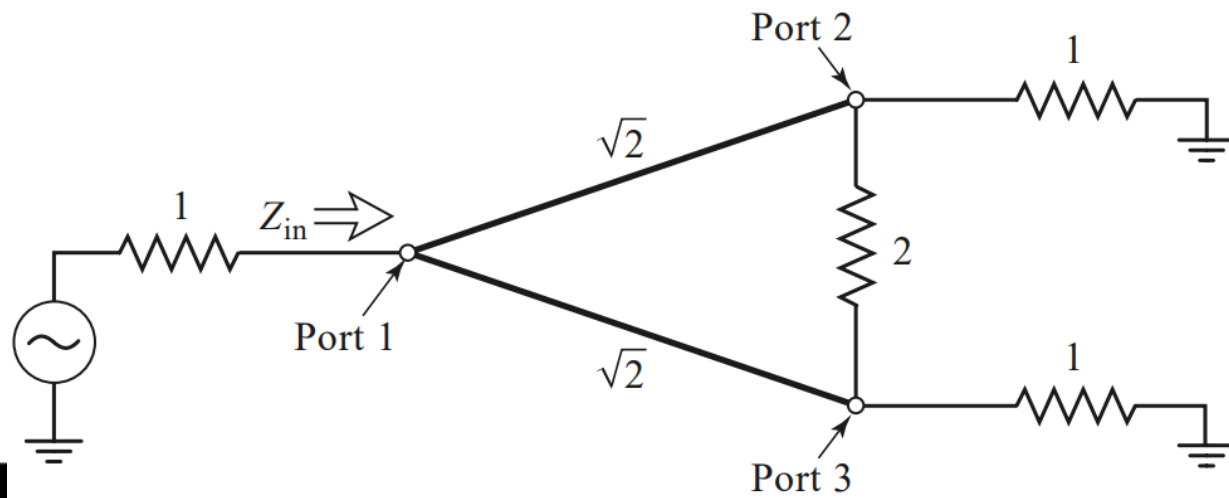6.5 Summary Wilkinson Power divider

- Divider driven at port 1: Outputs are matched:
No power is dissipated in resistor.
Divider is lossless when outputs are matched.
- **Reflected power from ports 2 or 3 is dissipated in resistor**
- $S_{23} = S_{32} = 0$: Ports 2 and 3 are isolated





For splitting the power equally at Ports 2 and 3 in the ratio of 1:1, using Wilkinson power divider when characteristic impedance is 70 ohms, Design the Wilkinson power divider network.

- **Find the values**

as shown in the figure:

with the given

characteristic impedance $Z_0 = 70$

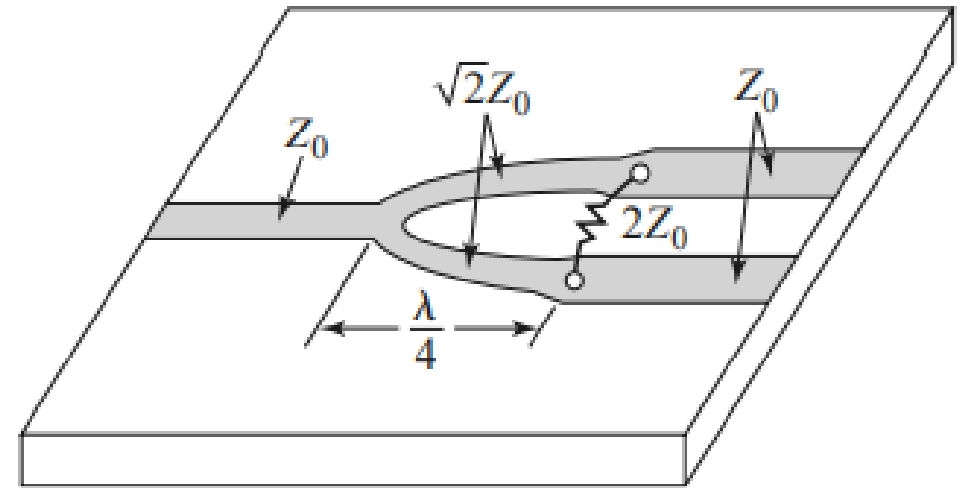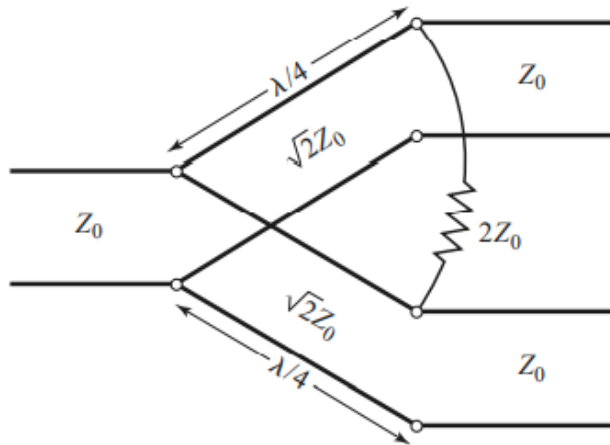

- The S matrix : $[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} = \begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & 0 & 0 \\ -j/\sqrt{2} & 0 & 0 \end{bmatrix}$