

6.6 MaximallyFlat(Binomial or Butterworth) and Chebychev(EqualRipple) filters

Module:6 Microwave Passive circuits
Course: BECE305L – Antenna and Microwave Engineering

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: richards.stanislaus@vit.ac.in



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI

Module:6 Microwave Passive circuits 7 hours

- T junction and resistive power divider, Wilkinson power divider, branch line coupler (equal & unequal), Rat Race Coupler, Filter design: Low pass filter (Butterworth and Chebyshev) - Richards transformation and stepped impedance methods.
- Source of the contents: Pozar

2. FILTER DESIGN BY THE INSERTION LOSS

METHOD: Characterization by Power loss ratio

- **Insertion loss method:**

a filter response is defined by its insertion loss, or power loss ratio, P_{LR} :

- $P_{LR} = \frac{\text{Power available from source}}{\text{Power delivered to the load}} = \frac{P_{inc}}{P_{load}} = \frac{1}{1-|\Gamma(\omega)|^2}$
- This quantity is reciprocal of $|S_{12}|^2$ if both load and source are matched.
- Insertion loss (IL)= $10 \log_{10} P_{LR}$
- $|\Gamma(\omega)|^2$ is an even function of ω . It can be expressed as polynomials M and N in ω^2 : $|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2)+N(\omega^2)}$
- $P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$ Reflection ratio is also constrained.

2.1 Characterization by Power loss ratio:


a) Maximally flat (Binomial or Butterworth response)

- Provides flattest possible passband response for given filter complexity.

- Low pass filter, it is specified by

$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

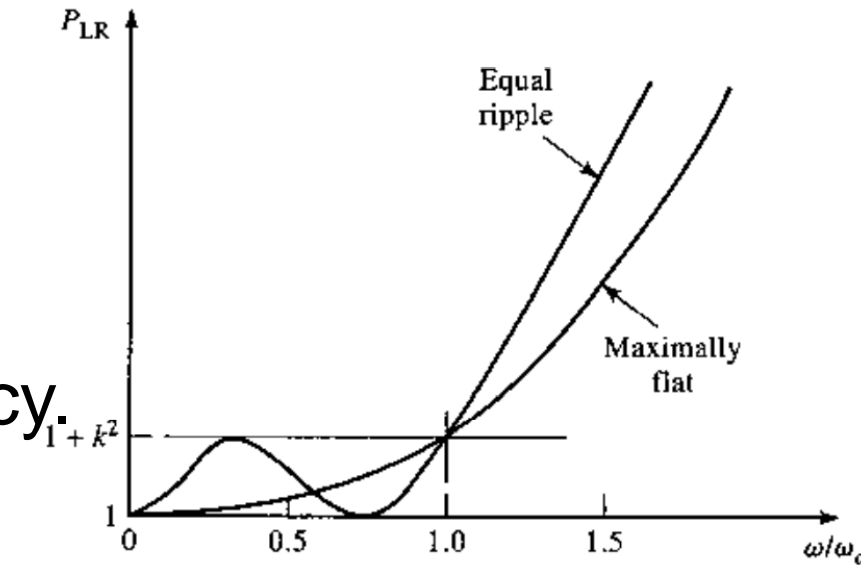- N is order of the filter and ω_c is cutoff frequency.
- Pass band extends from $\omega = 0$ to $\omega = \omega_c$
- At the edge, the power loss ratio is $1 + k^2$ (If -3dB point, $k = 1$)



2.1 Characterization by Power loss ratio:

a) Maximally flat (**Binomial or Butterworth response**)

- For $\omega > \omega_c$, attenuation increases monotonically with frequency.
- For $\omega \gg \omega_c$, $P_{LR} \approx k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$ (Insertion loss increases at rate of 20dB/decade)
- Like binomial response, for multisection quarter-wave matching transformer, the first $(2N - 1)$ derivatives are zero at $\omega = 0$.

2.1 Characterization by Power loss ratio:

b) Equal ripple (Chebyshev)

- Chebyshev polynomial is used to specify insertion loss ***Nth order low pass filter*** as

$$P_{LR} = 1 + k^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)$$

2.1 Characterization by Power loss ratio:

b) Equal ripple (Chebyshev)

- Chebyshev polynomial is used to specify insertion loss Nth order low pass filter as

$$P_{LR} = 1 + k^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)$$

Results in a **sharper cutoff** but with **ripples in passband**

Ripple amplitude $1 + k^2$, with $T_N(x)$ oscillates between ± 1 for $|x|^2 < 1$

- Thus Passband ripple level are dependent on k^2

2.1 Characterization by Power loss ratio:

b) Equal ripple (Chebyshev)

- Chebyshev polynomial is used to specify insertion loss Nth order low pass filter as

$$P_{LR} = 1 + k^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)$$

Results in a sharper cutoff but with ripples in passband

Ripple amplitude $1 + k^2$, with $T_N(x)$ oscillates between ± 1 for $|x|^2 < 1$

- Thus Passband ripple level are dependent on k^2

- For **large** x , $T_n(x) \approx \frac{1}{2} (2x)^N$

For $\omega \gg \omega_c$, insertion loss $P_{LR} \approx \frac{k^2}{4} \left(\frac{2\omega}{\omega_c} \right)^{2N}$


Chebyshev case $> \frac{2^{2N}}{4}$ times binomial case

- This also increases at $20N \text{ dB/decade}$

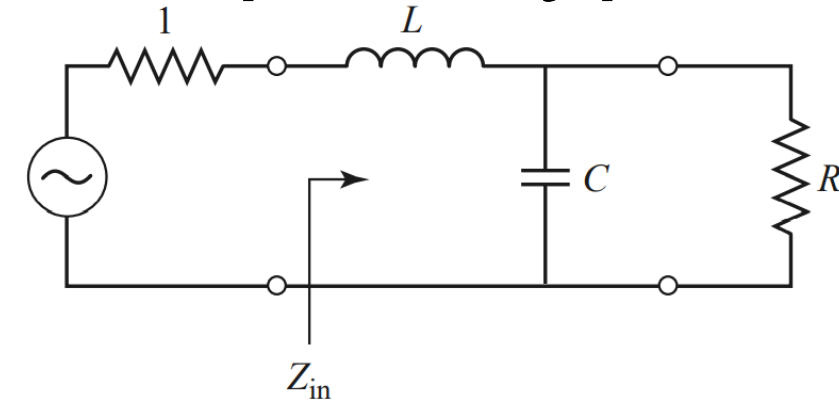3.1 Maximally flat low pass filter prototype


- Consider **2 element Low pass filter prototype**
- Normalized element values L and C for maximally flat response.

$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$



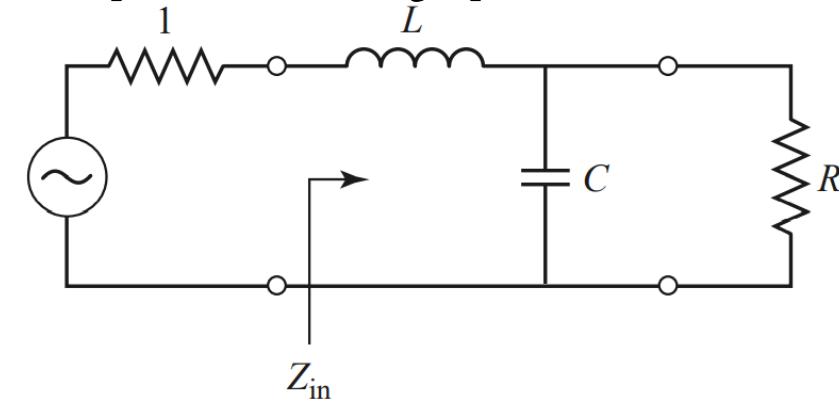3.1 Maximally flat low pass filter prototype

- Consider 2 element Low pass filter prototype
- Normalized element values L and C for maximally flat response.




$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

- Source impedance of 1Ω and cutoff frequency $\omega_c = 1$ rad/sec
- Desired loss ratio for $N = 4$,

$$P_{LR} = 1 + \omega^4$$

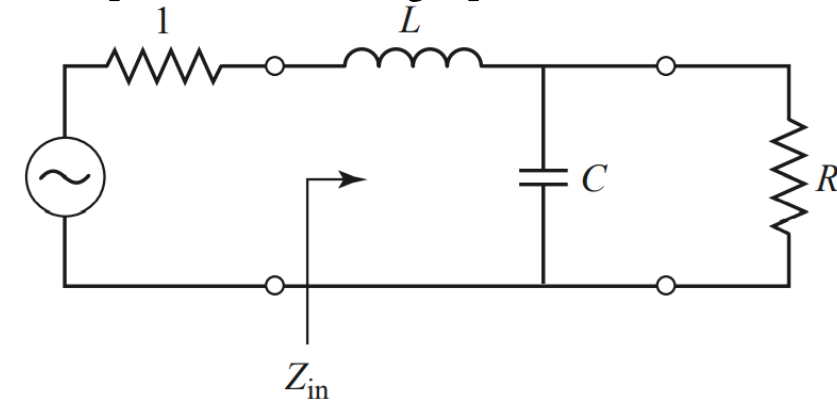3.1 Maximally flat low pass filter prototype

- Consider 2 element Low pass filter prototype
- Normalized element values L and C for maximally flat response.



$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$


- Source impedance of 1Ω and cutoff frequency $\omega_c = 1$ rad/sec
- Desired loss ratio for $N = 4$,

$$P_{LR} = 1 + \omega^4$$

- Input impedance of this filter $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$

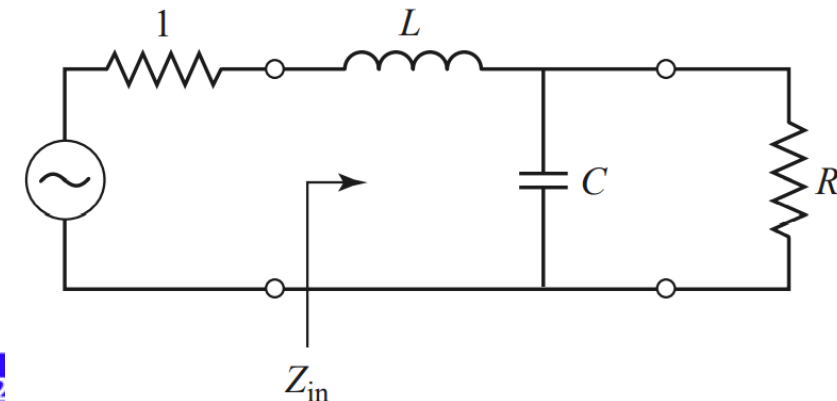
3.1 Maximally flat low pass filter prototype

- $P_{LR} = 1 + \omega^4$ $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$



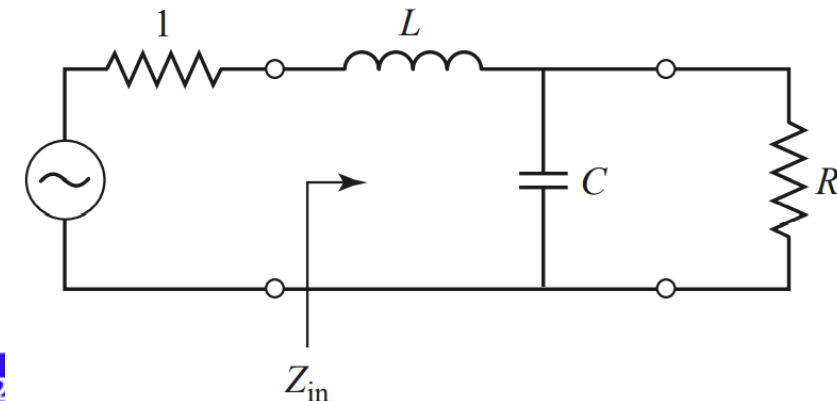3.1 Maximally flat low pass filter prototype


- $P_{LR} = 1 + \omega^4$ $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$
- This is expression of polynomial in ω^2
- $R = 1$ since $P_{LR} = 1$ for $\omega = 0$



3.1 Maximally flat low pass filter prototype

- $P_{LR} = 1 + \omega^4$ $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$
- This is expression of polynomial in ω^2
- $R = 1$ since $P_{LR} = 1$ for $\omega = 0$
- Coefficient of ω^2 must vanish

$$C^2 + L^2 - 2LC = (C - L)^2 = 0$$

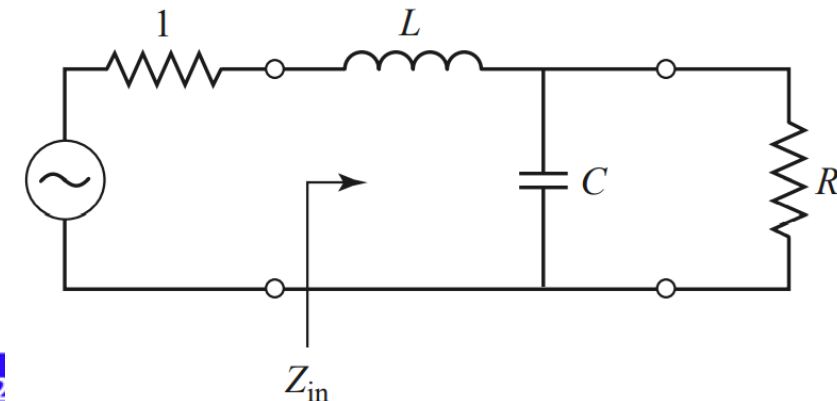


3.1 Maximally flat low pass filter prototype

- $P_{LR} = 1 + \omega^4 \quad Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1-R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$
- This is expression of polynomial in ω^2
- $R = 1$ since $P_{LR} = 1$ for $\omega = 0$
- Coefficient of ω^2 must vanish


$$C^2 + L^2 - 2LC = (C - L)^2 = 0$$
- The $L = C$. For coefficient of ω^4 to be unity,
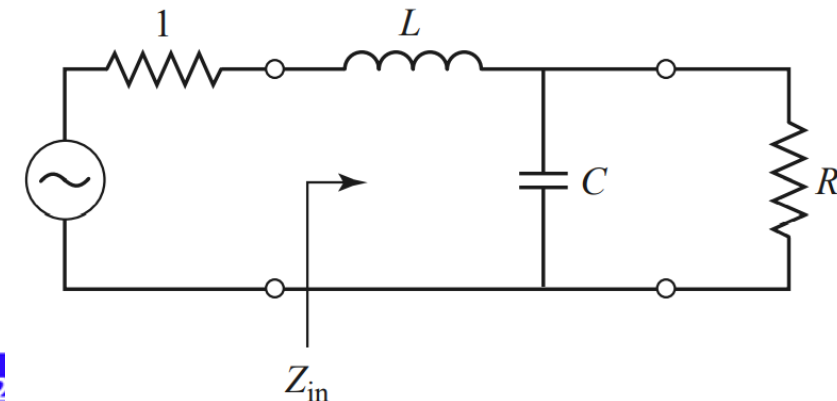
$$\frac{1}{4} L^2 C^2 = \frac{1}{4} L^4 = 1 \quad L = C = \sqrt{2}$$



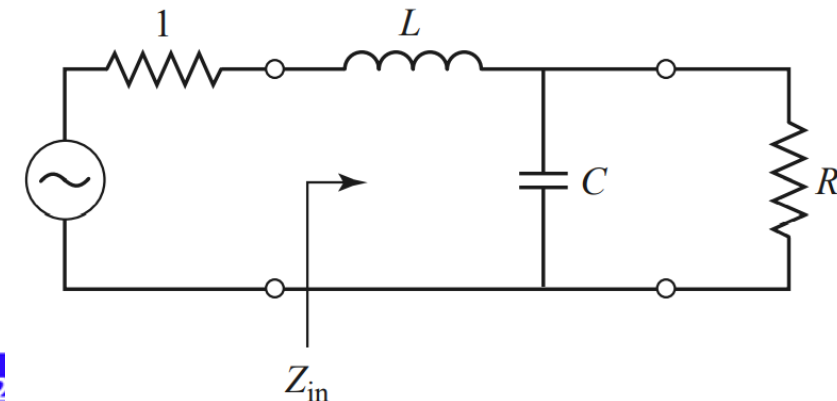
3.1 Maximally flat low pass filter prototype

- $P_{LR} = 1 + \omega^4$ $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 R^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$
- $L = C = \sqrt{2}$
- **Procedure can be extended to find the element values for filters with arbitrary N elements.**



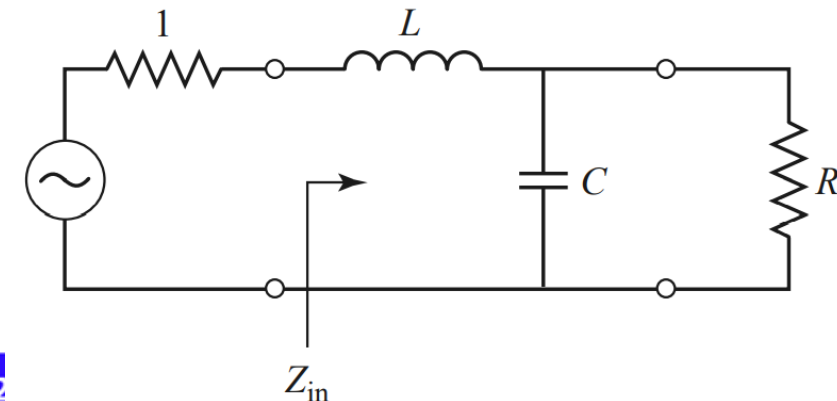3.1 Maximally flat low pass filter prototype

- $P_{LR} = 1 + \omega^4$ $Z_{in} = j\omega L + \frac{R(1-j\omega RC)}{1+\omega^2 R^2 C^2}$
- $P_{LR} = 1 + \frac{1}{4R^2} [(1 - R)^2 + (R^2 C^2 + L^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$
- $L = C = \sqrt{2}$
- Procedure can be extended to find the element values for filters with arbitrary N elements.
- **For normalized low pass design, source impedance is 1Ω and cutoff frequency ω_c rad/sec**
- Element values for ladder type circuit are given



3.1 Maximally flat low pass filter prototype

- Element values for ladder type circuit are given with $g_0 = 1, \omega_c = 1, N = 1$ to 10 .

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.


3.1 Maximally flat low pass filter prototype

- g_0 is generator impedance is 1
- g_{N+1} is at the load impedance for a filter having N reactive elements
- Series
 $g_0 = \text{generator resistance} / \text{generator conductance}$


3.1 Maximally flat low pass filter prototype

- Element values for ladder type circuit are given

Prototype beginning
with shunt element

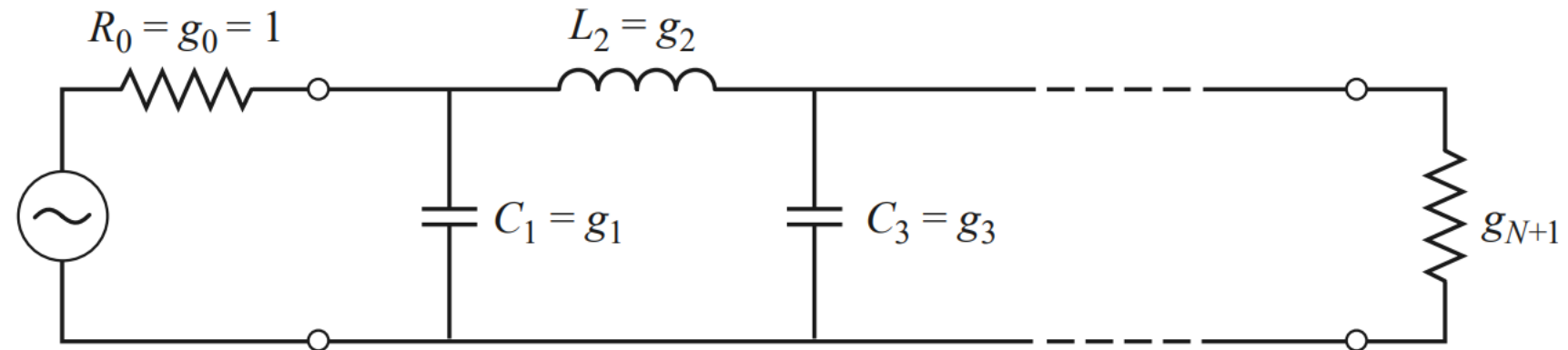

Prototype beginning
with series element

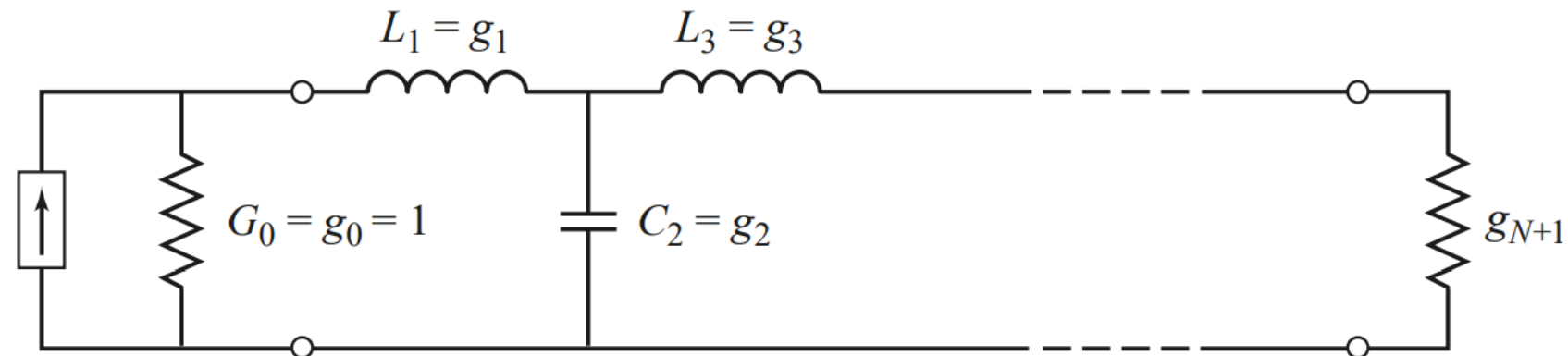


3.1 Maximally flat low pass filter prototype

- g_0 is generator impedance is 1
- g_{N+1} is at the load impedance for a filter having N reactive elements
- Series
 - $g_0 = \text{generator resistance} / \text{generator conductance}$
 - g_k ($k = 1 \text{ to } N$) = inductance for series inductors
capacitance for shunt capacitors


3.1 Maximally flat low pass filter prototype

- Element values for ladder type circuit are given

Prototype beginning
with shunt element

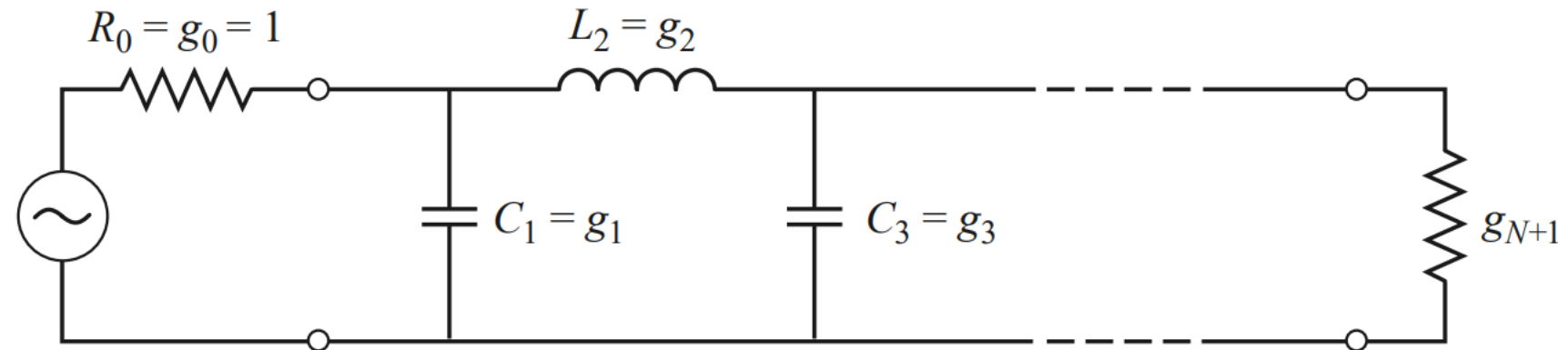

Prototype beginning
with series element

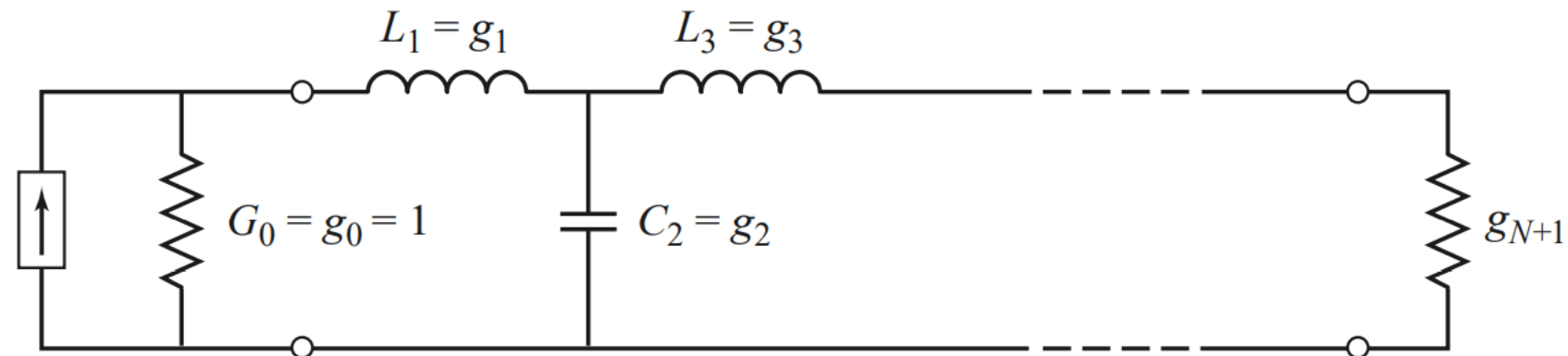

3.1 Maximally flat low pass filter prototype

- g_0 is generator impedance is 1
- g_{N+1} is at the load impedance for a filter having N reactive elements

- Series

$g_0 = \text{generator resistance} / \text{generator conductance}$

g_k ($k = 1 \text{ to } N$) = inductance for series inductors

capacitance for shunt capacitors


$g_{N+1} = \text{load resistance if } g_N \text{ is a shunt capacitor}$

load conductance if g_N is a series inductor


3.1 Maximally flat low pass filter prototype

- Element values for ladder type circuit are given

Prototype beginning with shunt element

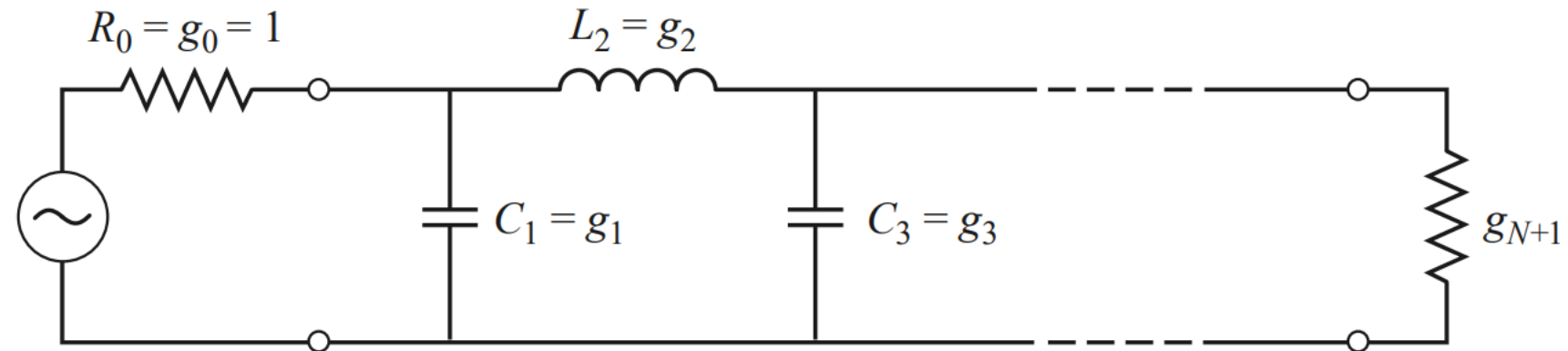


Prototype beginning with series element

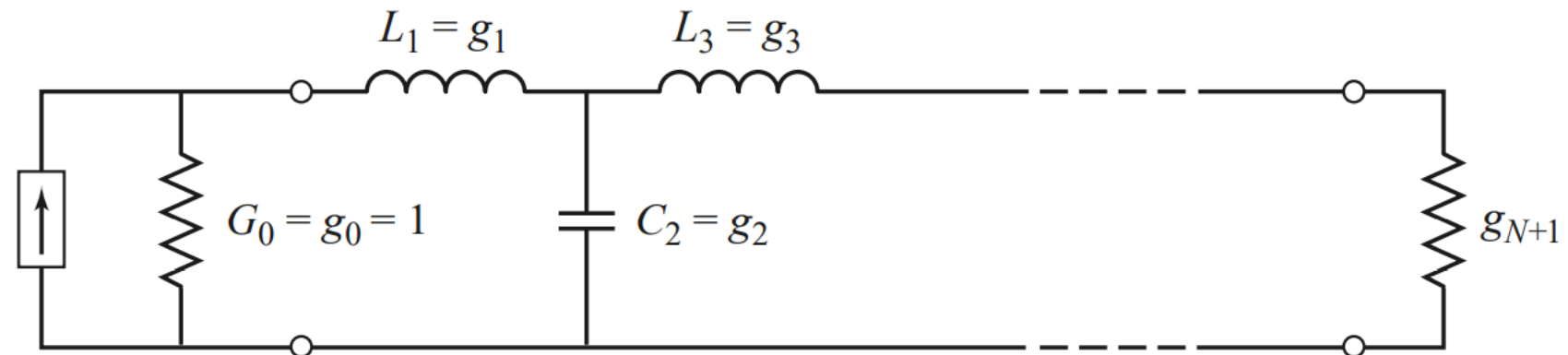

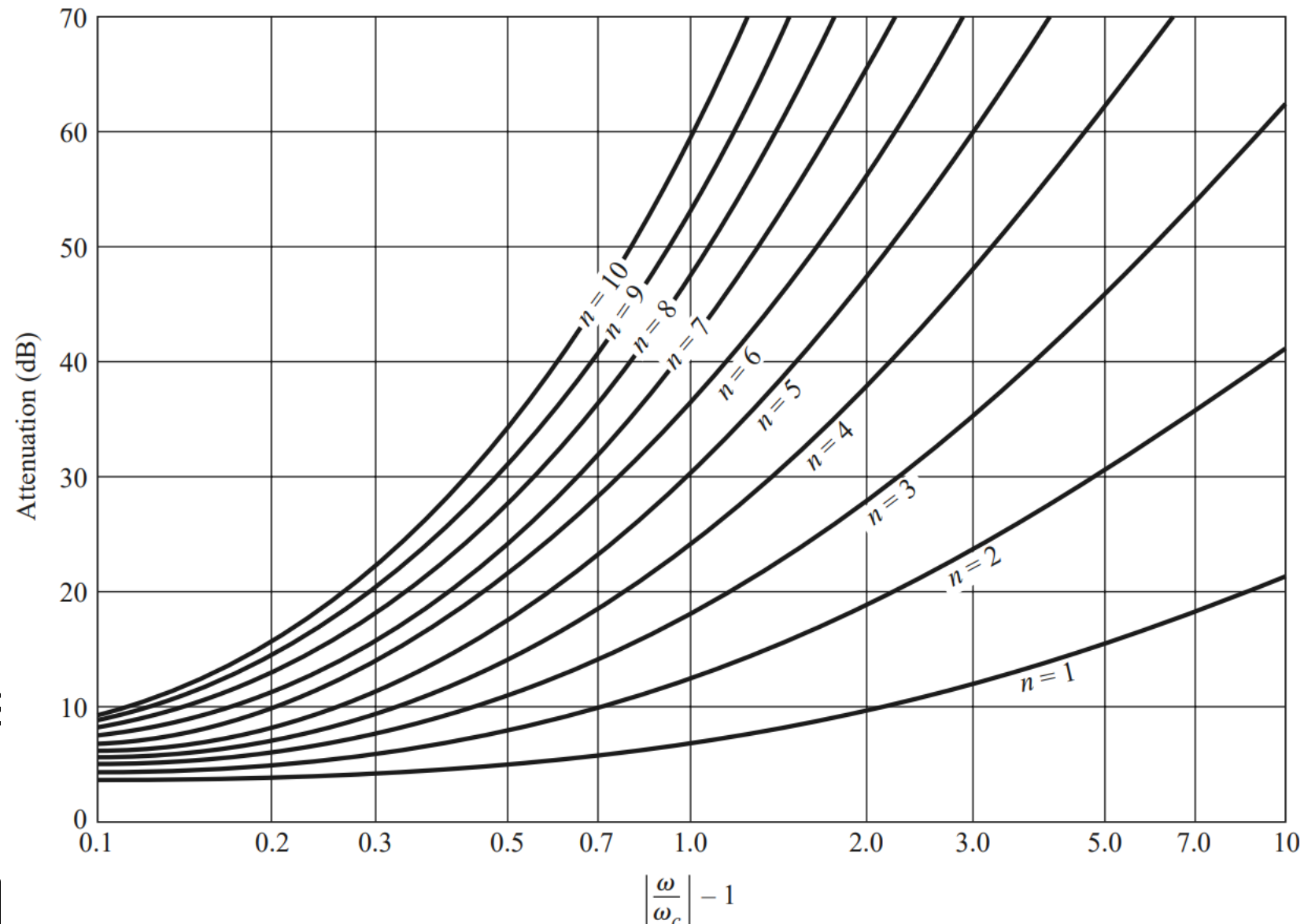3.1 Maximally flat low pass filter prototype

- Both the circuits will give same response.
- Attenuation characteristics for various N vs Frequency
- For $N > 10$, Two lower order filters in cascade are used.



4. Equal ripple Low Pass filter prototype (Chebyshev)

- $\omega_c = 1 \text{ rad/sec}$
Power loss ratio: $P_{LR} = 1 + k^2 T_N^2(\omega)$
 $1 + k^2$: ripple level in passband
-

4. Equal ripple Low Pass filter prototype (Chebyshev)

- $\omega_c = 1 \text{ rad/sec}$
Power loss ratio: $P_{LR} = 1 + k^2 T_N^2(\omega)$
 $1 + k^2$: ripple level in passband
- Chebyshev polynomial property: $T_N(0) = \begin{cases} 0 & \text{for } N \text{ odd,} \\ 1 & \text{for } N \text{ even,} \end{cases}$
-


4. Equal ripple Low Pass filter prototype (Chebyshev)

- $\omega_c = 1 \text{ rad/sec}$
Power loss ratio: $P_{LR} = 1 + k^2 T_N^2(\omega)$
 $1 + k^2$: ripple level in passband
- Chebyshev polynomial property: $T_N(0) = \begin{cases} 0 & \text{for } N \text{ odd,} \\ 1 & \text{for } N \text{ even,} \end{cases}$
- Filter will have the power loss ratio
 $P_{LR} = 1$ at $\omega = 0$ for N odd
 $P_{LR} = 1 + k^2$ at $\omega = 0$ for N even

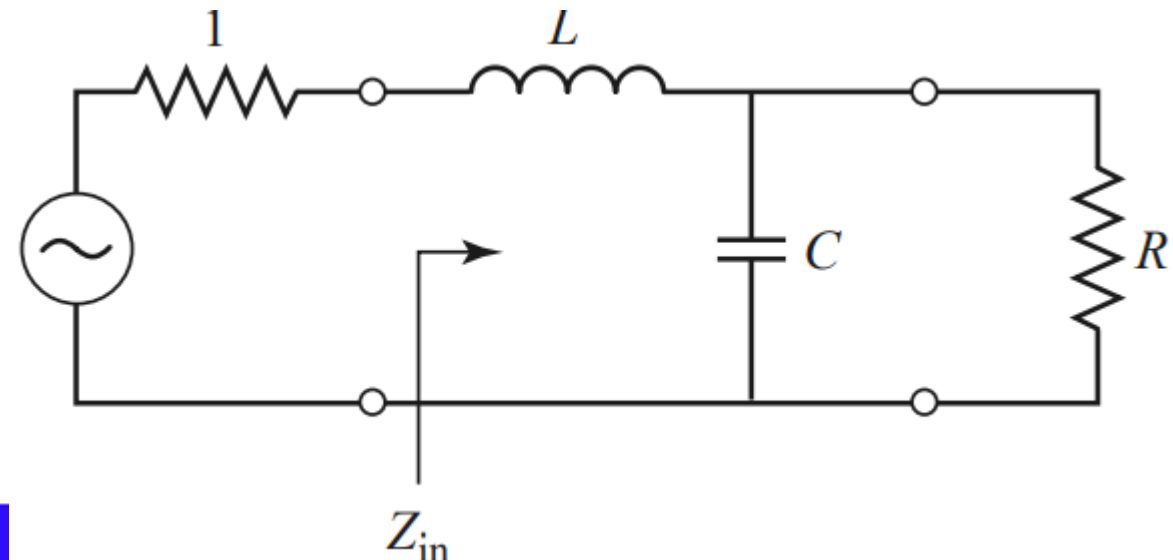4. Equal ripple Low Pass filter prototype (Chebyshev)

- $\omega_c = 1 \text{ rad/sec}$
Power loss ratio: $P_{LR} = 1 + k^2 T_N^2(\omega)$
 $1 + k^2$: ripple level in passband
- Chebyshev polynomial property:
- Filter will have the power loss ratio
 $P_{LR} = 1$ at $\omega = 0$ for N odd
 $P_{LR} = 1 + k^2$ at $\omega = 0$ for N even
- $k^2 = \frac{(1-R)^2}{4R}$ or
- $R = 1 + 2k^2 \pm 2k\sqrt{1 + k^2}$ for N even

$$T_N(0) = \begin{cases} 0 & \text{for } N \text{ odd,} \\ 1 & \text{for } N \text{ even,} \end{cases}$$



4. Equal ripple Low Pass filter prototype (Chebyshev): 0.5dB ripple

0.5 dB Ripple											
<i>N</i>	<i>g</i> ₁	<i>g</i> ₂	<i>g</i> ₃	<i>g</i> ₄	<i>g</i> ₅	<i>g</i> ₆	<i>g</i> ₇	<i>g</i> ₈	<i>g</i> ₉	<i>g</i> ₁₀	<i>g</i> ₁₁
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

4. Equal ripple Low Pass filter prototype (Chebyshev) : 3dB ripple

3.0 dB Ripple											
<i>N</i>	<i>g</i> ₁	<i>g</i> ₂	<i>g</i> ₃	<i>g</i> ₄	<i>g</i> ₅	<i>g</i> ₆	<i>g</i> ₇	<i>g</i> ₈	<i>g</i> ₉	<i>g</i> ₁₀	<i>g</i> ₁₁
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095


4. Equal ripple Low Pass filter prototype (Chebyshev)

- Table for designing equal ripple low pass filters with normalized source impedance


- Cutoff frequency $\omega'_c = \frac{1rad}{R_0 = g_0 = 1}$

The ladder circuits:

Prototype beginning with shunt element

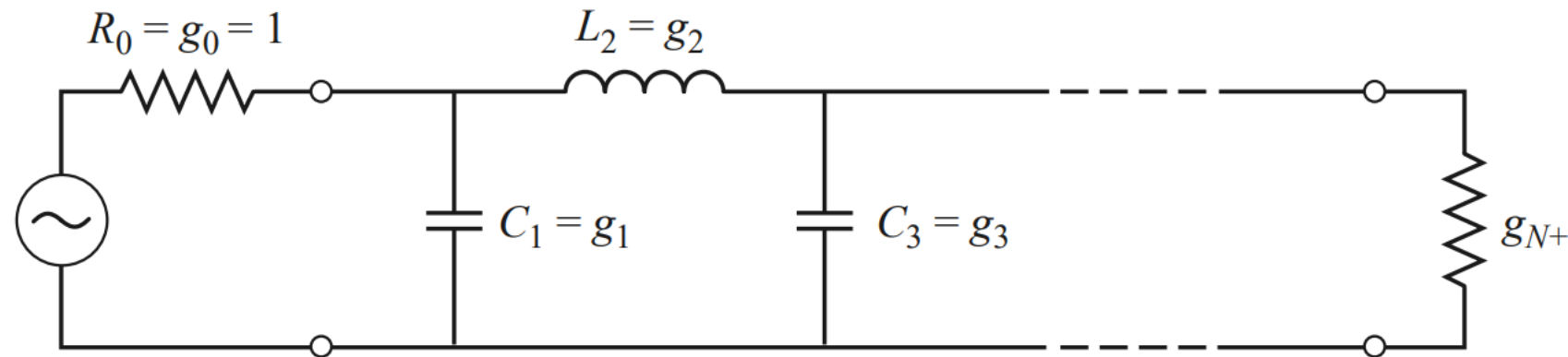

Prototype beginning with series element

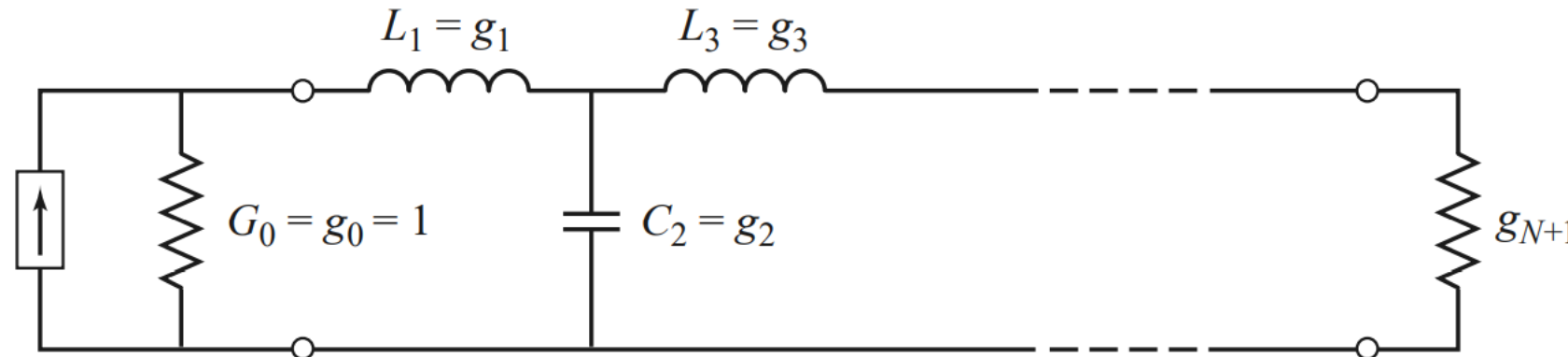


4. Equal ripple Low Pass filter prototype (Chebyshev)

- Table for designing equal ripple low pass filters with normalized source impedance
- Cutoff frequency $\omega'_c = \frac{1rad}{sec}$
The ladder circuits:
- The design data depends on specified passband ripple (0.5dB or 3dB)
- Notice: Load impedance $g_{N+1} \neq 1$ for even N

4. Equal ripple Low Pass filter prototype (Chebyshev)

- Table for designing equal ripple low pass filters with normalized source impedance
- Cutoff frequency $\omega'_c = \frac{1rad}{sec}$
The ladder circuits:
- The design data depends on specified passband ripple (0.5dB or 3dB)
- Notice: Load impedance $g_{N+1} \neq 1$ for even N
- If stopband attenuation is specified, the curves can be used to determine the necessary value of N for the ripples.

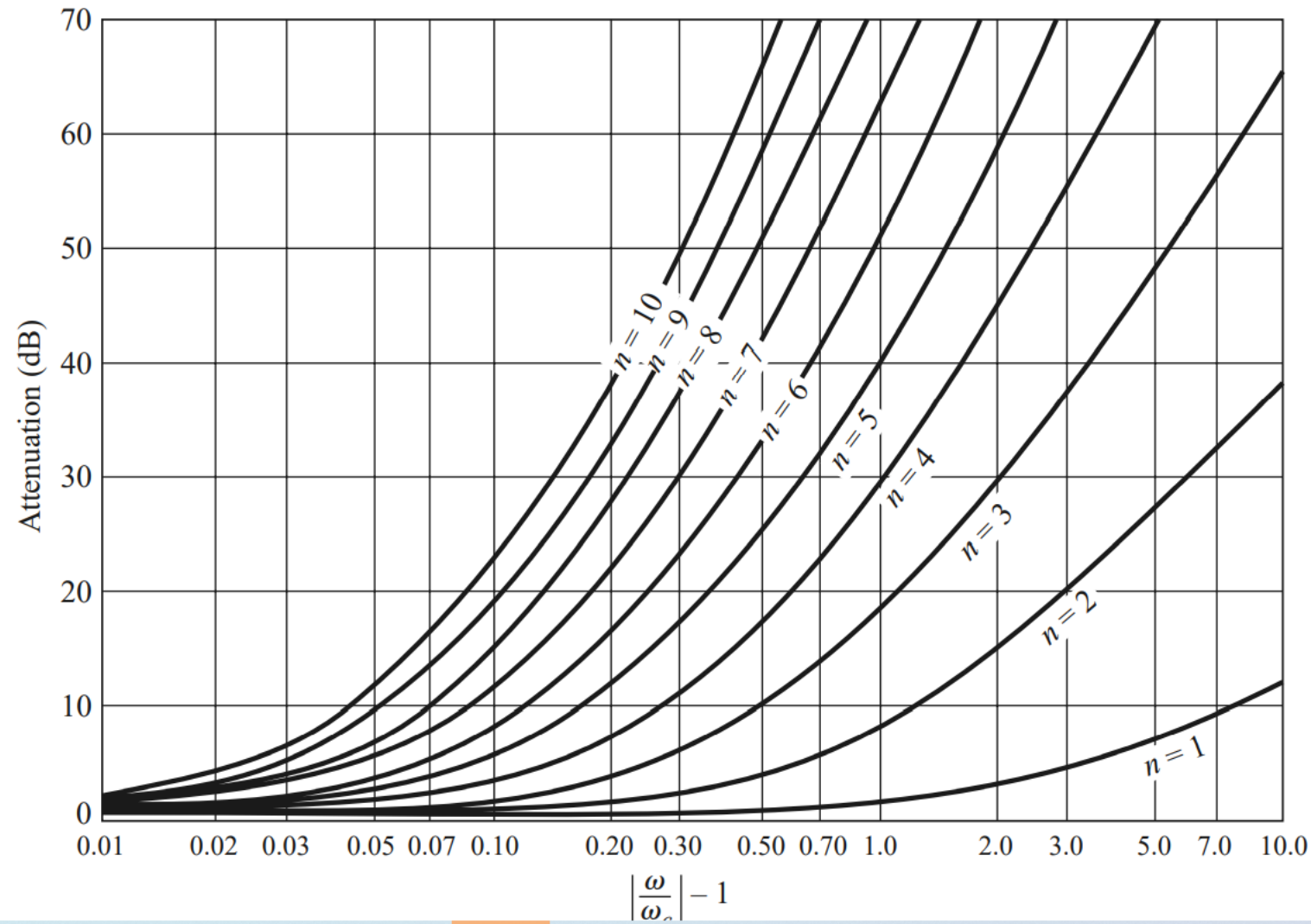4. Equal ripple Low Pass filter prototype (Chebyshev): 0.5dB ripple Attenuation



4. Equal ripple Low Pass filter prototype (Chebyshev) : 3dB ripple attenuation

