

6.7 Richards Transformation, Stepped impedance

Module:6 Microwave Passive circuits
Course: BECE305L – Antenna and Microwave Engineering

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: richards.stanislaus@vit.ac.in



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI

Module:6 Microwave Passive circuits 7 hours

- T junction and resistive power divider, Wilkinson power divider, branch line coupler (equal & unequal), Rat Race Coupler, Filter design: Low pass filter (Butterworth and Chebyshev) - Richards transformation and stepped impedance methods.
- Source of the contents: Pozar

4.1 Filter implementation: Problems

- The lumped-element filter designs discussed (binomial, chebychev) generally work well at low frequencies,
- but two problems arise at higher RF and microwave frequencies.
 - 1) lumped-element inductors and capacitors are generally available only for a limited range of values – are difficult to implement at microwave frequencies.

Distributed elements, such as open-circuited or short-circuited transmission line stubs, are often used to approximate ideal lumped elements.

- 2) At microwave frequencies the distances between filter components is not negligible.

4.1 Filter implementation: Solution


- The first problem is treated with **Richards' transformation**, used to convert lumped elements to transmission line sections.
- **Kuroda's identities** can then be used to physically separate filter elements by using transmission line sections.
- Because such additional transmission line sections do not affect the filter response, this type of design is called **redundant filter synthesis**.
improve the filter response; such non-redundant synthesis does not have a lumped-element counterpart.

4.2 Richards' Transformation $\Omega = \tan \beta \ell = \tan \left(\frac{\omega \ell}{v_p} \right)$

- Frequency ω is mapped to Ω plane
- Ω repeats itself at a period of $\frac{\omega \ell}{v_p} = 2\pi$
- This was introduced to synthesize LC network using open- and short-circuited transmission line stubs
- Impedance in Ω plane is obtained by replacing ω with $\Omega = \tan \beta \ell$
- Reactance of inductor: $jX_L = jL\Omega = jL \tan \beta \ell$
(Replace inductor with short circuited stub of length $\beta \ell$ and characteristic impedance L)
- Susceptance of capacitor: $jB_C = jC\Omega = jC \tan \beta \ell$
(Replace capacitor with open circuit stub of length $\beta \ell$ and characteristic impedance C)
- Unity filter impedance is assumed.

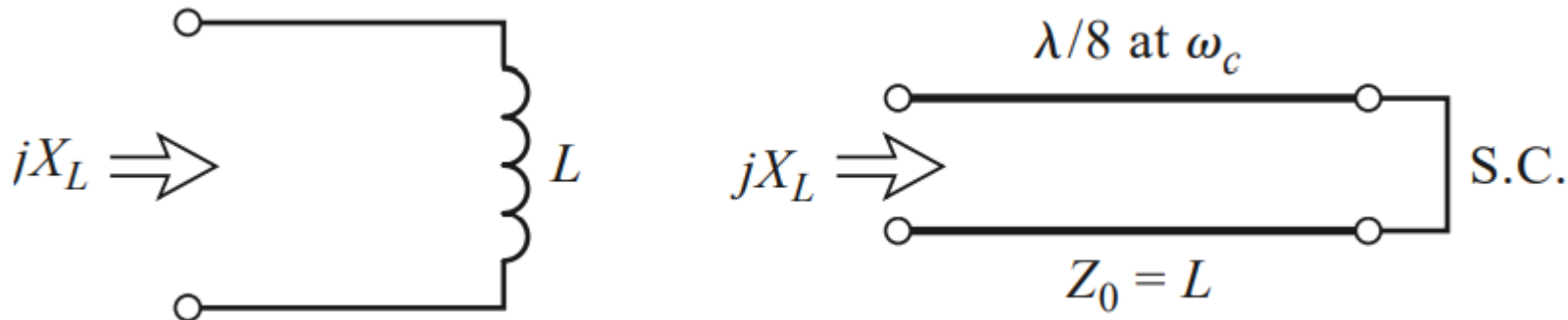
4.2 Richards' Transformation $\Omega = \tan \beta \ell = \tan \left(\frac{\omega \ell}{v_p} \right)$

- Reactance of inductor: $jX_L = jL\Omega = jL \tan \beta \ell$
(Replace inductor with short circuited stub of length $\beta \ell$ and characteristic impedance L)



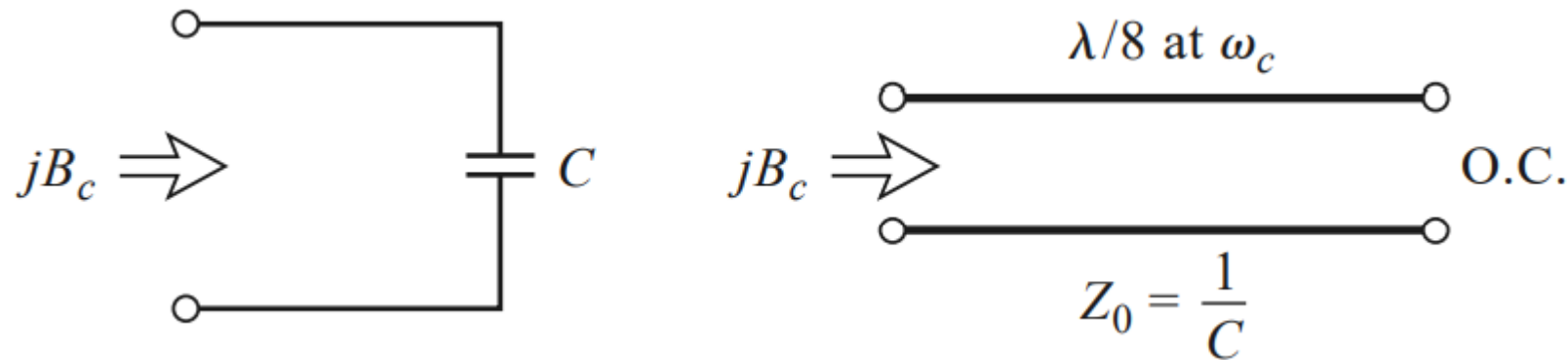4.2 Richards' Transformation $\Omega = \tan \beta \ell = \tan \left(\frac{\omega \ell}{v_p} \right)$

- Susceptance of capacitor: $jB_c = jC\Omega = jC \tan \beta \ell$
(Replace capacitor with open circuit stub of length $\beta \ell$ and characteristic impedance C)



4.2 Richards' Transformation $\Omega = \tan \beta \ell = \tan \left(\frac{\omega \ell}{v_p} \right)$

- At cut-off frequency ω_c in ω plane, with λ is wavelength at ω_c
 $\Omega = 1 = \tan \beta \ell$ which means $\beta \ell = \pi/4$ or the stub length of $\lambda/8$.
Electrical lengths of all the stubs are same.
Hence, they are known as **commensurate lines**.
- At frequency $\omega_0 = 2\omega_c$, the stub length will be $\lambda/4$ and attenuation pole occurs ($\beta \ell = \pi/2$ and $\tan \beta \ell = \infty$)
- The response away from ω_c will be different and not same.
- In addition, the response will be periodic in frequency, repeating every $4\omega_c$.

4.3 Kuroda's identities


- The four Kuroda identities use redundant transmission line sections to achieve a more practical microwave filter implementation by performing any of the following operations
 - Physically separate transmission line stubs
 - Transform series stubs into shunt stubs, or Transform shunt stubs into series stubs
 - Change impractical characteristic impedances into more realizable values
 - The additional transmission line sections are called unit elements and are $\lambda/8$ long at ωc ;
- The unit elements are thus commensurate with the stubs used to implement the inductors and capacitors of the prototype design

4.3 Kuroda's identities


- Each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\lambda/8$ at ω_c)
- The **inductors** and **capacitors** represent **short-circuit stub** and **open-circuit stubs** respectively.

$$n^2 = 1 + Z_2/Z_1$$

1

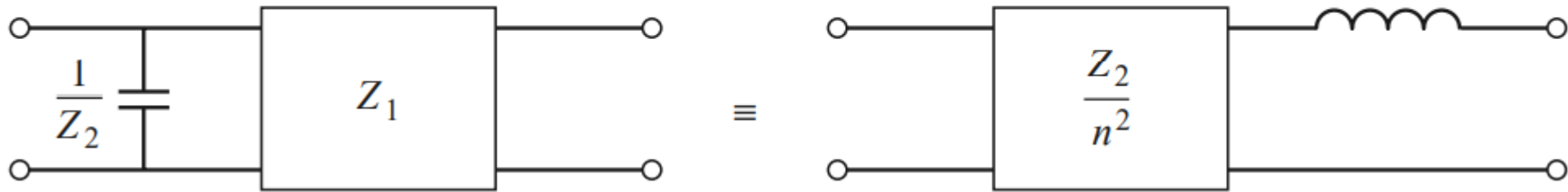


2

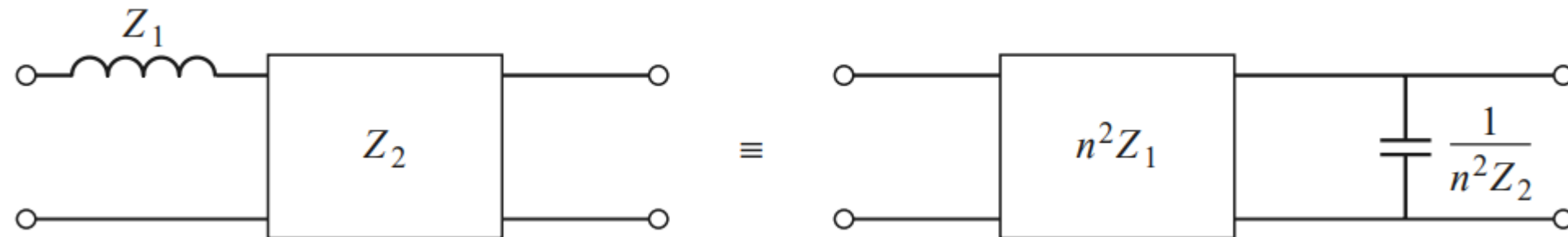

4.3 Kuroda's identities


- Each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\lambda/8$ at ω_c)
- The **inductors** and **capacitors** represent **short-circuit stub** and **open-circuit stubs** respectively.

$$n^2 = 1 + Z_2/Z_1$$

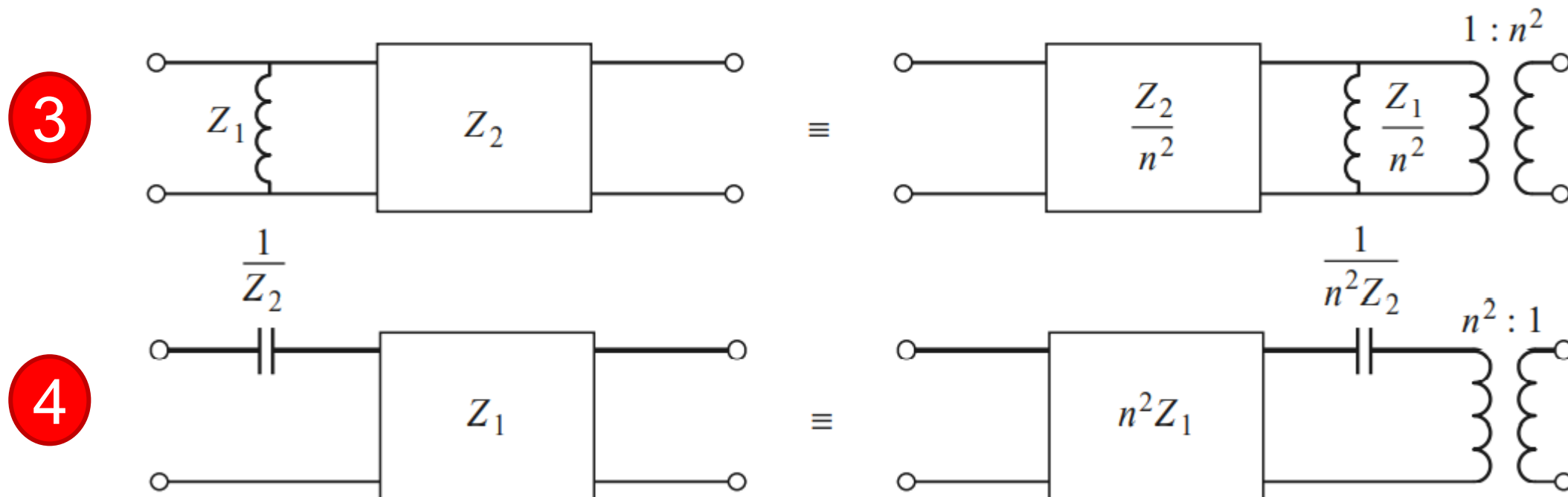

4.3 Kuroda's identity - 1

1

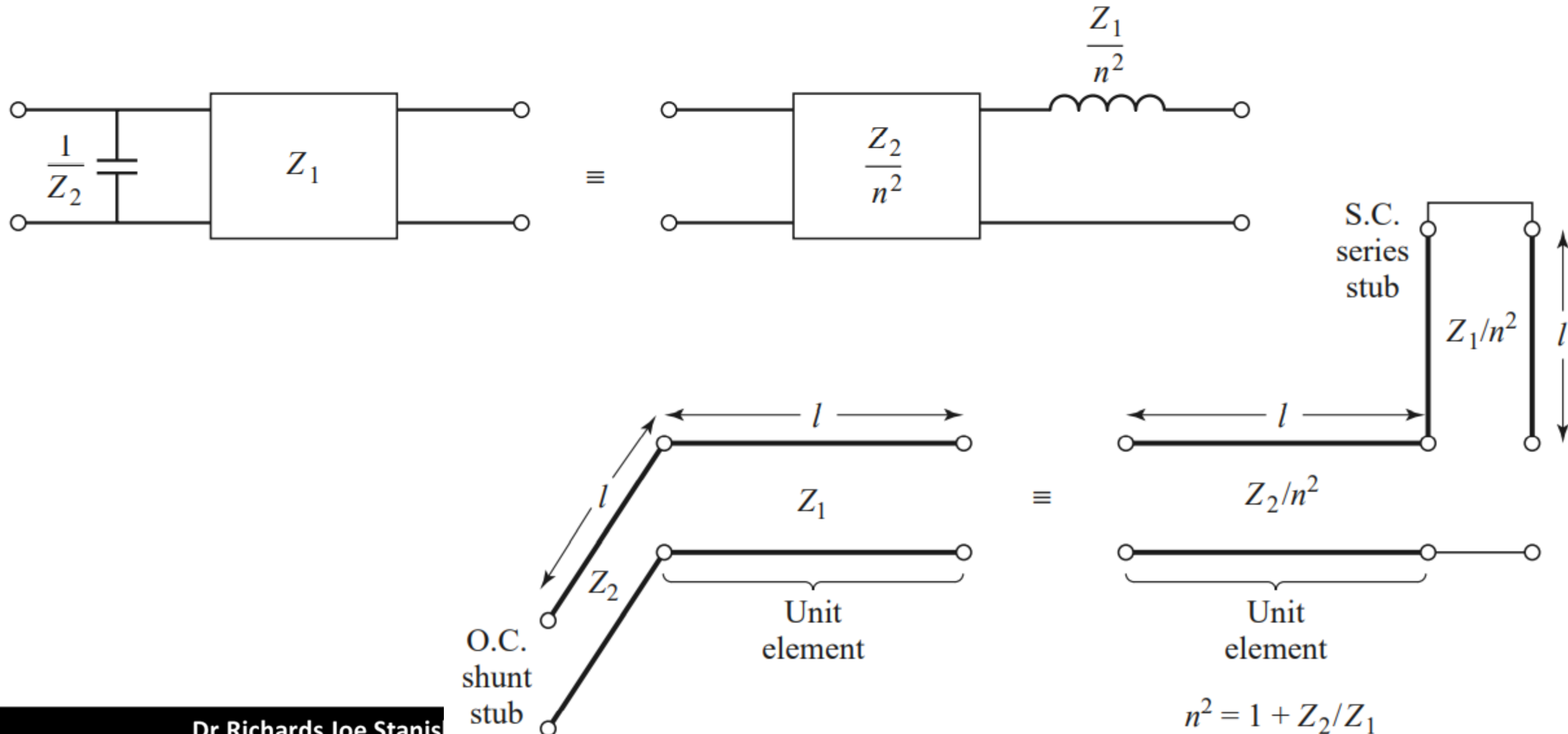

5. Stepped impedance LPF

- A relatively easy way to implement low-pass filters in microstrip or stripline: use alternating sections of very high and very low characteristic impedance lines. (**stepped-impedance, or hi-Z, low-Z filters**)
- Popular because they are **easier to design** and **take up less space** than a similar low-pass filter using stubs.
- Because of the approximations involved, however, their electrical performance is not as good, so the use of such filters is usually limited to applications where a sharp cutoff is not required (for instance, in rejecting out-of-band mixer products).

5. Stepped impedance LPF

- Approximate equivalent circuits for short sections of transmission lines.




Used for $\beta l \ll \pi/2$:

Equivalent circuit for small βl and large Z_0

$$\beta l = \frac{LR_0}{Z_h} \quad (\text{inductor})$$

Equivalent circuit for small βl and small Z_0

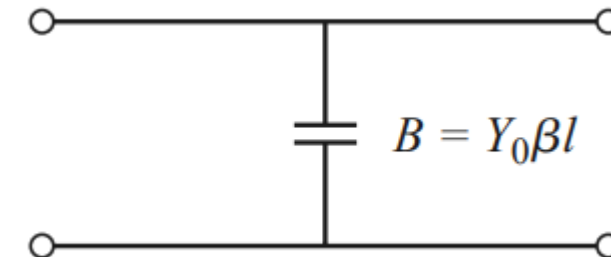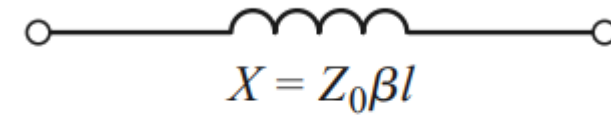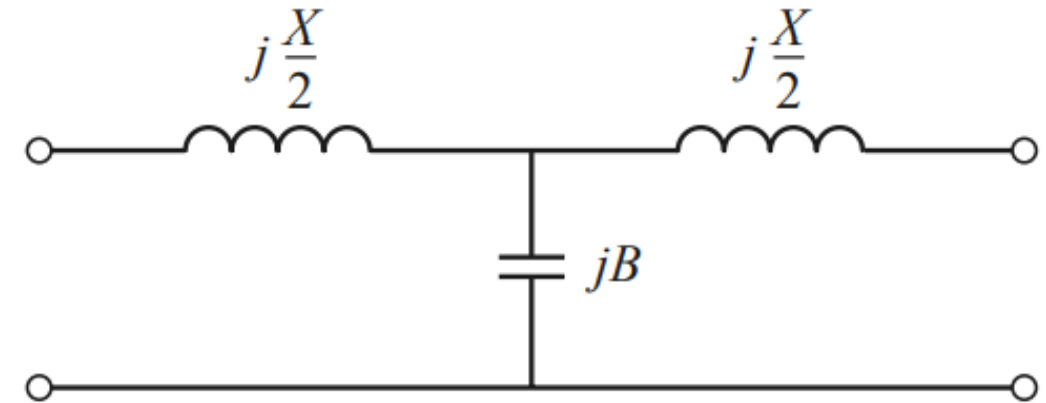
$$\beta l = \frac{CZ_\ell}{R_0} \quad (\text{capacitor}),$$




Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.

Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.
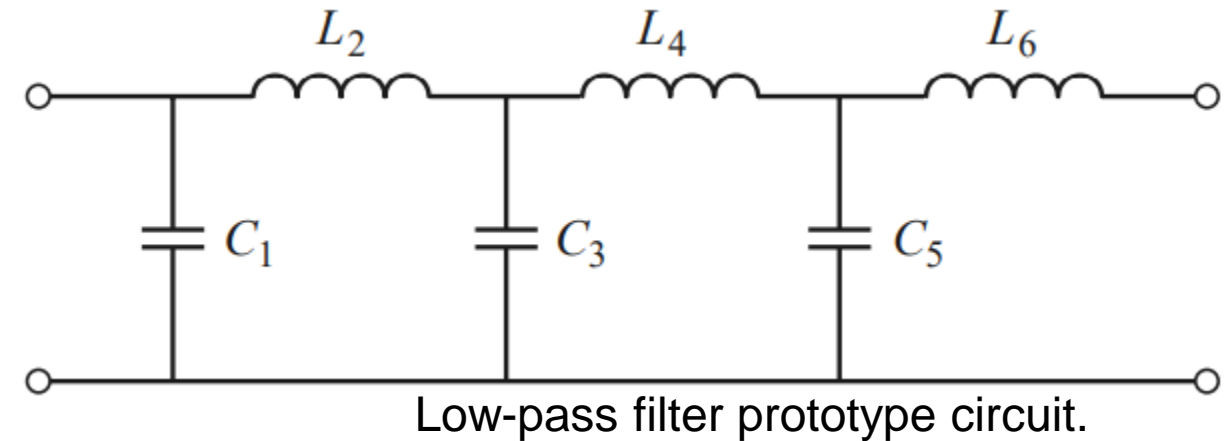
$$\frac{\omega}{\omega_c} - 1 = \frac{4.0}{2.5} - 1 = 0.6;$$



Stepped impedance implementation

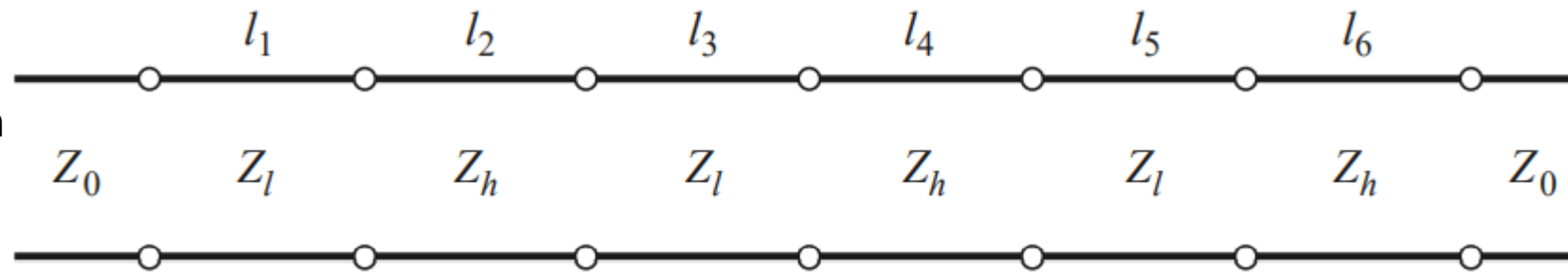


Microstrip layout of the final filter



Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.

$$\frac{\omega}{\omega_c} - 1 = \frac{4.0}{2.5} - 1 = 0.6;$$

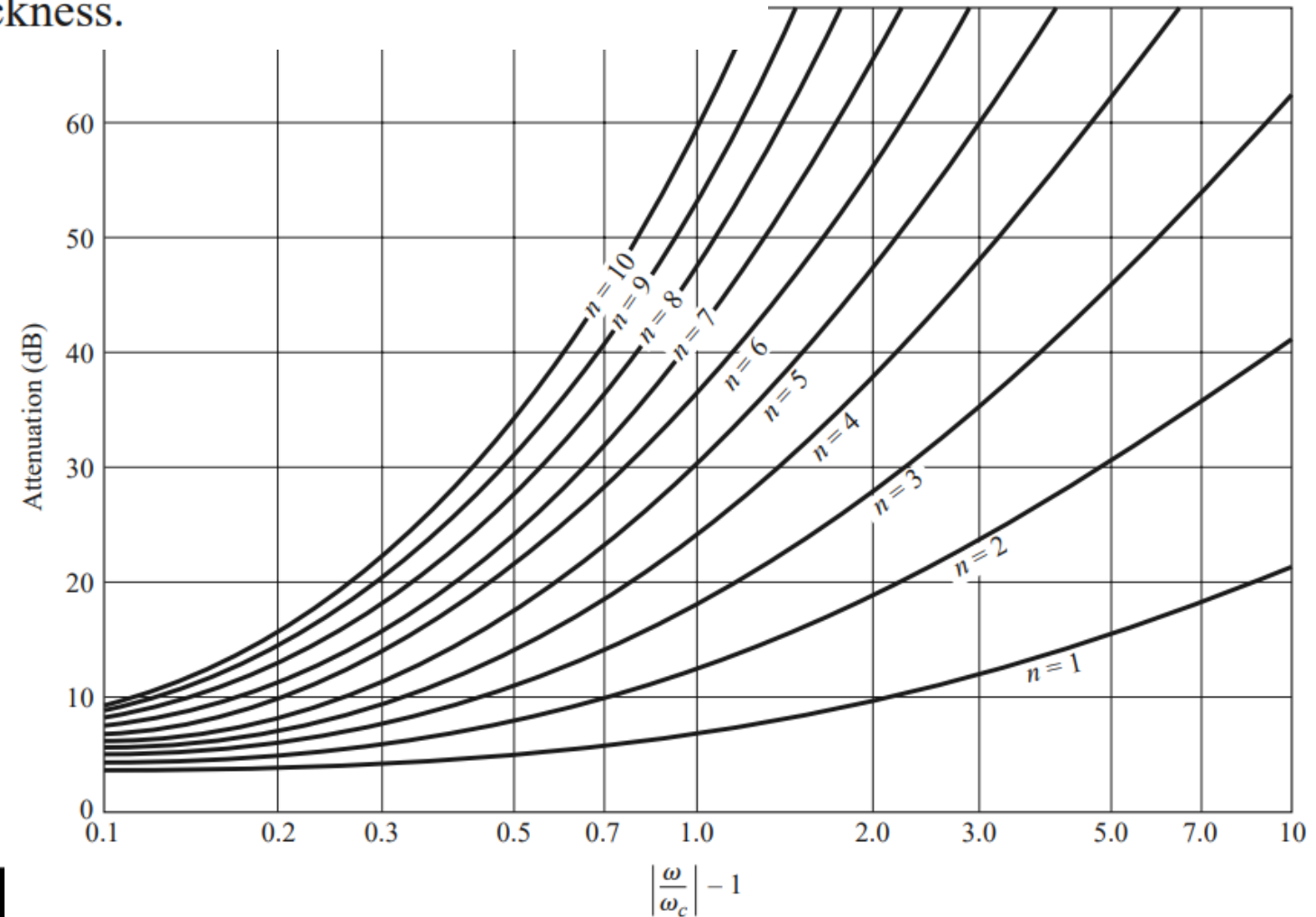$N = 6$ should give the required attenuation at 4.0 GHz



Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.

$$\frac{\omega}{\omega_c} - 1 = \frac{4.0}{2.5} - 1 = 0.6$$

$N = 6$ should give the required attenuation at 4.0 GHz

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.

$$\frac{\omega}{\omega_c} - 1 = \frac{4.0}{2.5} - 1 = 0.6$$

$N = 6$ should give the required attenuation at 4.0 GHz

$$g_1 = 0.517 = C_1,$$

$$g_2 = 1.414 = L_2,$$

$$g_3 = 1.932 = C_3,$$

$$g_4 = 1.932 = L_4,$$

$$g_5 = 1.414 = C_5,$$

$$g_6 = 0.517 = L_6.$$

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Design a stepped-impedance low-pass filter having a maximally flat response and a cutoff frequency of 2.5 GHz. It is desired to have more than 20 dB insertion loss at 4 GHz. The filter impedance is $50\ \Omega$; the highest practical line impedance is $120\ \Omega$, and the lowest is $20\ \Omega$. Consider the effect of losses when this filter is implemented with a microstrip substrate having $d = 0.158\text{ cm}$, $\epsilon_r = 4.2$, $\tan \delta = 0.02$, and copper conductors of 0.5 mil thickness.

$$\frac{\omega}{\omega_c} - 1 = \frac{4.0}{2.5} - 1 = 0.6;$$

N = 6 should give the required attenuation at 4.0 GHz

$$g_1 = 0.517 = C_1,$$

$$g_2 = 1.414 = L_2,$$

$$g_3 = 1.932 = C_3,$$

$$g_4 = 1.932 = L_4,$$

$$g_5 = 1.414 = C_5,$$

$$g_6 = 0.517 = L_6.$$

Section	$Z_i = Z_\ell \text{ or } Z_h (\Omega)$	$\beta \ell_i \text{ (deg)}$	$W_i \text{ (mm)}$	$\ell_i \text{ (mm)}$
1	20	11.8	11.3	2.05
2	120	33.8	0.428	6.63
3	20	44.3	11.3	7.69
4	120	46.1	0.428	9.04
5	20	32.4	11.3	5.63
6	120	12.3	0.428	2.41

$$\beta \ell = \frac{L R_0}{Z_h} \quad (\text{inductor}) \quad \beta \ell = \frac{C Z_\ell}{R_0} \quad (\text{capacitor}),$$

- Very important

