

## 6.3 Quadrature Hybrid or Branchline Coupler

**Module:6 Microwave Passive circuits**  
**Course: BECE305L – Antenna and Microwave Engineering**

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: [richards.stanislaus@vit.ac.in](mailto:richards.stanislaus@vit.ac.in)




**VIT<sup>®</sup>**  
**Vellore Institute of Technology**  
(Deemed to be University under section 3 of UGC Act, 1956)  
CHENNAI

# Module:6      Microwave Passive circuits 7 hours

- T junction and resistive power divider, Wilkinson power divider, branch line coupler (equal & unequal), Rat Race Coupler, Filter design: Low pass filter (Butterworth and Chebyshev) - Richards transformation and stepped impedance methods.
- .
- Source of the contents: Pozar
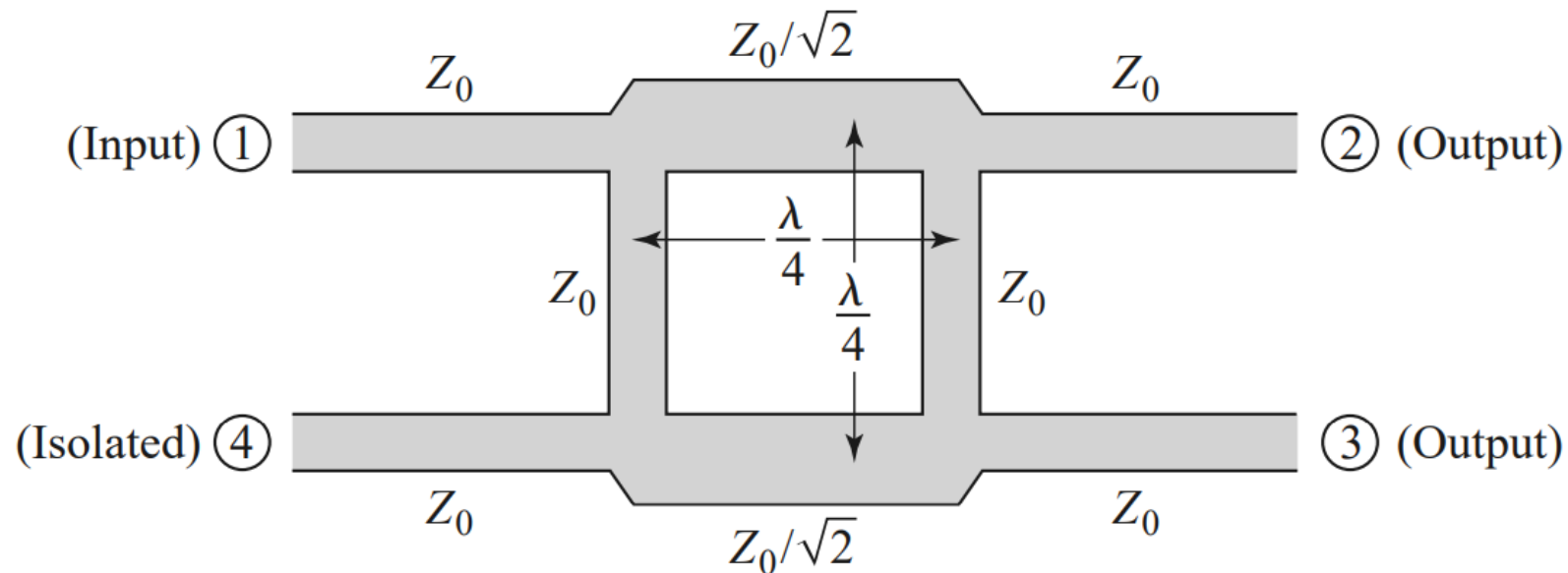
# 8.1 Introduction to Quadrature hybrids

- Quadrature hybrids are  $3dB$  directional couplers  
With  $90^\circ$  phase difference in outputs of the through and coupled arms.
- Applications: Microstrip lines or Stripline forms
- Also known as Branch-line hybrid



## 8.2 Basic operation of Quadrature hybrids

- Power entering port 1  
Even division of power between ports 2 and 3  
Phase shift between two ports:  $90^\circ$
- Port 4 is isolated from port 1.

• S matrix:  $[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$


High degree of Symmetry:

Any port can be input,

**Isolated port will be on the same side**


**Output ports on the opposite sides**

- Each row – transposition of other row

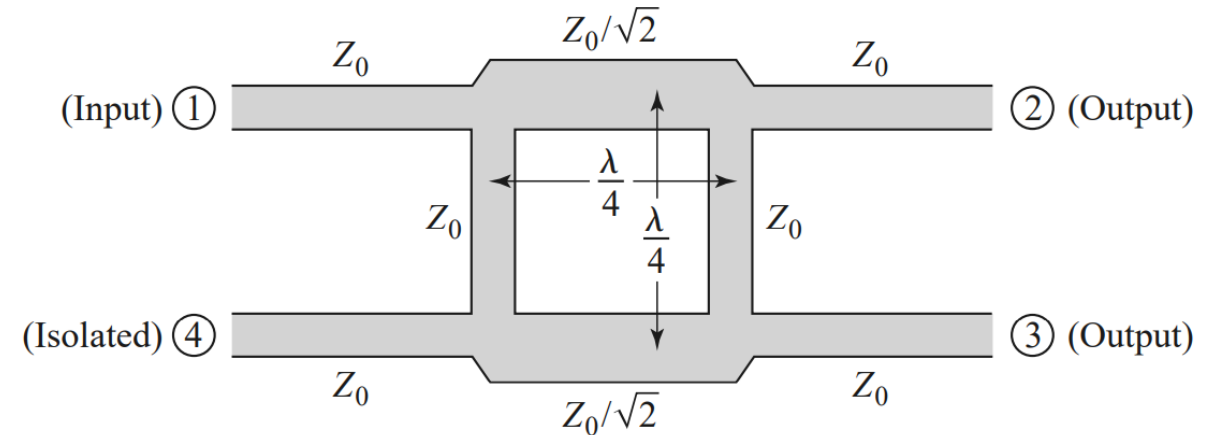


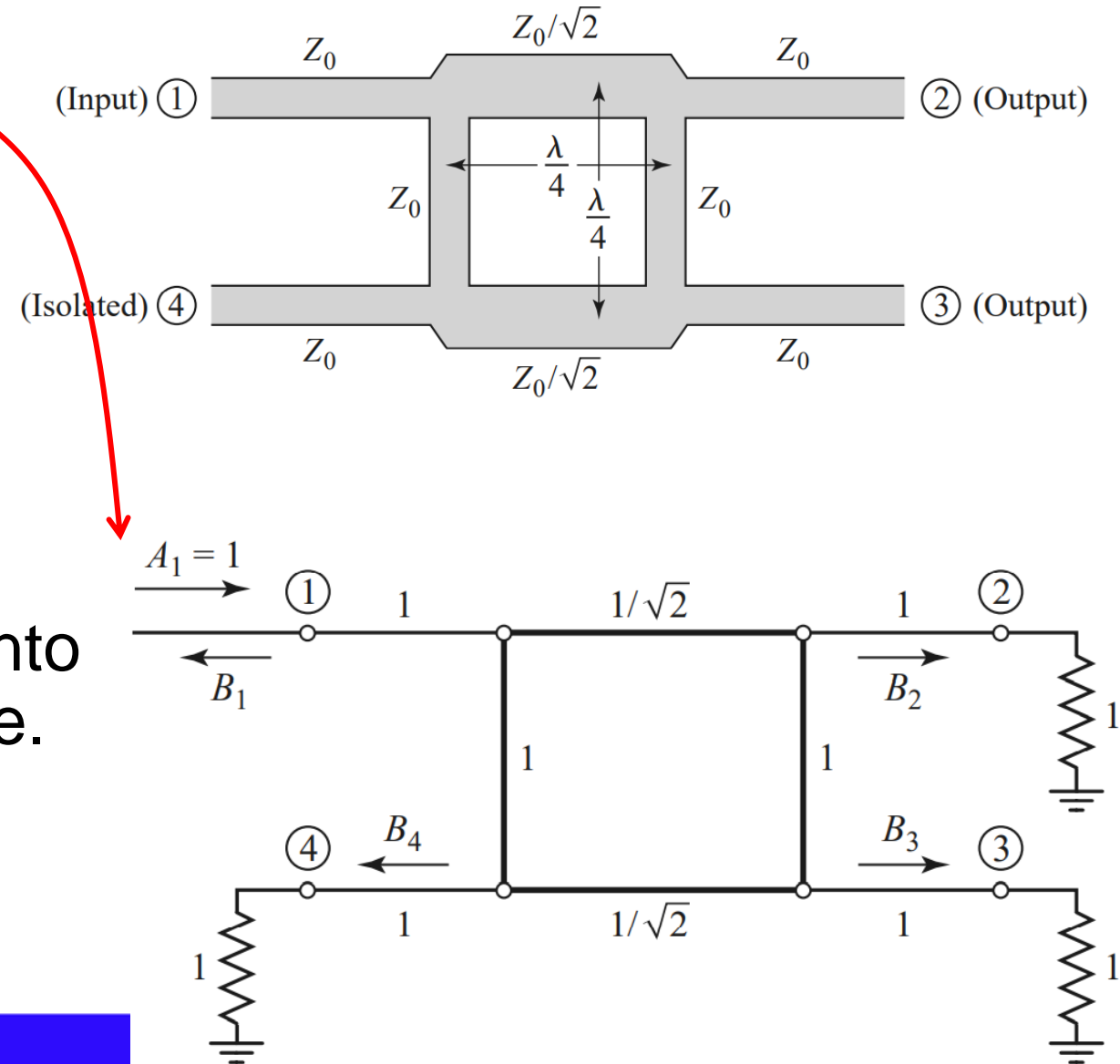
## 8.3 Even-Odd mode analysis

- Schematic in normalized form
- Each line : transmission line with indicated characteristic impedance normalized to  $Z_0$
- Return ground path not indicated
- Wave of unit amplitude  $A_1 = 1$  is incident at port 1
- This will be modified(decomposed) into superposition of Even and Odd mode.




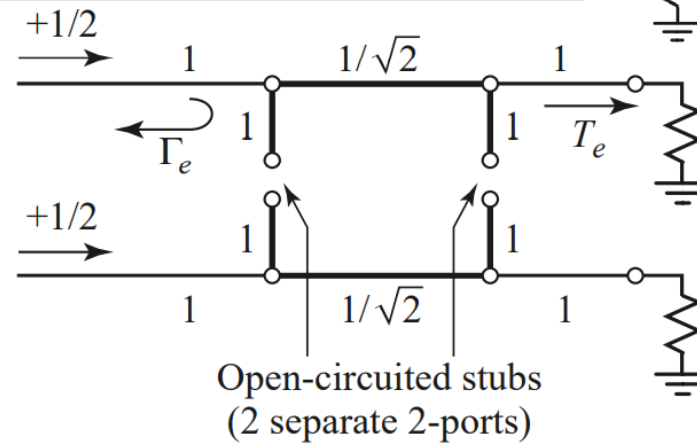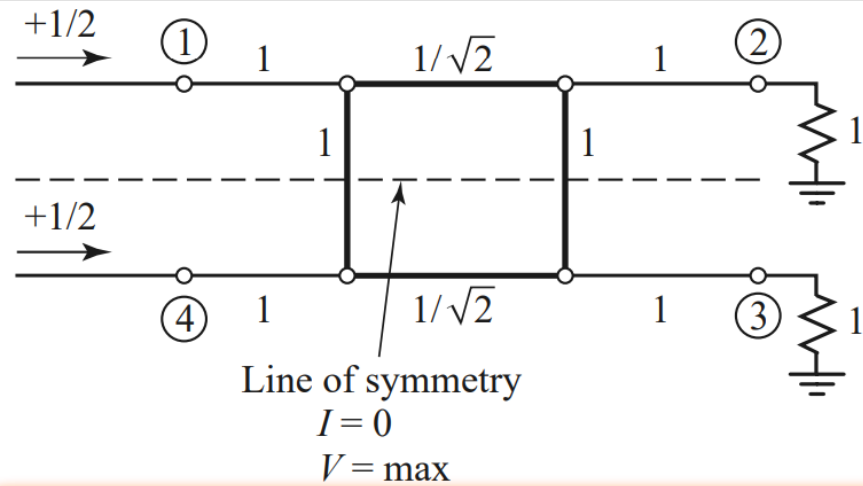
# 8.3 Even-Odd mode analysis


Modified(decomposed) into superposition of Even and Odd modes.



Even mode  
excitation




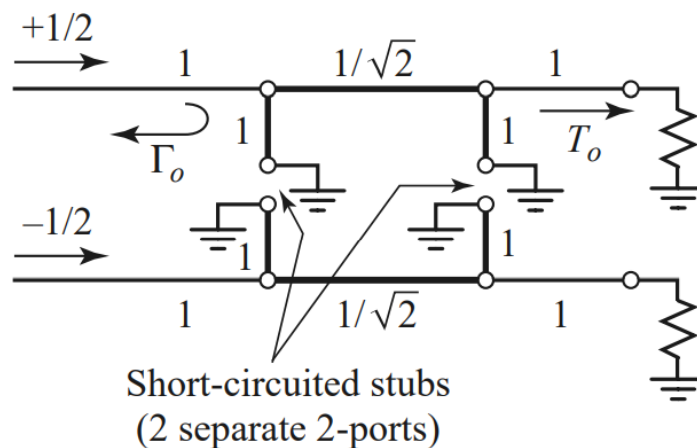
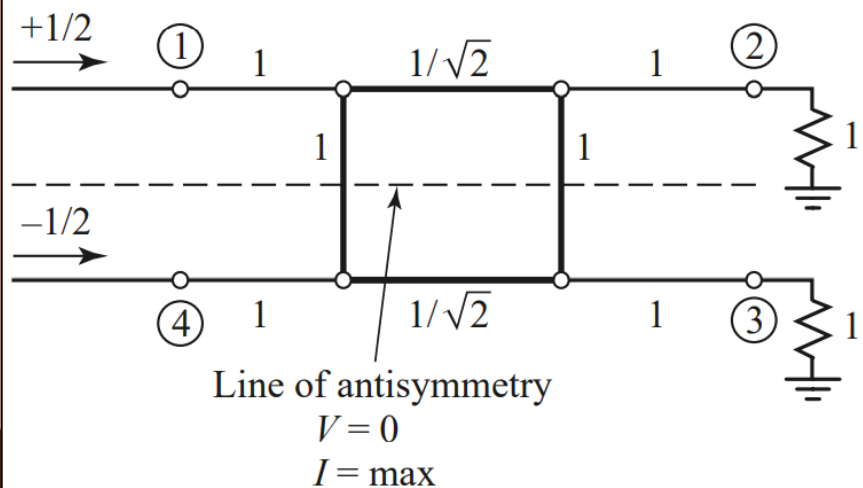


Odd mode  
excitation

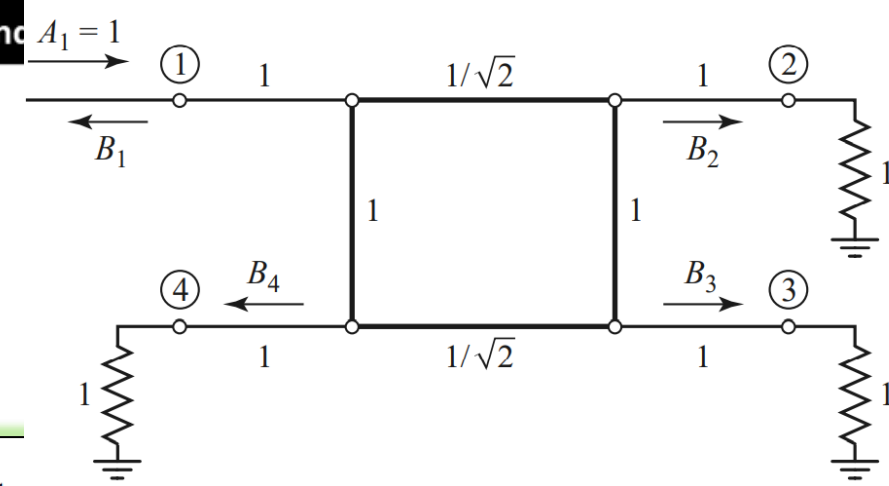
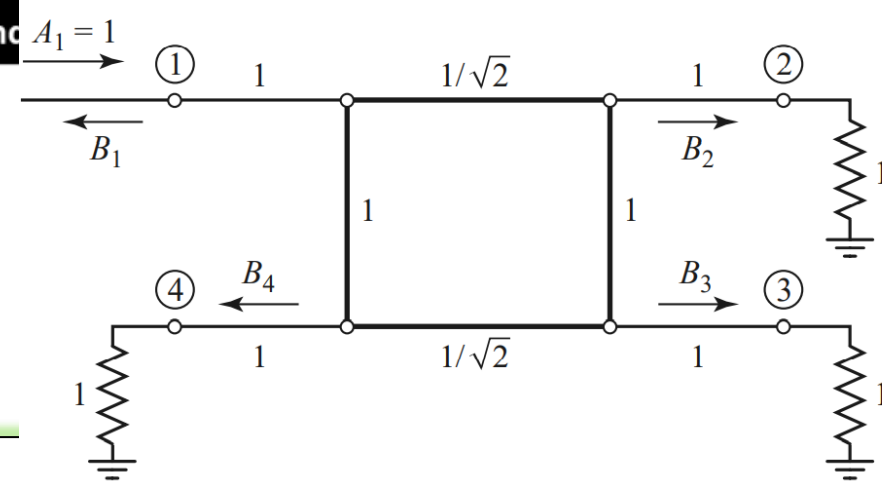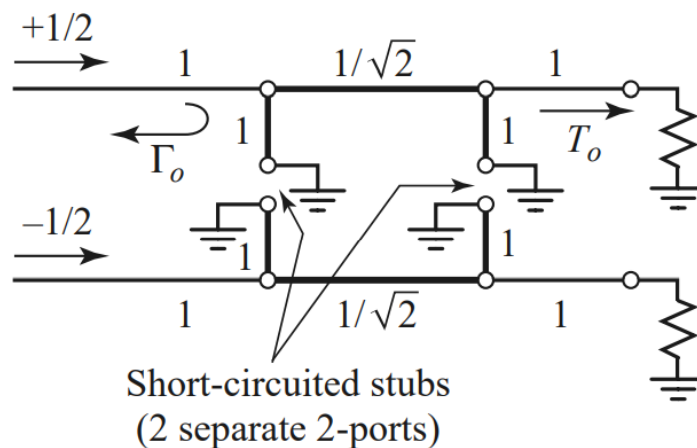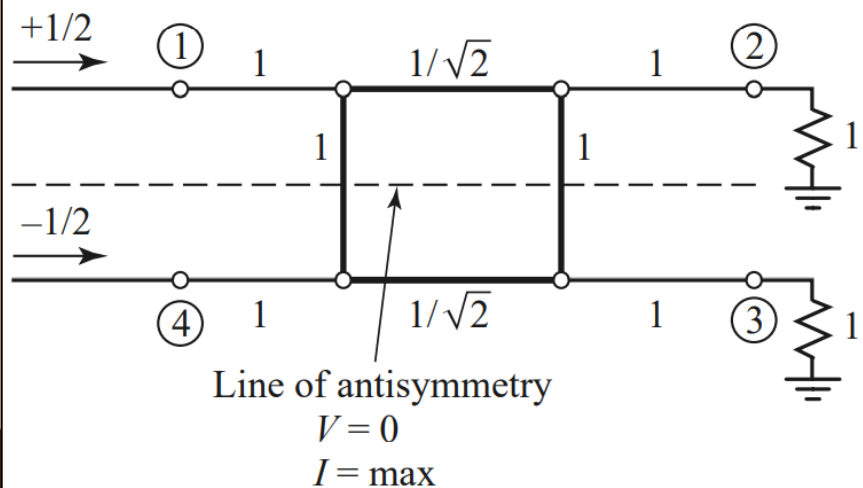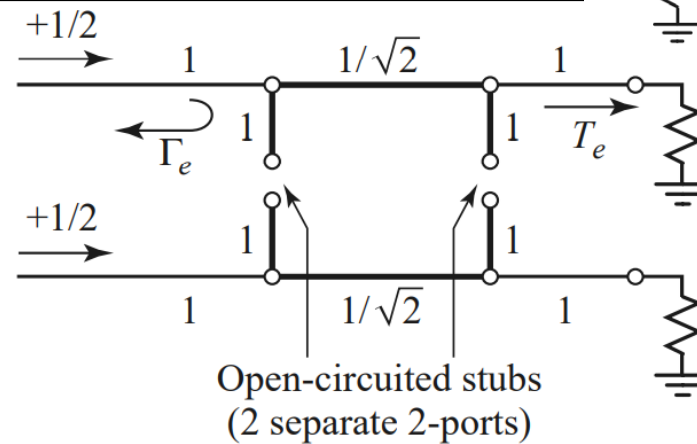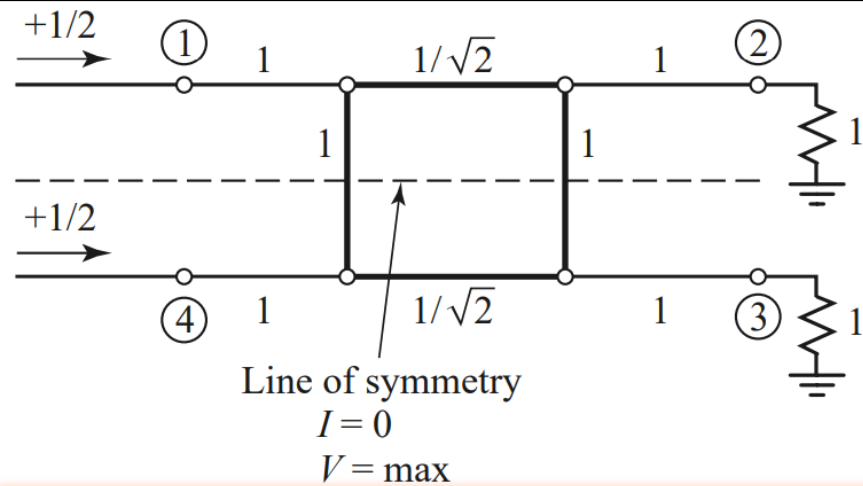
# 8.3 Even-Odd mode analysis

$\Gamma_{e,o}$  and  $T_{e,o}$ : Even and odd mode reflection and transmission coefficients.



*Emerging waves at each port*

$$B_1 = \frac{1}{2} \Gamma_e + \frac{1}{2} \Gamma_o$$

$$B_2 = \frac{1}{2} T_e + \frac{1}{2} T_o$$

$$B_3 = \frac{1}{2} T_e - \frac{1}{2} T_o$$

$$B_4 = \frac{1}{2} \Gamma_e - \frac{1}{2} \Gamma_o$$

## 8.3 Even-Odd mode analysis

$\Gamma_{e,o}$  and  $T_{e,o}$ : Even and odd mode reflection and transmission coefficients.

For  $\lambda/4$  transmission line between two neighbouring ports,

$$\Gamma_e = 0, T_e = -\frac{1}{\sqrt{2}}(1 + j)$$


$$\Gamma_o = 0, T_o = \frac{1}{\sqrt{2}}(1 - j)$$

$$B_1 = 0, \text{ Matched port 1}$$

$$B_2 = -\frac{j}{\sqrt{2}} \text{ (Half power } -90^\circ \text{ phase shift from port 1 to 2)}$$

$$B_3 = -\frac{1}{\sqrt{2}} \text{ (Half power } -180^\circ \text{ phase shift from port 1 to 3)}$$

$$B_4 = 0 \text{ (No power to port 4)}$$

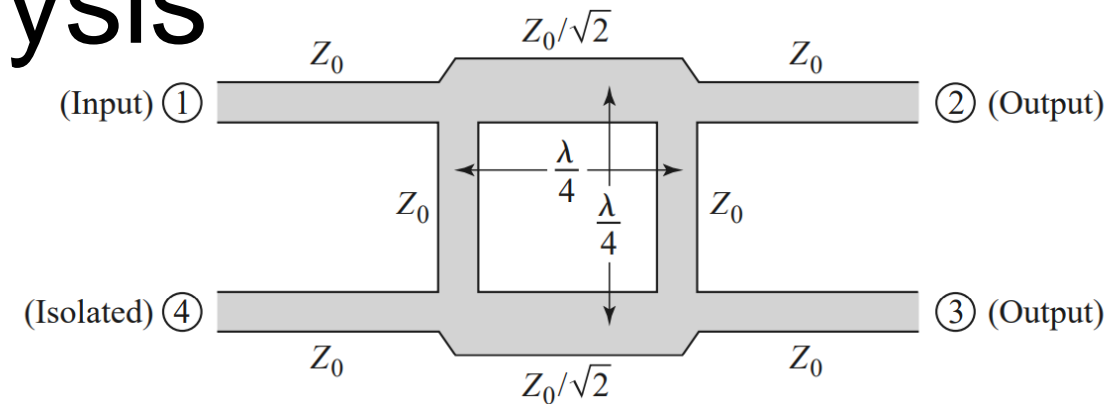

*Emerging waves at each port*

$$B_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o$$

$$B_2 = \frac{1}{2}T_e + \frac{1}{2}T_o$$


$$B_3 = \frac{1}{2}T_e - \frac{1}{2}T_o$$

$$B_4 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$


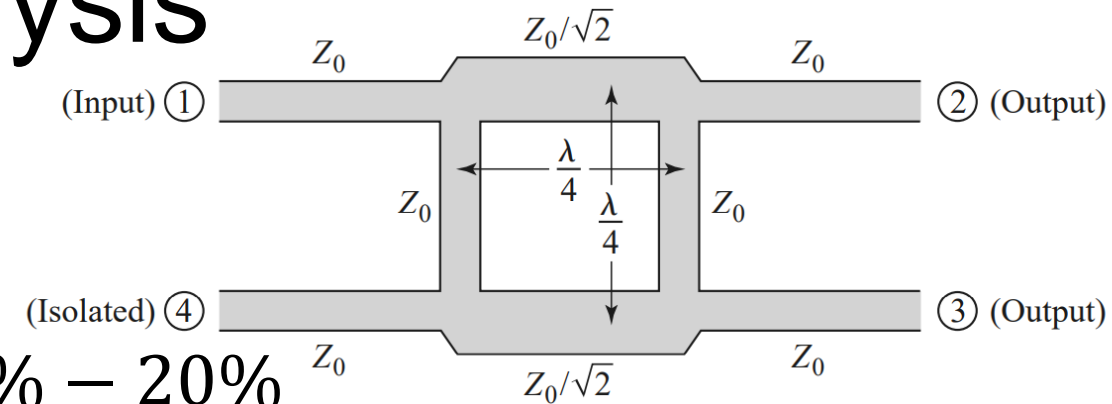
## 8.3 Even-Odd mode analysis

- In practice,  
Quarter-wave length requirement  
Bandwidth of branch-line is limited to 10% – 20%
- Further increase can be possible by  
Multi-section matching transformers  
Multi-hole directional couplers  
Cascade of multi-sections
- Unequal power division is also possible



## 8.4 Problem on Quadrature Hybrid

Design a  $50\Omega$  branchline quadrature hybrid junction

- Lines are  $\lambda/4$  at design frequency  $f_0$   
Branchline impedances are :  $\frac{Z_0}{\sqrt{2}} = \frac{50}{\sqrt{2}} = 35.4\Omega$