
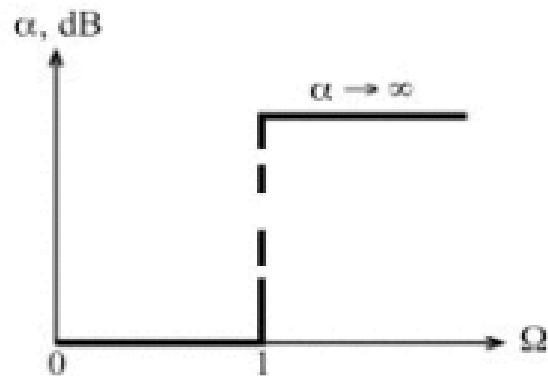


# Filter Design


# Filter Configuration

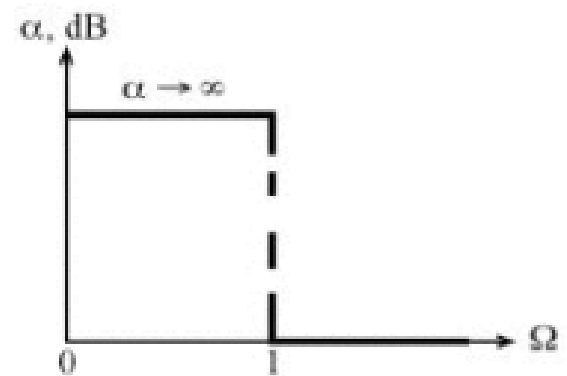


Low-pass filter



High-pass filter

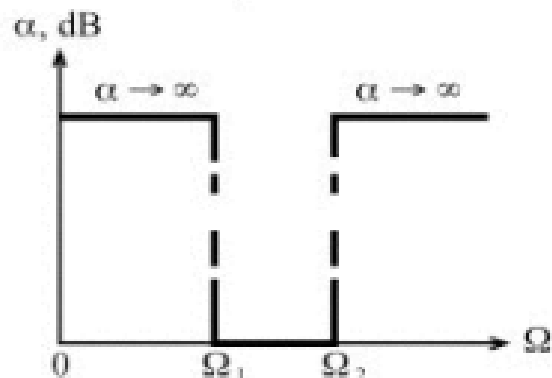

Bandpass filter

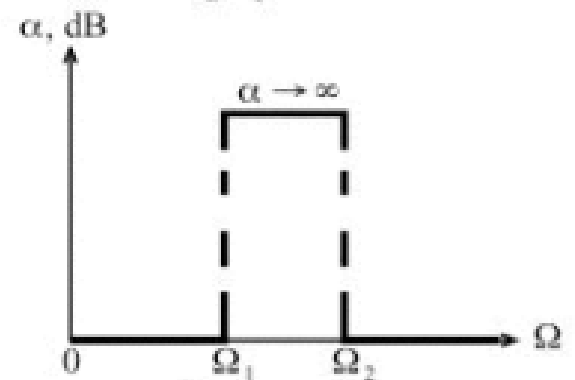

Bandstop filter

$$\Omega = \frac{\omega}{\omega_c}$$

where  $\omega_c$  is defined as the cutoff frequency for low-pass and high-pass filters and the center frequency for bandpass and bandstop filters.

# Filter Frequency Response

A perfect filter would have zero insertion loss in the pass band, infinite attenuation in the stop band, and a linear phase response (to avoid signal distortion) in the pass band.

## Binomial


- easy to implement, monotonic profile, requires numerous elements

## Chebyshev

- equal amplitude variations, steeper profile than Butterworth
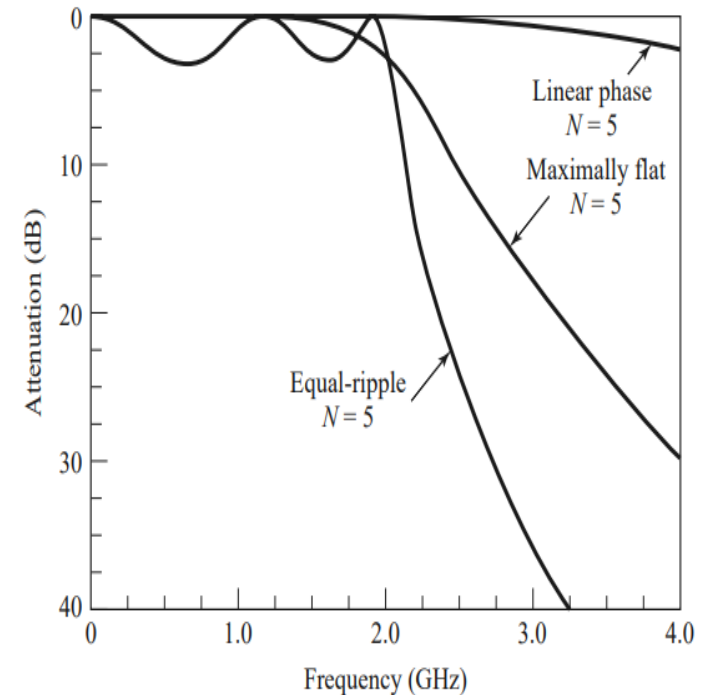
## Elliptic


- amplitude varies in both stopband and passband, steepest profile, complicated design




# Filter Definitions

- **Insertion loss** - how much power is lost in going through the filter.  $IL = 10 \log P_{in}/P_L$   
IL quantity is the reciprocal of  $|S_{12}|^2$
- **Ripple** - the flatness of the signal in the passband.
- **Bandwidth** - the width of the passband


# Filter Design

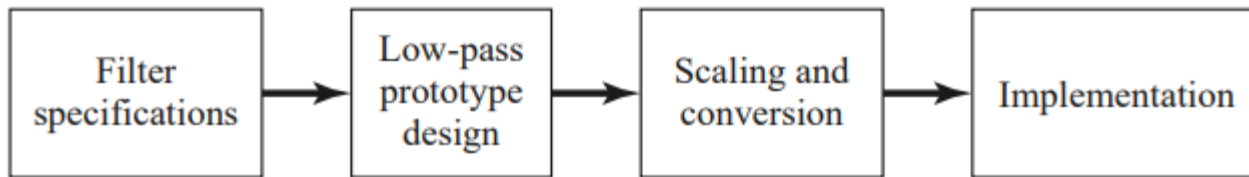

## Filter Design Process

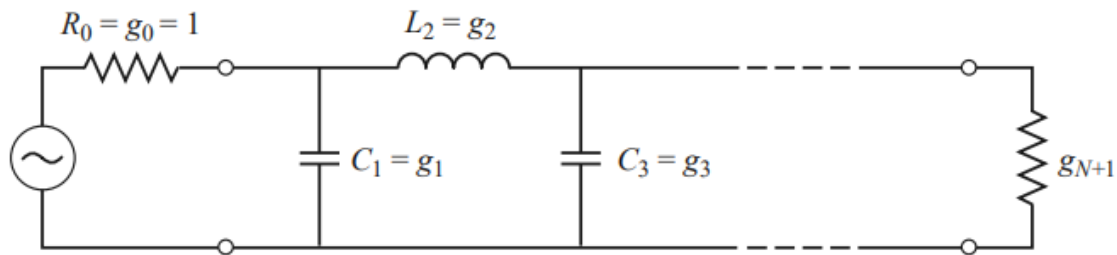

(a)

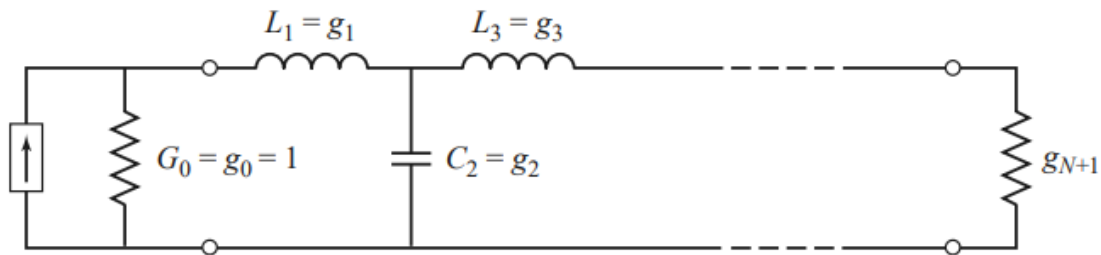

## Filter Design Prototype

# Maximally Flat LPF element Values

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ ,  $N = 1$  to 10)

$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

# Equiripple Filter element Values (0.5 dB

ripple)

**TABLE 8.4** Element Values for Equal-Ripple Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ ,  $N = 1$  to 10, 0.5 dB and 3.0 dB ripple)

$N$	0.5 dB Ripple										
	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

# Equiripple Filter element Values (3 dB Ripple)

3.0 dB Ripple											
$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.



# Filter Design by Richards Transformation and Kuroda's Identity

## Lumped element filter

- difficult to implement at MW frequency, as they are available at limited range
- Distance between filter components are not negligible



## Richards Transformation

- Lumped element converted to transmission line section

## Kuroda's identity




- Separate filter elements using transmission line structure
- Doesnot affect filter response, hence known as redundant filter
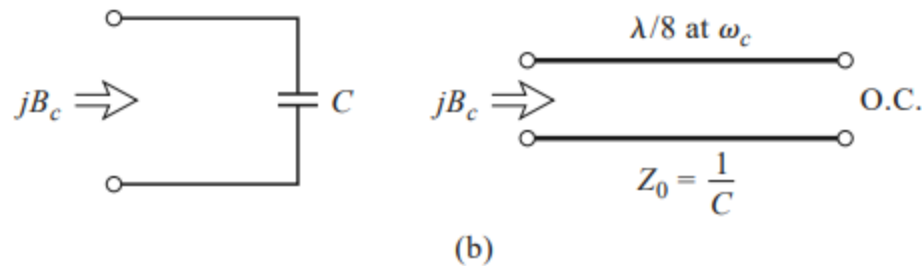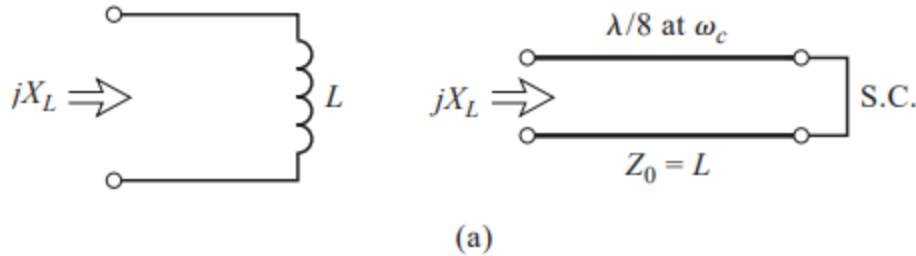
# Lumped element implementation in Transmissionline





**Richards' transformation.** (a) For an inductor to a short-circuited stub. (b) For a capacitor to an open-circuited stub.

## Kuroda's identity

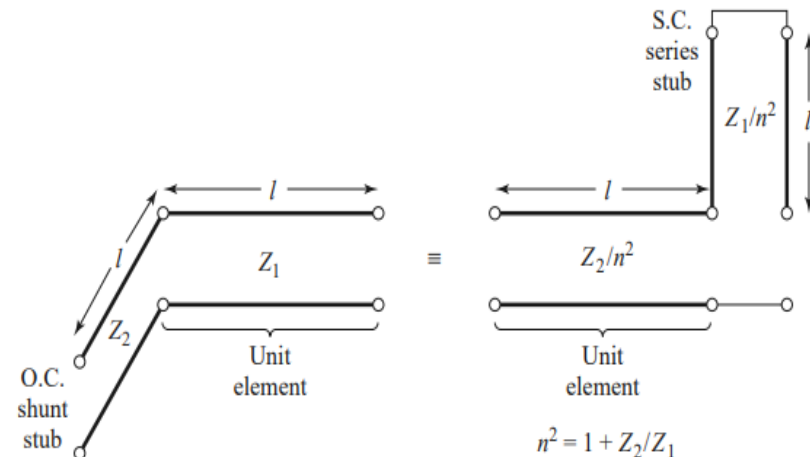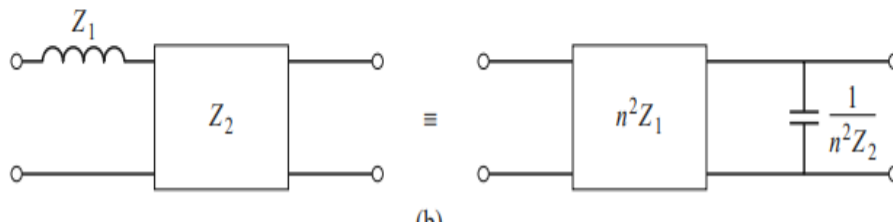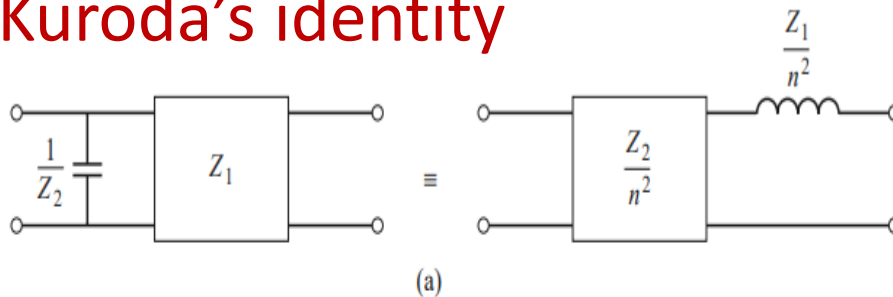

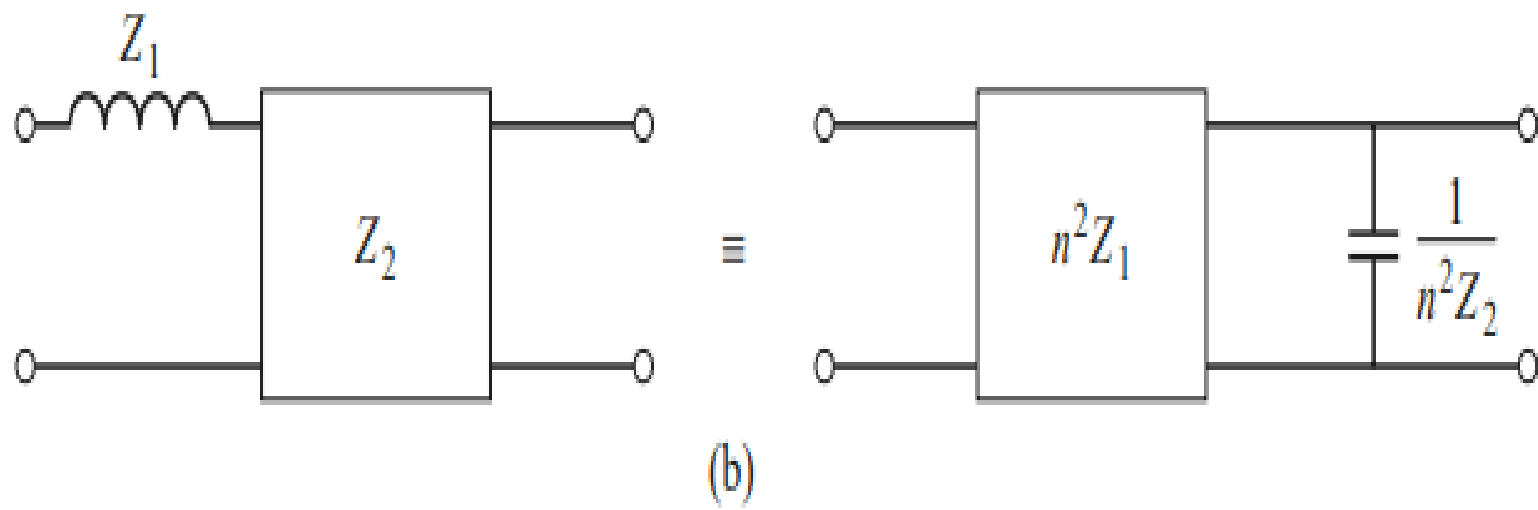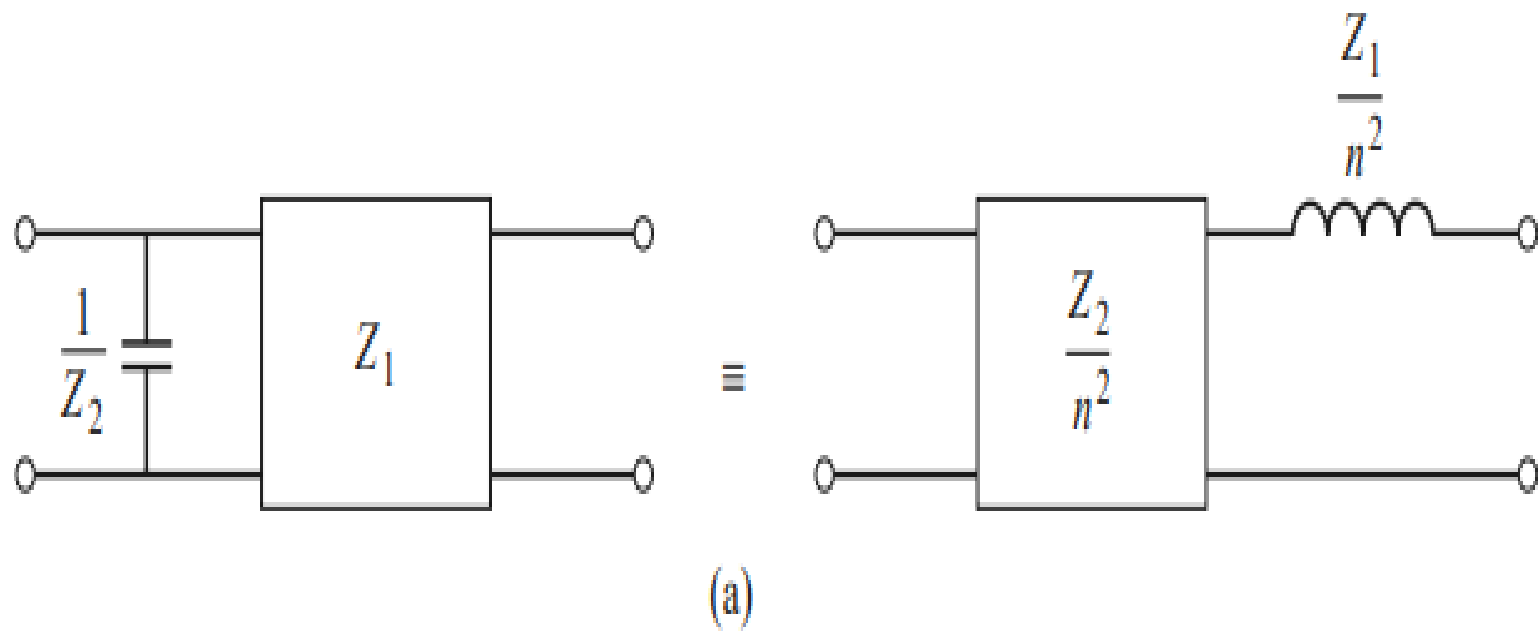Equivalent circuits illustrating Kuroda identity (a) in Table 8.7



# Problems

3. Design a lowpass filter for 3dB equi-ripple response for following specifications: frequency of operation 4 GHz, 3<sup>rd</sup> order,, impedance  $50\Omega$ . Consider a T section prototype and implement using shunt stub.
4. Design a lowpass filter for the following specifications: frequency of operation 4 GHz, 3<sup>rd</sup> order, maximally flat response, impedance  $50\Omega$ . Consider a T section prototype and implement using shunt stub.


5. Design a low-pass, third-order, maximally flat filter using only series stubs. The cutoff frequency is 6 GHz and the impedance is  $50\Omega$ .
6. Design a low-pass, third-order, 3 dB ripple Chebyshev filter using series stubs only. The cutoff frequency is 6 GHz and the impedance is  $50\Omega$ .
7. Design 4<sup>th</sup> order maximally flat filter using shunt stubs at 8 GHz and the impedance is  $50\Omega$ .

# Stepped Impedance Filter

Stepped impedance filter

- Easiest method to implement LPF
- Use low and high impedances
- Popular because, less space than stubs
- Sharp cutoff not possible due to approximation

# Stepped Impedance Filter

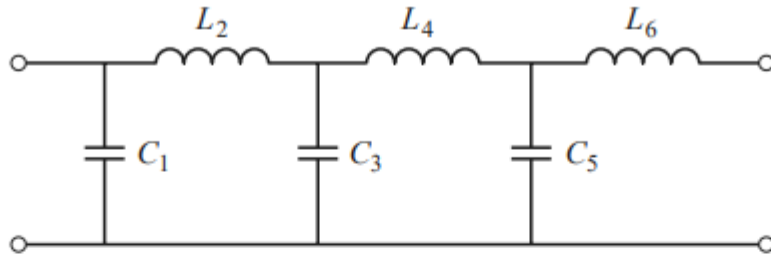


(a)

Inductor


$$\beta l = \frac{LR_0}{Z_h}$$

Capacitor

$$\beta l = \frac{CZ_l}{R_0}$$

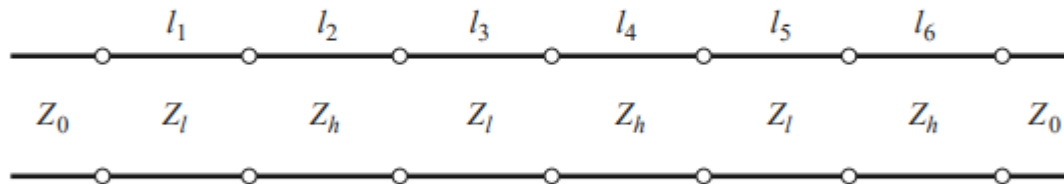

(b)

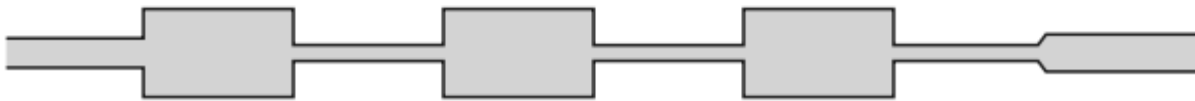

(c)


a. LPF Prototype b. Stepped impedance implementation c. Microstrip Layout

$R_0$  is the filter impedance; L, C are element values from the table.

# Filter Design

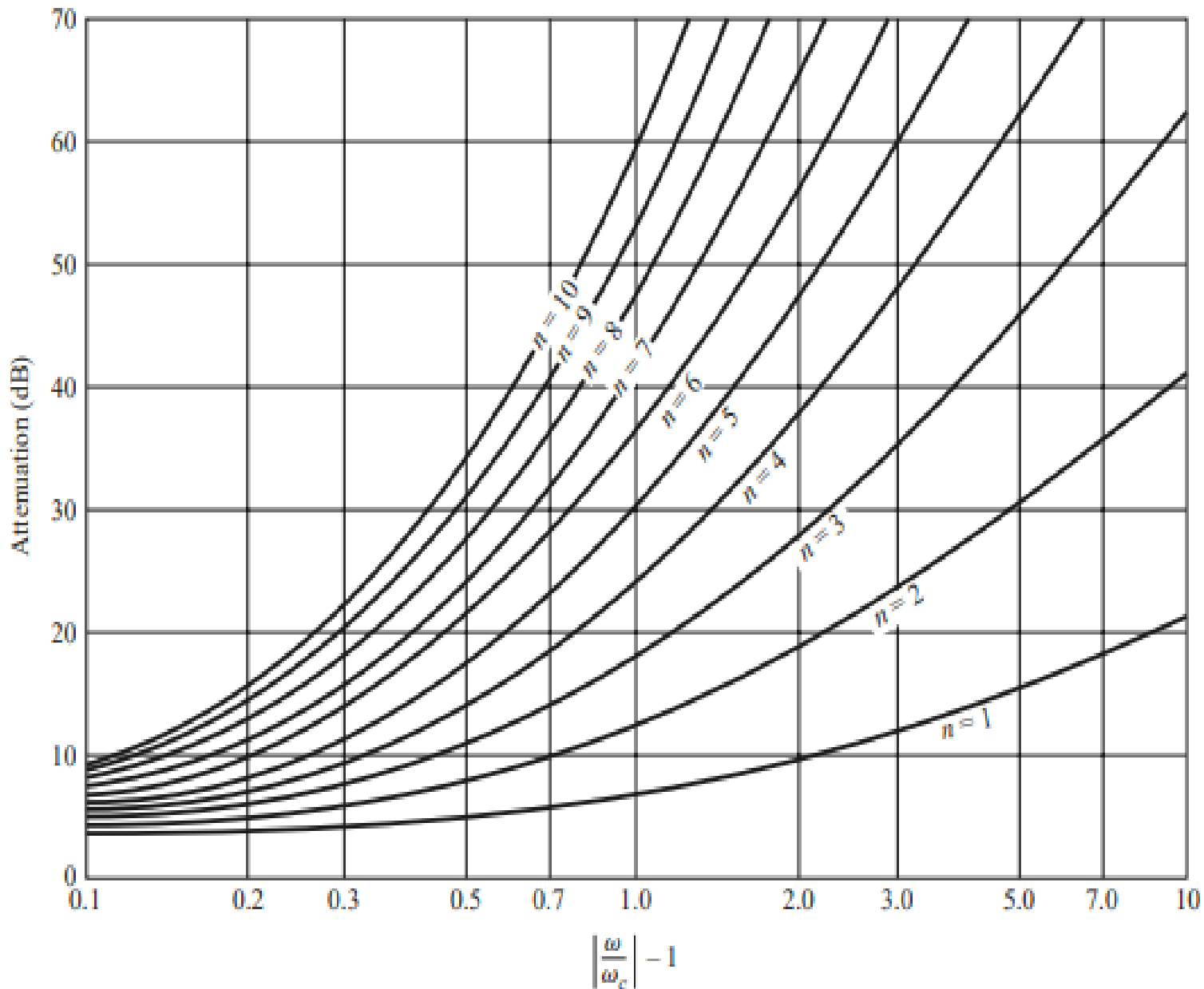8. Design a stepped-impedance low-pass filter having maximally flat response and a cut off frequency of 2.5 GHz. It is necessary to have more than 20 dB insertion loss at 4 GHz. The filter impedance is  $50\ \Omega$ . The highest practical line impedance is  $150\ \Omega$  and the lowest is  $10\ \Omega$ .
9. Design a stepped-impedance low-pass filter with  $f_c = 2.0\ \text{GHz}$  and  $R_0 = 50$ . Assume a maximally flat  $N = 5$  response, and solve for the necessary line lengths and impedances if  $Z_1 = 10\ \Omega$  and  $Z_h = 150\ \Omega$





Attenuation versus normalized frequency for maximally flat filter prototypes

a cutoff frequency of --- GHz and a fifth-order / 0.5 dB equal-ripple response. Assume  $R_0 = 50\Omega$ ,  $Z_1 = 15\Omega$ , and  $Z_h = 120\Omega$ .

- (a) Find the required electrical lengths of the five sections,
- (b) Lay out the microstrip implementation of the filter on an substrate having  $\epsilon_r = 4.4$ , thickness  $h = 1.6$  mm, with copper conductor of 0.5 mil thick. Use CAD to plot the insertion loss versus frequency in the passband of the filter

# Filter Response

